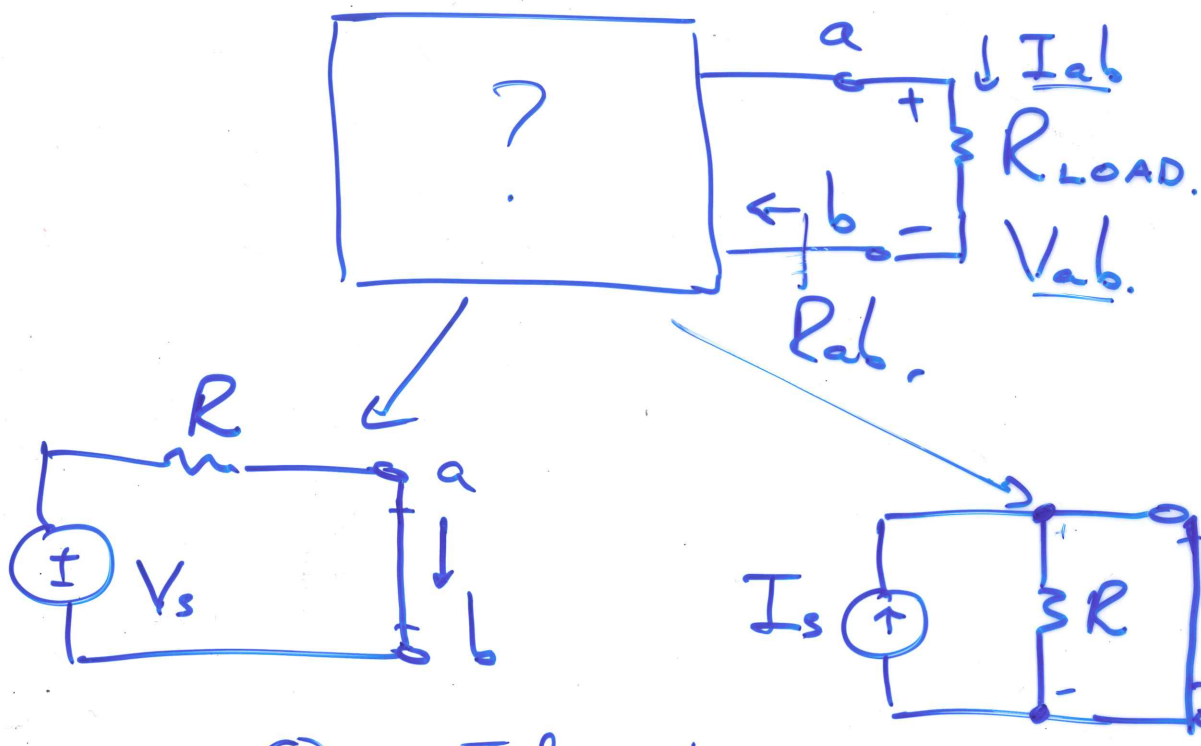


* Source Transformation.



- ① * If a-b is Open Circ $V_{ab} = ?$ ✓
- ② * If a-b is Short Circuit $I_{ab} = ?$ ✓
- ③ * If sources are off. $R_{ab} = ?$

① $V_{ab} = V_s = 10$

① $V_{ab} = I_s R = 10$


② $I_{ab} = V_s / R$

② $I_{ab} = I_s = 1A$

③ $R_{ab} = R = 10$


③ $R_{ab} = R = 10$

$$R_L = 10\Omega$$

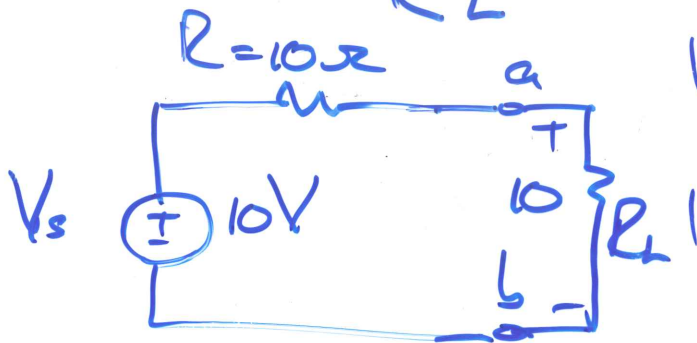




$$V_{ab} = 5V$$

$$I_{ab} = 10/20 = \frac{1}{2}A$$

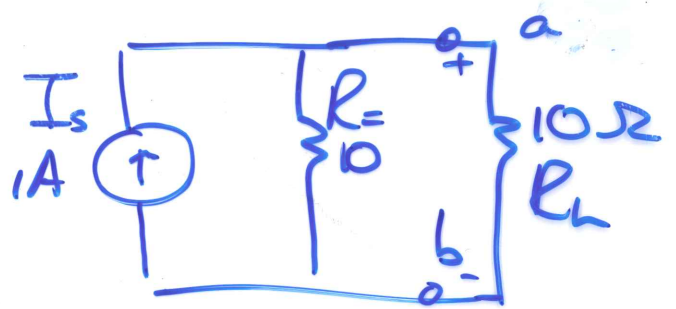

$$V_{ab} = 5V$$

$$I_{ab} = 5/10 = \frac{1}{2}A$$

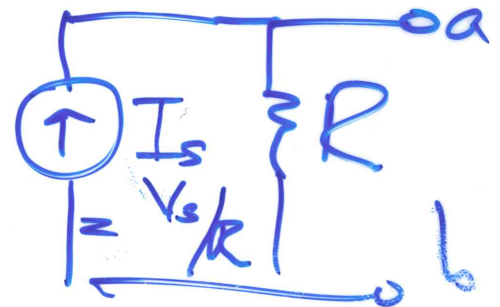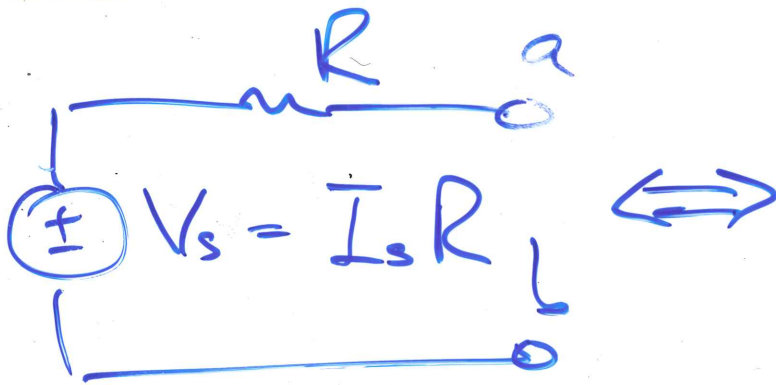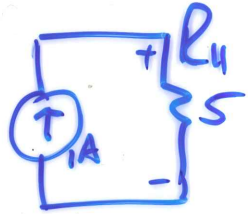

Equivalent