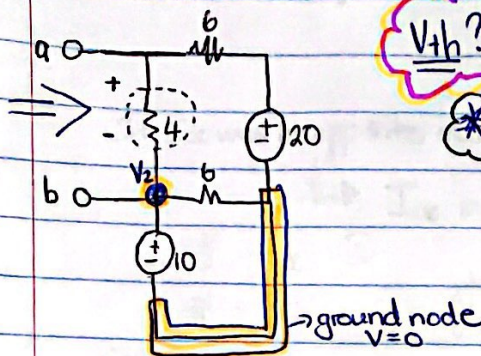


16 April
EBN:



V_{th} ?

need voltage of 4Ω

* method: Nodal

* But you know that $V_2 = 10V$

$$\frac{V_1 - 20}{6} + \frac{V_1 - 10}{4} = 0$$


$$V_1 = 14V$$

But it is a imaginary supernode.

$$V_1 - V_2 = V_{ab} = V_{th}$$

$$14 - 10 = 4V = V_{th}$$


Norton:

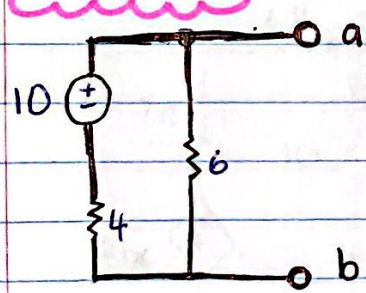

- ① 1 step: close a gap with a line
- ② Assign current moving from a to b.


Norton: I_N

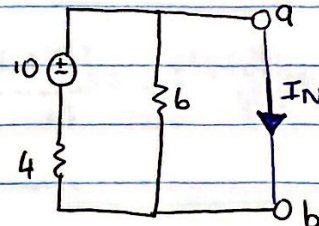→ we will use nodal or KVL only when you have one box.




- Doing with respect to a-b. So current is different than from R_{th}

⊕ ↑

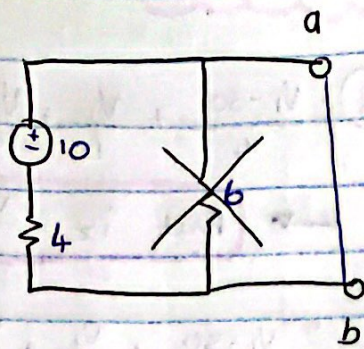

→ Remove resistor
as $V=0$
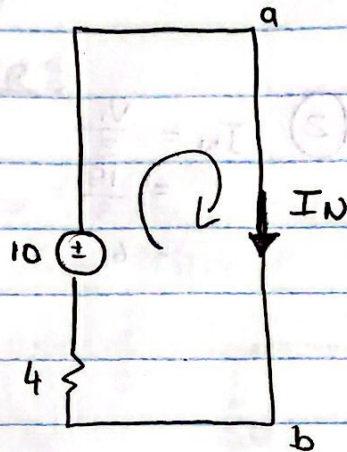
$$\text{as } \begin{cases} I = \frac{V}{R} \\ 0 = \frac{V}{R} \\ 0 = V \end{cases}$$




Do KVL:

$$4 I_N = 10$$

$$I_N = 2.5$$


Ex2:

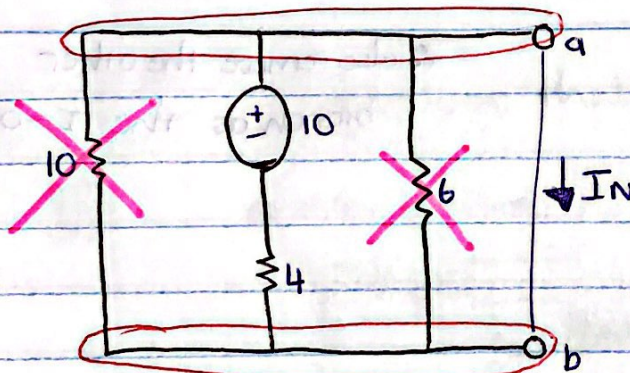

→ when you close a line: check if you have parallel resistors
→ check nodes then you will see the parallel resistors.

Then do KVL

Ex3:

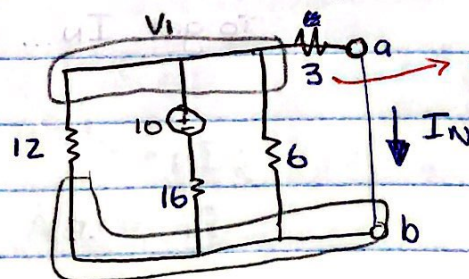


$$\frac{V_1}{12} + \frac{V_1 - 10}{16} + \frac{V_1}{6} + \frac{V_1}{3} = 0$$

$$V_1 = \dots$$

So then $I_N = \frac{V_1}{3}$

Ex 3:

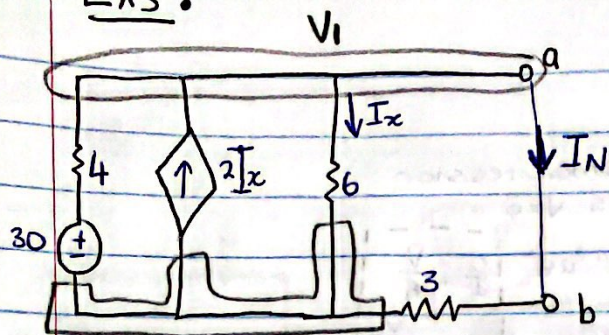

Calculate I_N .

$$(1) \frac{V_1 - 30}{4} + \frac{V_1}{6} + \frac{V_1}{3} - 2I_x = 0$$

→ But $I_x = \frac{V_1}{6}$

$$\frac{V_1 - 30}{4} + \frac{V_1}{6} + \frac{V_1}{3} - 2\left(\frac{V_1}{6}\right) = 0$$


$$V_1 = 18V$$

$$(2) I_N = \frac{V_1}{3}$$

$$= \frac{18}{3}$$


$$= 6$$

Ex 4:

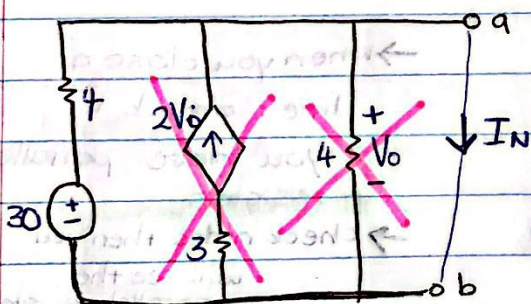

→ $V_o = 0$ because of the parallel.

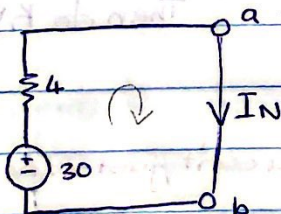• also remove the other branch as the $I = 0$



Then you can use KVL
To get I_N ...


$$4I_N = 30$$

$$I_N = 7.5A$$

Ex 5:


$\rightarrow V_0 = 0$

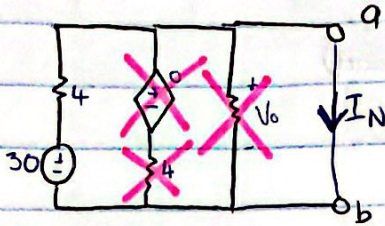$\rightarrow$ then the 4Ω also cancels out as the 4Ω is in parallel again...



MAX POWER:


$$P_{\max} = \frac{V_{th}^2}{4R_{th}}$$

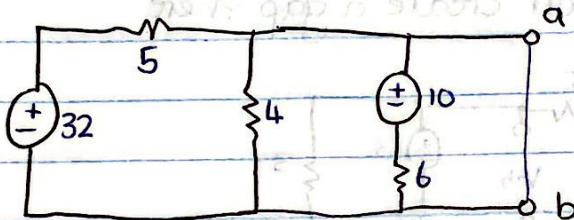

Make sure that you have a gap $\rightarrow V_{th}$

R_{th} :

① close with line

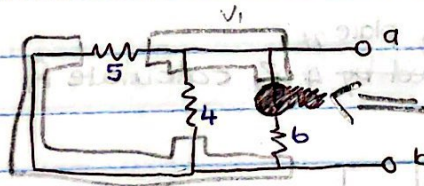

② use $\frac{1}{r_p} = \frac{1}{5} + \frac{1}{4} + \frac{1}{6}$
 $r_p = 1.62 \Omega$


V_{th}

$$\frac{V_1 - 32}{5} + \frac{V_1}{4} + \frac{V_1 - 10}{6} = 0$$

$$V_1 = 13.08$$


$\rightarrow P_{\max} = \frac{(13.08)^2}{4(1.62)}$

when they ask for R load:

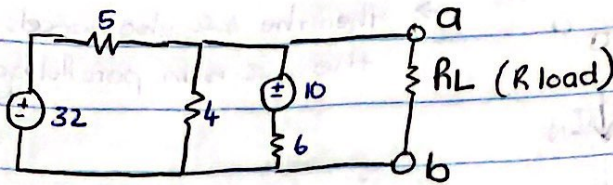


Calculate P_{max} absorbed by R_{load}

You should make a gap:

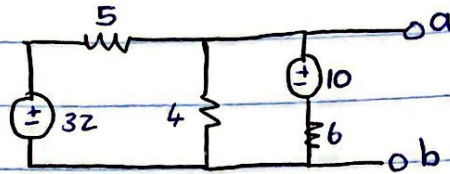

when you calculate V_{th} they will always give you a gap.

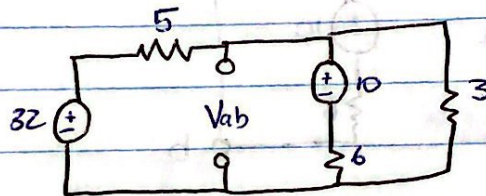
OR if they say at 4Ω for example then you create a gap there



$$\frac{V_{th} - 32}{5} + \frac{V_{th} - 10}{6} + \frac{V_{th}}{3} = 0$$


Ex 6

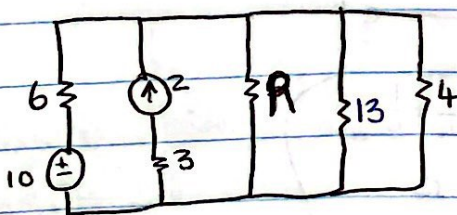
taking place at P_{max} absorbed by 4Ω calculate R



$\therefore R_{th}$ is 4Ω because they say P_{max} is taking place there.

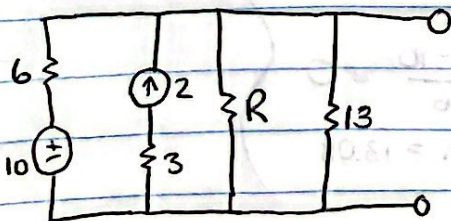$\rightarrow$ go on as if calculating R_{th} .



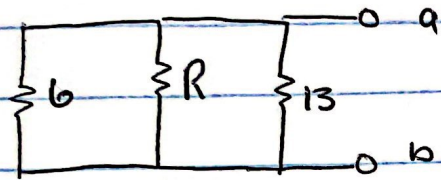

$$\left(\frac{1}{6} + \frac{1}{R} + \frac{1}{13}\right)^{-1} = 4$$

$$R = 156 \, \Omega$$