
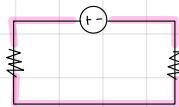





NODAL ANALYSIS

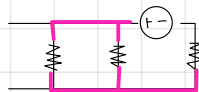



- identify nodes
- use node attached to 3/more branches/lines



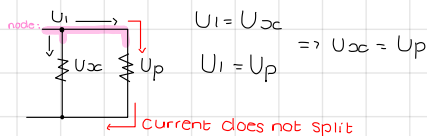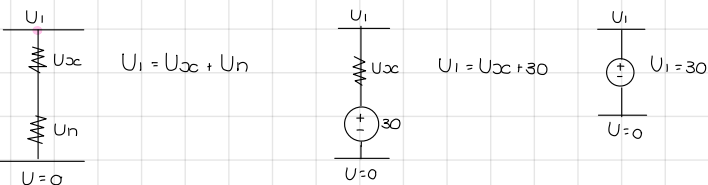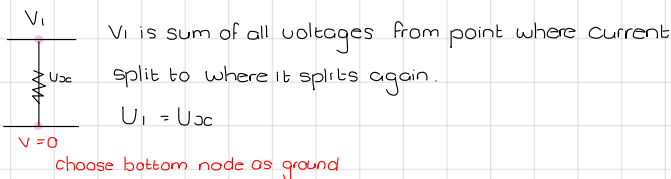- usable nodes: attached 3
- * reason: place where current splits




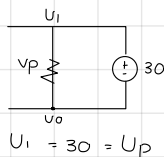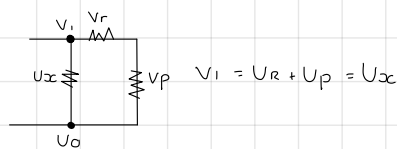if 2/more branches share 2 nodes, they are //
L // same voltage



nodal analysis steps

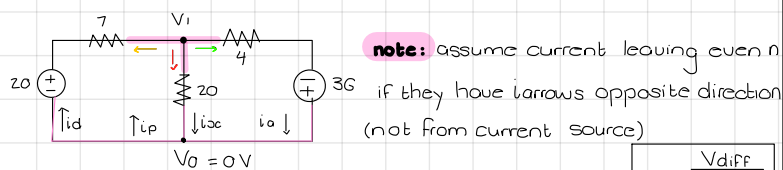1. Identify nodes: connected 3/more lines/branches
2. Assign variables & 1 node as ground (U=0)
3. check for supernodes: and if -> take it out by using supernode equation, then combine the remaining nodes
4. Assume current is leaving the node, unless otherwise stated (original current source opposing assumed direction)
5. Apply nodal analysis




note: assume current leaving even if they have arrows opposite direction (not from current source)

$$\frac{V_1 - (+20) - 0}{7} + \frac{V_1 - (0) - 0}{20} + \frac{V_1 - (-36) - 0}{4} = 0$$

$$V_1 = -13,87 \text{ V}$$

$$i_{xc} = \frac{V_1}{20} = -0,69 \quad i_{yp} = \left(\frac{V_1}{20} \right) = 0,69$$
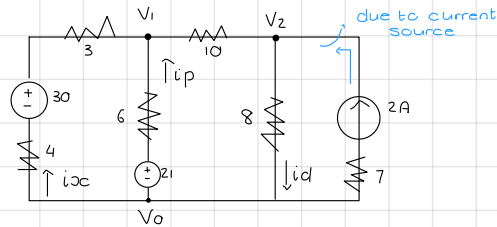
$$i_d = -\left(\frac{V_1 - 20}{7} \right) = 4,84 \quad i_a = \frac{V_1 + 36}{4} = 5,53$$



$$V_1: \frac{V_1 - (-30) - 0}{3+4} + \frac{V_1 - (-21) - 0}{6} + \frac{V_1 - (0) - V_2}{10} = 0$$

$$\frac{V_1}{7} - \frac{30}{7} + \frac{V_1}{6} - \frac{21}{6} + \frac{V_1}{10} - \frac{V_2}{10} = 0$$

$$V_1 \left(\frac{1}{7} + \frac{1}{6} + \frac{1}{10} \right) + V_2 \left(-\frac{1}{10} \right) = \frac{30}{7} + \frac{21}{6}$$

$$V_1 \left(\frac{43}{105} \right) + V_2 \left(-\frac{1}{10} \right) = \frac{109}{14}$$

$$V_2: \frac{V_2 - (0) - V_1}{10} + \frac{V_2 - (0) - 0}{8} - 2 = 0$$


$$\frac{1}{10} V_1 + \frac{9}{40} V_2 = 2$$

$$V_1 = 23,76 \text{ V} \quad V_2 = 19,45 \text{ V}$$

$$i_{xc} = -\left(\frac{V_1 - 30}{7} \right) = 0,89 \text{ A} \quad i_p = -\left(\frac{V_1 - 21}{6} \right) = 0,39 \text{ A}$$

$$i_d = \frac{V_2}{8} = 2,43 \text{ A}$$

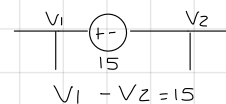SUPERNODE: voltage source between 2 node voltages without a resistor being involved





when you see a supernode you take it out by using an equation


equation

node voltage close to + polarity of middle voltage
- node voltage close to - polarity of middle voltage
middle voltage

imaginary supernode:

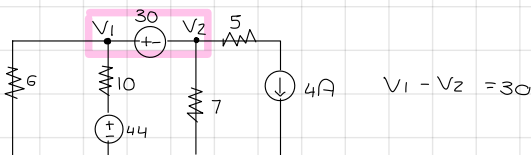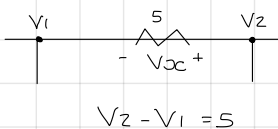

$$V_1 - V_2 = 30$$

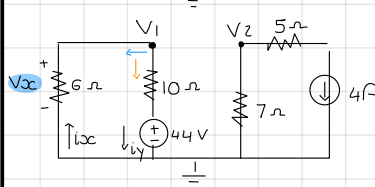

$$\frac{V_1}{6} + \frac{V_1 - 44}{10} + \frac{V_2}{7} + 4 = 0$$

$$\frac{4}{15} V_1 + \frac{1}{7} V_2 = \frac{2}{5}$$

$$\text{node 1} + \text{node 2} = 0$$

$$V_1 = 11,44 \quad V_2 = -18,56$$

Current cases

- $i_{xc} = -\left(\frac{V_1}{6} \right) = -1,907$
- $i_y = \frac{V_1 - 44}{10} = -3,256$