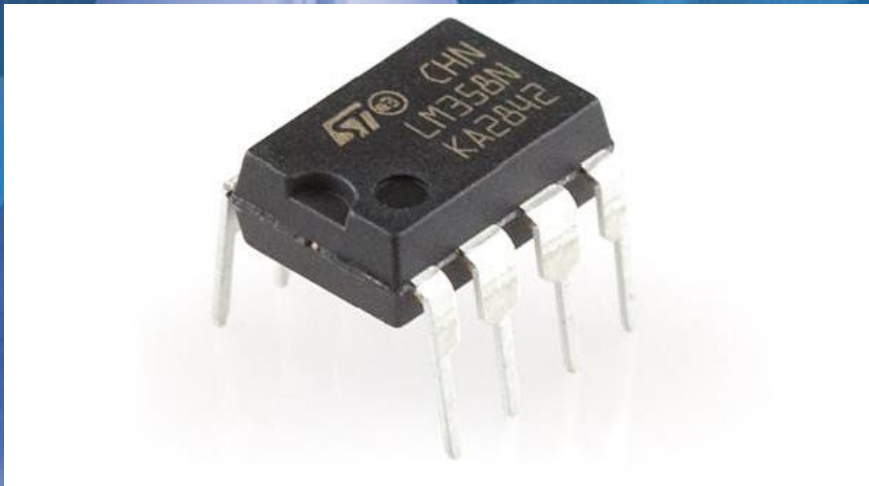


UNIVERSITY OF PRETORIA

Introduction to Operational Amplifier Circuits

(EBN 122: Electricity and Electronics)



22 September 2017

Department of Electrical, Electronic and
Computer Engineering



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Denkleiers • Leading Minds • Dikgopolo tša Dihalefi

Introduction




- Build **two Op-Amp** circuits
- Record the circuit characteristics
 - Input voltage vs Output voltage
- **Important:** Read about the basic concepts in your textbook
- During the practical you will receive the following:
 - **One UA741 Op-amp per group**
 - Connecting wires



Op-Amp



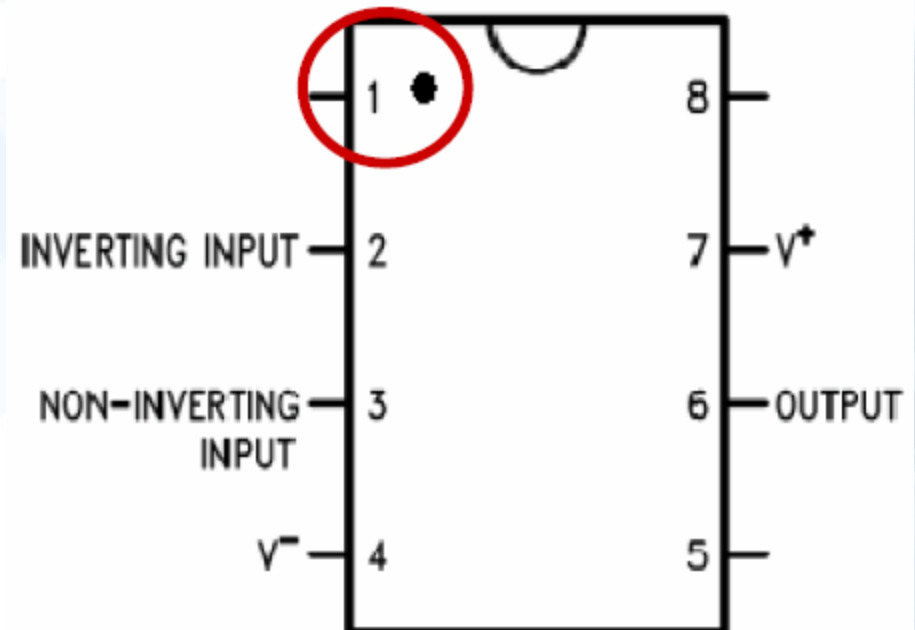
- Op-Amp: High-gain voltage amplifier with a differential input (+ and -) and usually a single-ended output.
- Used to perform mathematical operations on voltage signals.
 - Inversion
 - Addition
 - Subtraction
 - Integration
 - Etc.




Op-Amp



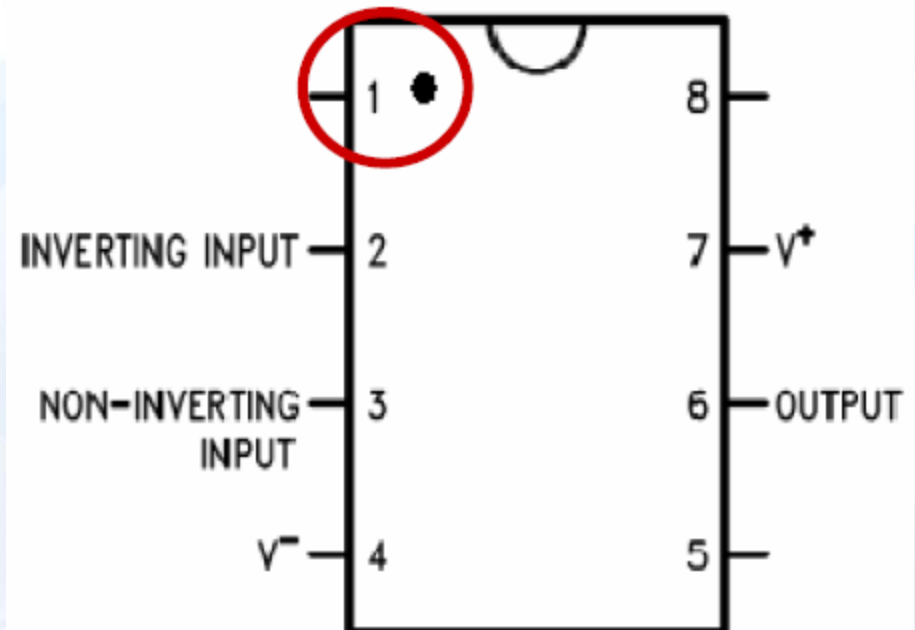
- Op-Amp used for this practical: 8 pin Dual In-Line Package.
- The pins correspond to the various inputs and outputs of the Op-Amp.
- **Note: Pin 1** is identified with the **dot (encircled in red)** next to it and all other pins are **counted counter-clockwise** from pin 1.



Op-Amp

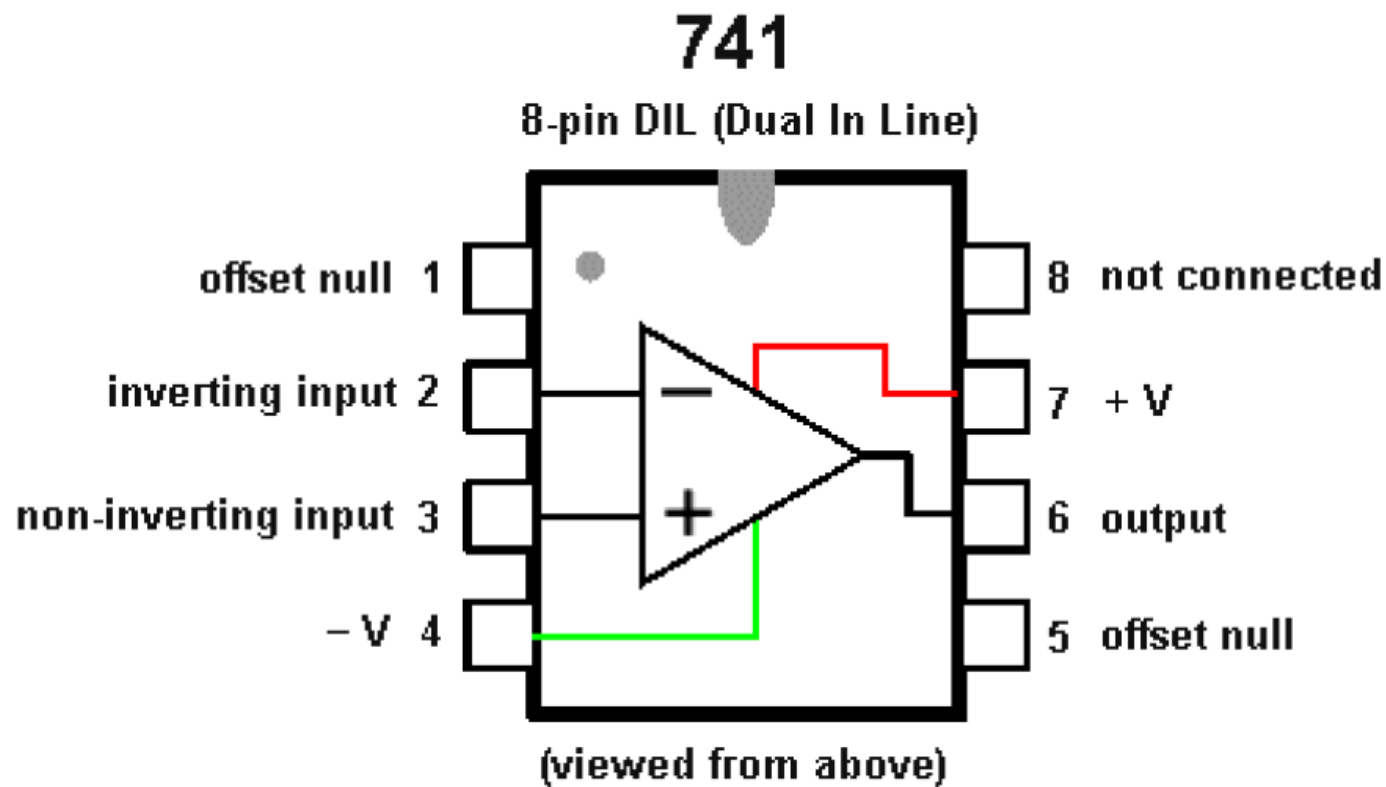


Constructions on Breadboard

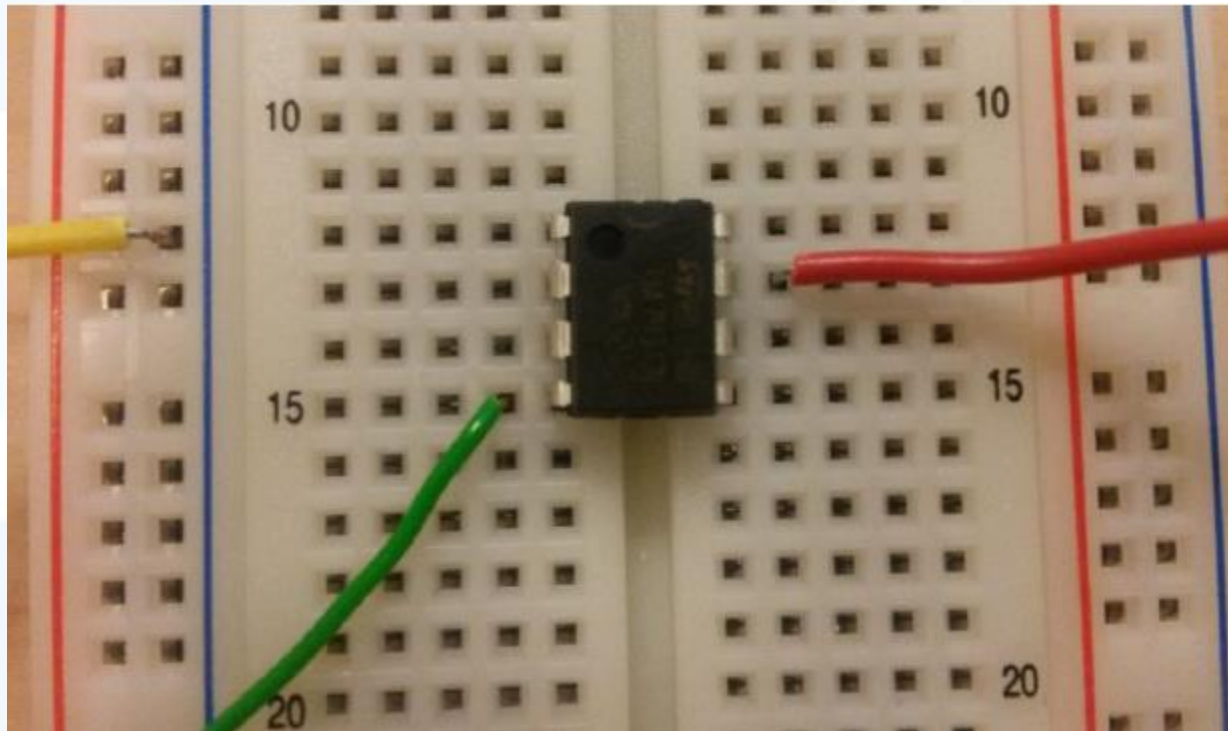



Constructions on Breadboard

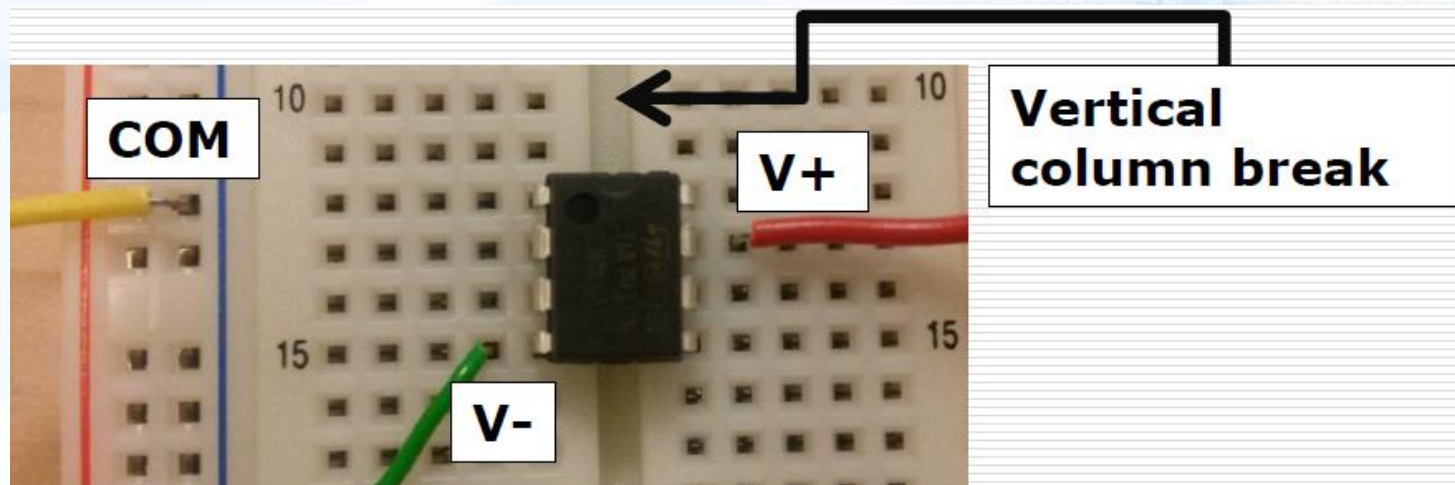- Place the Op-Amp on the breadboard so that pin 1-4 and 5-8 are separated by the **vertical column break** on the board – *as indicated below*.
- **Hint:** Connect the -12V (pin 4), +12V (pin 7) and ground (COM) rails to the breadboard as indicated.
- **Read practical 3 guidelines for more detail.**



Workstation



Power Supply



Function generator (Oscilloscope)



Practical Preparation



- **Important:** Lab rules

www.up.ac.za/en/eece/article/2008415/undergraduate-laboratory-rules



- NO FOOD OR DRINKS



- NO FLIP-FLOPS
- NO OPEN TOED SHOES
- NO BARE FEET



- NO HATS
- NO BEANIES
- NO HOODIES



- NO LISTENING TO MUSIC OR PLAYING ON CELL PHONES DURING THE PRACTICAL

Practical Preparation



- **Important:** Lab rules


www.up.ac.za/en/eece/article/2008415/undergraduate-laboratory-rules

- Practical 3 **guidelines** are available on **clickUP**.
- Bring your **component boxes**.



Practical Test Preparation

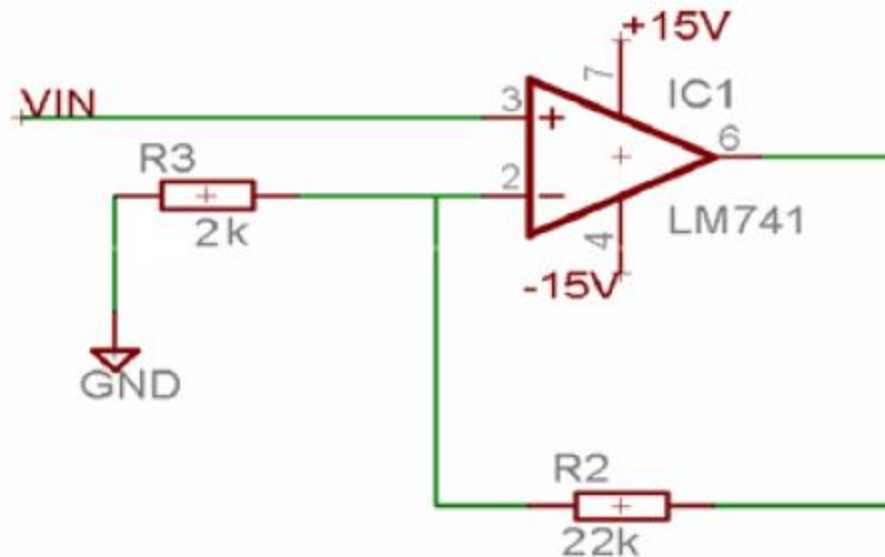
- You should be able to answer the following questions:
 - Is this an inverting or non-inverting amplifier?
 - Calculate the theoretical gain of the amplifier.
 - What is the relationship between input and output voltage?



Practical Test Preparation



- Amplification and saturation regions

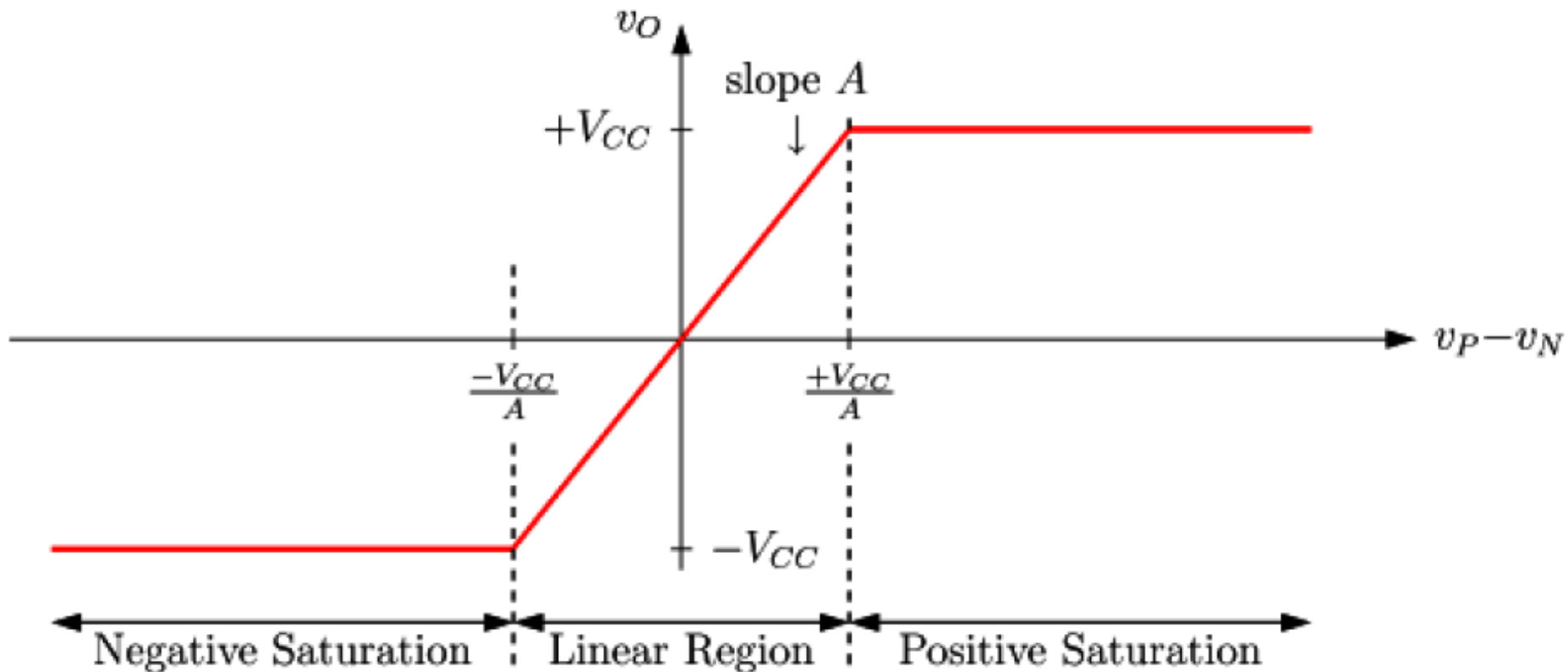

Conclusion



- Handle the Op-Amp with care
- **Please return** the Op-Amp and connecting wires after the practical
- Questions: ebn2017pracs@gmail.com