

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Department of Electrical, Electronic and
Computer Engineering

Semestertoets 2

Kopiereg voorbehou

Semester Test 2

Copyright reserved

Module EBN122
Elektrisiteit en Elektronika
October 2016

Module EBN122
Electricity and Electronics
October 2016



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Exam information:

Eksamensinligting:

Maximum marks: Maksimum punte:	45	Full marks: Volpunte:	46
Duration of paper: Duur van vraestel:	90 minutes 90 minute	Open / closed book: Oopboek / toeboek:	Closed Toe
Total number of pages (including this page): Totale aantal bladsye (hierdie blad ingesluit):	13		

IMPORTANT - BELANGRIK

- The examination regulations of the University of Pretoria apply.*
Die eksamenregulasies van die Universiteit van Pretoria geld.
- All questions must be answered on the ANSWER SHEET.*
Alle vrae moet op die ANTWOORDBLAD beantwoord word.
- Students may do their own rough calculations on the question paper – the question paper will not be taken in.*
Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
- Answers must include units!*
Antwoorde moet eenhede insluit!
- Final answers must be written as real numbers, and not as fractions.*
Finale antwoorde moet as reële getalle geskryf word, en nie as breuke nie.

Dosent(e): Lecturer(s):	1. D le Roux
	2. R dos Santos
	3. J Joubert


VRAAG/QUESTION 1 [8]

Question 1.1 [4]

Using nodal analysis solve for V_S and V_x , if given that $V_0 = 8\text{ V}$.

Vraag 1.1 [4]

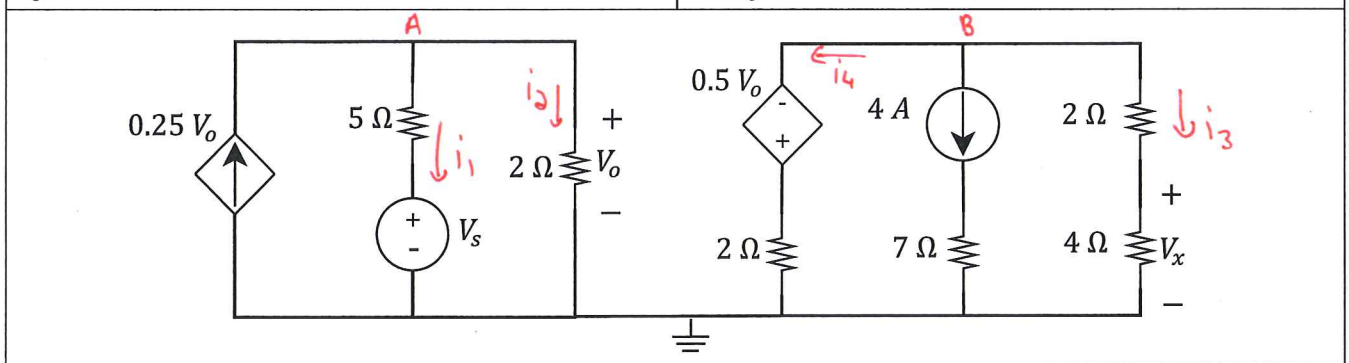Gebruik node analyse om V_S en V_x op te los, indien gegee dat $V_0 = 8\text{ V}$.



KCL at A: $0.25V_0 = i_1 + i_2$

$$0.25V_0 = \frac{V_0 - V_S}{5} + \frac{V_0}{2}$$

$$V_0 = 8\text{ V}$$

$$2 = \frac{8 - V_S}{5} + 4$$

$$10 = 8 - V_S + 20$$

$$V_S = \underline{18\text{ V}}$$

KCL at B: $i_4 + 4 + i_3 = 0$

$$\frac{V_B - (-0.5V_0)}{2} + 4 + \frac{V_B - 0}{2+4} = 0$$

$$V_0 = 8\text{ V}$$


$$\frac{V_B + 4}{2} + \frac{V_B}{6} = -4$$

$$3V_B + 12 + V_B = -24$$

$$4V_B = -36$$

$$V_B = -9\text{ V}$$

$$\text{Voltage Division: } V_x = \frac{4 \times V_B}{2+4} = \frac{4 \times -9}{6} = \underline{-6\text{ V}}$$

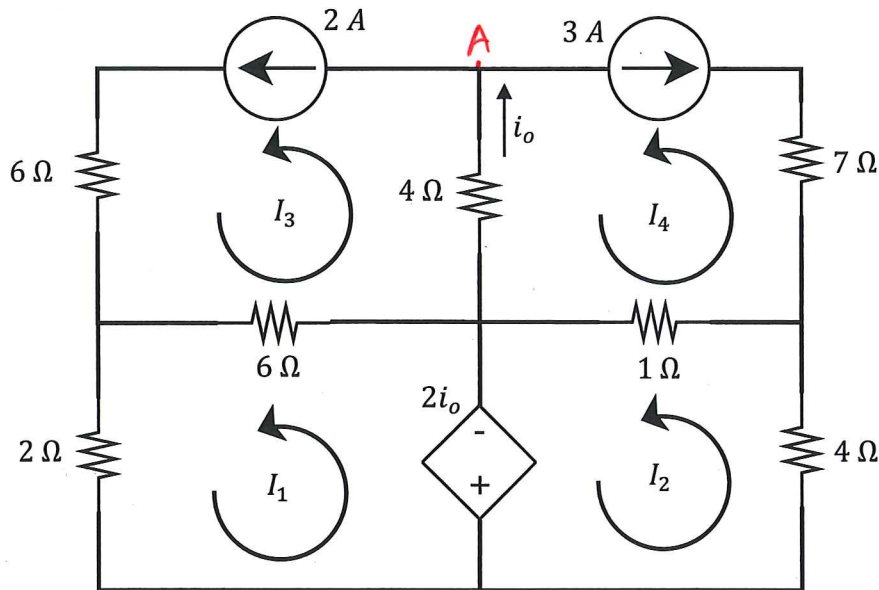Question 1.2 [4]Using mesh analysis determine I_1 and I_2 .**Vraag 1.2 [4]**Gebruik lusanalyse om I_1 en I_2 op te los.

$$I_3 = 2A$$

$$I_4 = -3A$$

$$\text{KCLA: } i_o = 2 + 3 = 5A$$

$$\text{Loop 1: } 2I_1 + 6(I_1 - I_3) + 2i_o = 0$$

$$8I_1 - 6I_3 = -2i_o$$

$$8I_1 = 6I_3 - 2i_o$$

$$8I_1 = 6 \times 2 - 2 \times 5$$

$$I_1 = \frac{2}{8} = 0.25A \rightarrow$$

$$\text{Loop 2: } 4I_2 + 1(I_2 - I_4) - 2i_o = 0$$

$$5I_2 - I_4 = 2i_o$$

$$5I_2 = 2i_o + I_4$$

$$5I_2 = 2 \times 5 + (-3)$$

$$I_2 = \frac{7}{5} = 1.4A \rightarrow$$


VRAAG/QUESTION 2 [22]

Question 2.1 [2]

Using the principle of linearity, determine the ratio: $\frac{I_0}{I_s}$.

Vraag 2.1 [2]

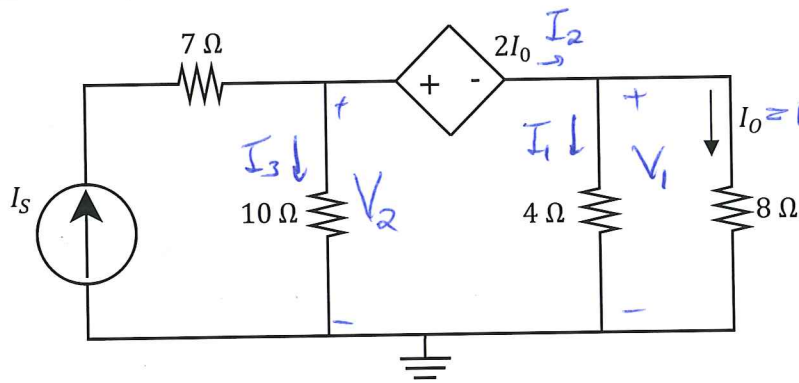Deur gebruik te maak van die beginsel van lineariteit, bepaal die verhouding: $\frac{I_0}{I_s}$.



* Assume $I_0 = 1A$.

$$\rightarrow V_1 = 8V$$

$$\rightarrow I_1 = \frac{8}{4} = 2A$$

$$\rightarrow I_2 = I_1 + I_0 = 3A$$

* KVL: $-V_2 + 2I_0 + V_1 = 0$

$$V_2 = 2(1) + 8 = 10V$$

$$\rightarrow I_3 = \frac{10}{10} = 1A$$

$$\rightarrow I_s = I_2 + I_3 = 3 + 1 = 4$$

$$\frac{I_0}{I_s} = \frac{1}{4} = \underline{0.25}$$



✓✓

Question 2.2 [4]


- a) Determine the individual contribution of the 320 mA current source to V_X .
- b) Determine the individual contribution of the 10 V voltage source to V_X .

Vraag 2.2 [4]

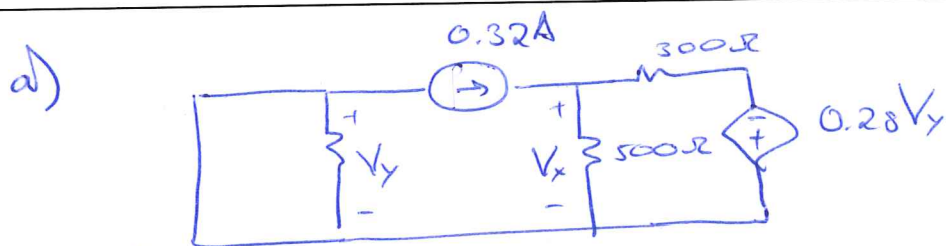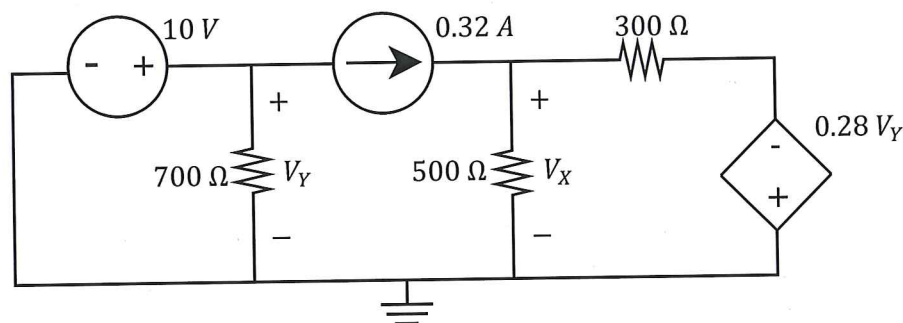- a) Bepaal die unieke bydra van die 320 mA stroombron tot V_X .
- b) Bepaal die unieke bydra van die 10 V spanningsbron tot V_X .




$V_Y = 0V$

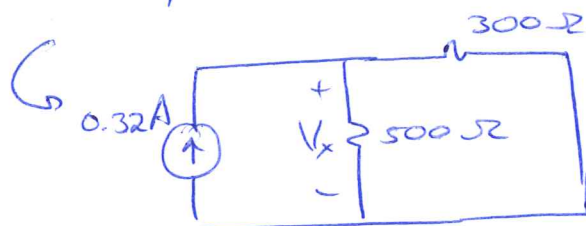

$$V_X = 0.32 \times (300 \parallel 500)$$

$$= \frac{0.32 \times 300 \times 500}{800}$$

$$= \underline{60V} \quad \checkmark$$

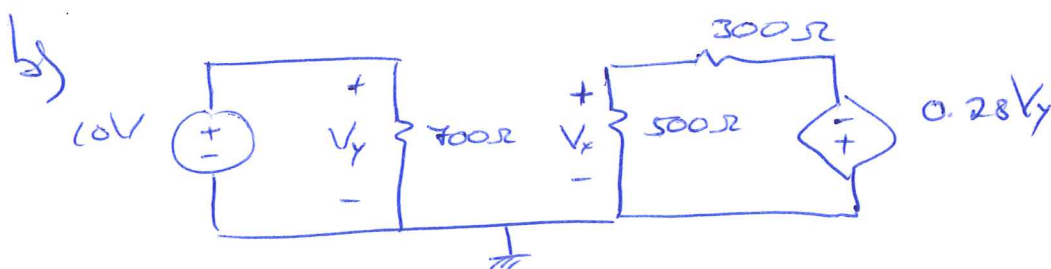

$V_Y = 10V$

$V_X = \frac{500}{800} \times (-0.28V_Y)$ (Voltage divider)






$$= \underline{-1.75V} \quad \checkmark$$

Question 2.3 [4]

The aim is to simplify the circuit on the left to obtain the circuit on the right with respect to the $10\text{ k}\Omega$ resistor. Make use of source transformation and determine V_T and R_T .

Vraag 2.3 [4]

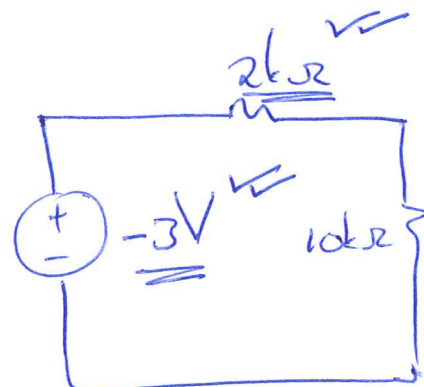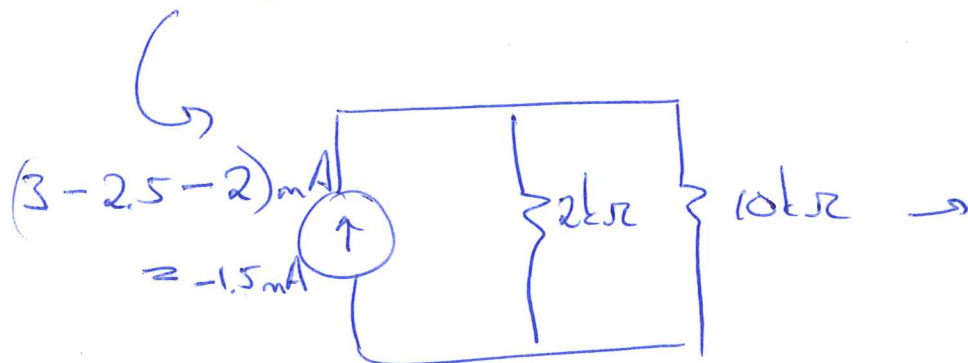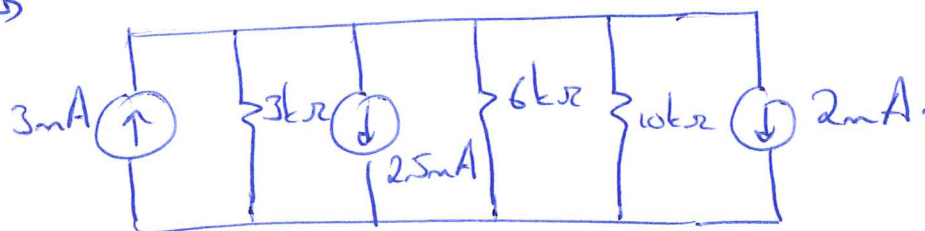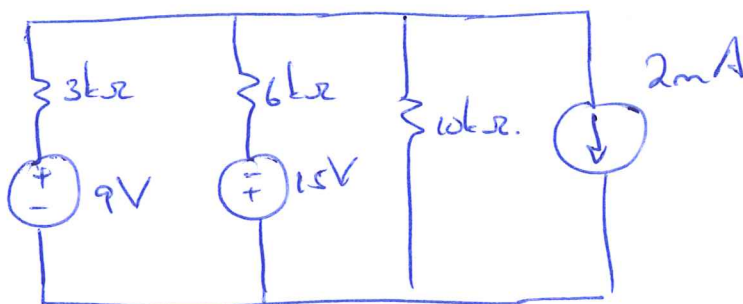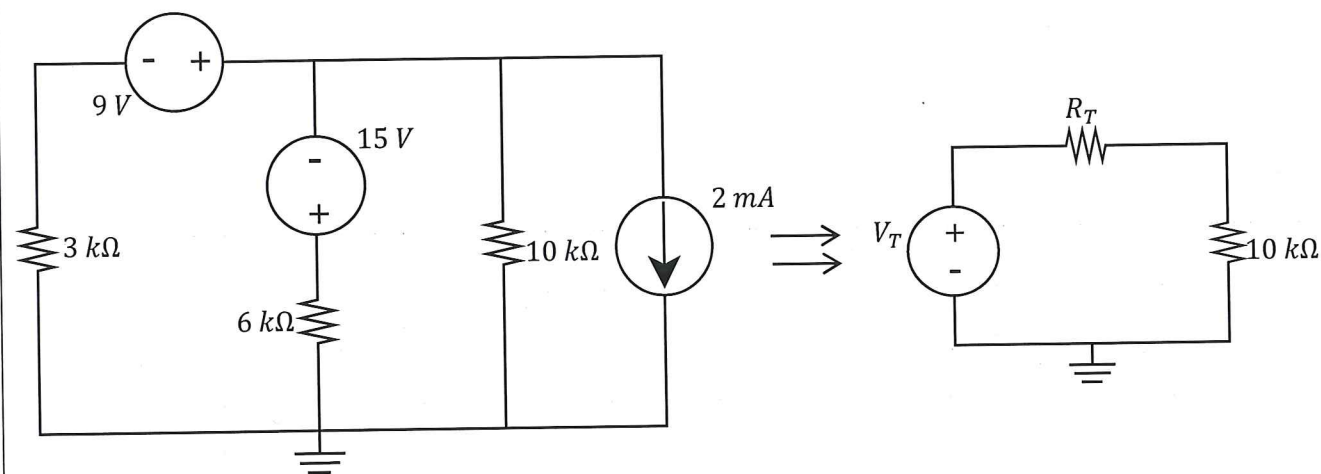Die doel is om die linkerkantse kringbaan te vereenvoudig na die regterkantse kringbaan met verwysing tot die $10\text{ k}\Omega$ weerstand. Maak gebruik van brontransformasie en bepaal V_T en R_T .




$$R_u = 6\text{ k}\Omega \parallel 3\text{ k}\Omega = \frac{6 \times 3}{6 + 3} = \underline{2\text{ k}\Omega}$$

Question 2.4 [4]

Determine the Thevenin equivalent voltage V_{TH} and resistance R_{TH} w.r.t. terminals $a-b$.


Vraag 2.4 [4]

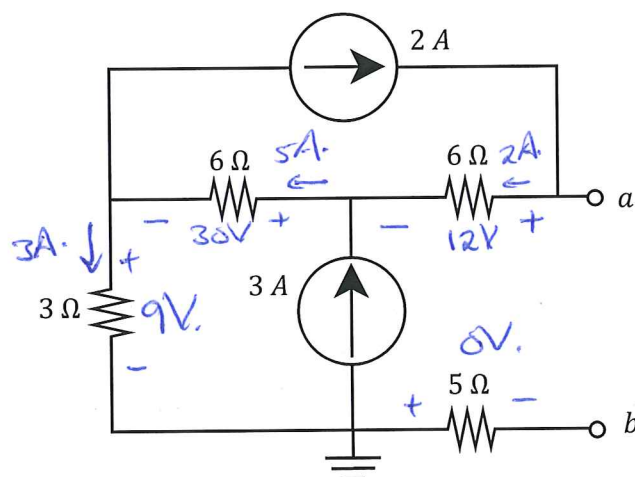Bepaal die Thevenin ekwivalente spanning V_{TH} en weerstand R_{TH} t.o.v. terminale $a-b$.



* V_{TH} KVL: $V_{ab} = 12 + 30 + 9 = \underline{\underline{51V}}$ ✓

* R_{TH} :

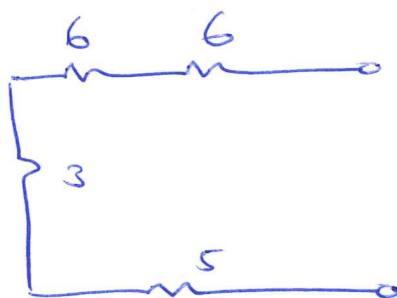

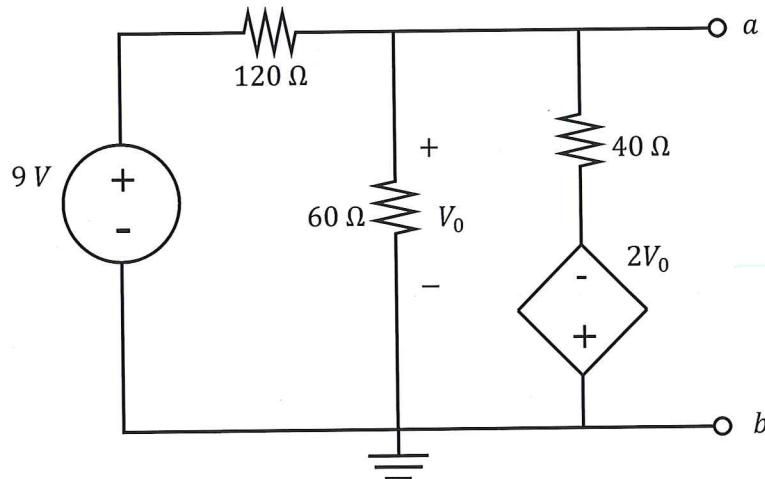
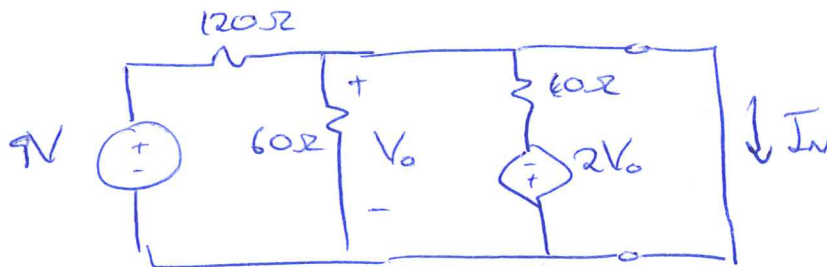
$R_{TH} = 6 + 6 + 3 + 5$
 $= \underline{\underline{20\Omega}}$ ✓

Question 2.5 [4]


Determine the Norton equivalent current I_N and resistance R_N wrt terminals $a-b$.

Vraag 2.5 [4]


Bepaal die Norton ekwivalente stroom I_N en weerstand R_N tov terminale $a-b$.

 I_N 

↳ $V_0 = 0V$

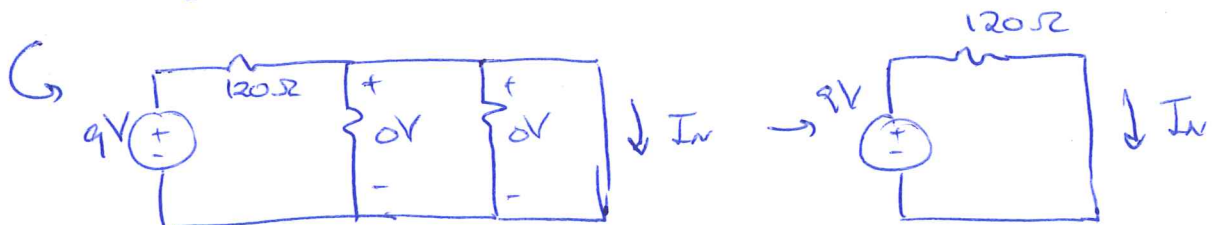

$$I_N = \frac{9}{120} = 75mA \quad \checkmark$$

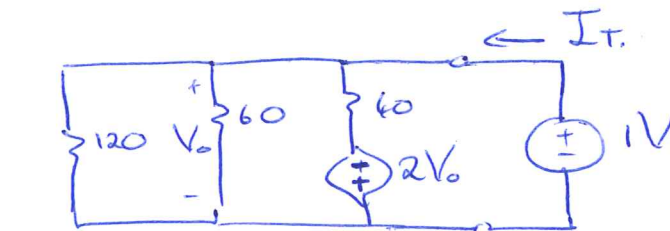 R_N 

↳ $V_0 = 1V$

$$* I_T = \frac{1+2}{40} + \frac{1}{60} + \frac{1}{120} = \frac{1}{10}$$

$$R_N = \frac{1}{I_T} = 10\Omega \quad \checkmark$$

Question 2.6 [4]


The short circuit current of a circuit is $I_N = 6 \text{ mA}$. The circuit delivers maximum power to a load of $R_L = 10 \text{ k}\Omega$.

- a) What is the maximum power P_{max} absorbed by the load resistor R_L ?
 b) If a resistor of $15 \text{ k}\Omega$ is placed in parallel to the load resistor R_L , what is the total power absorbed by the parallel combination? (I.e. the total power absorbed by the combined resistance $(15 \parallel 10) \text{ k}\Omega$.)



Vraag 2.6 [4]

Die kortsluitstroom van 'n kringbaan is $I_N = 6 \text{ mA}$. Die kringbaan lewer maksimum drywing aan 'n las van $R_L = 10 \text{ k}\Omega$.

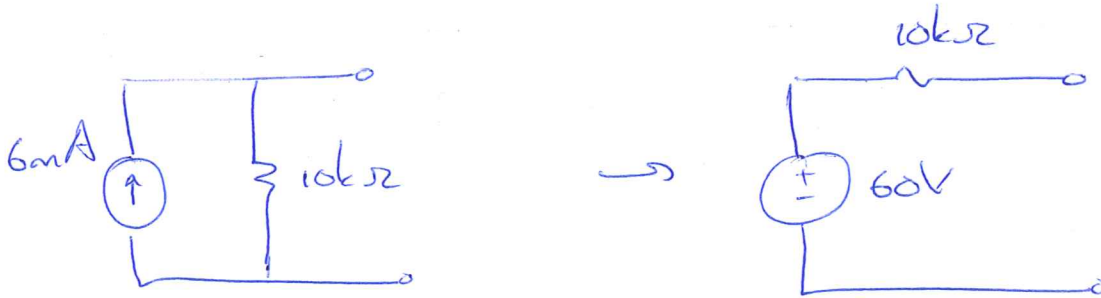- a) Wat is die maksimum drywing P_{max} wat deur die lasweerstand verkwis word?
 b) Indien 'n weerstand van $15 \text{ k}\Omega$ parallel aan die las weerstand R_L gekoppel word, wat is die totale drywing wat deur die parallelle kombinasie geabsorbeer word? (M.a.w. die total drywing geabsorbeer deur die gekombineerde weerstand $(15 \parallel 10) \text{ k}\Omega$.)


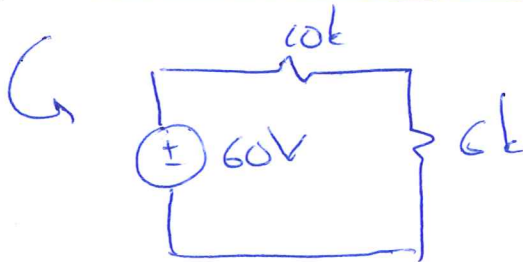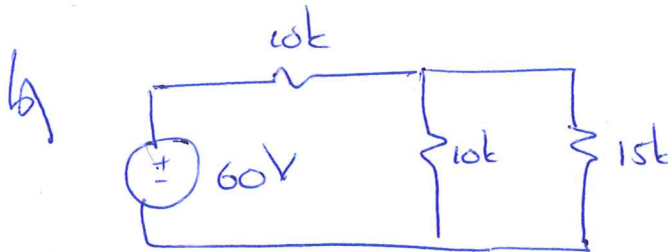
$$a) P_{max} = \frac{V_{TH}^2}{4 R_{TH}} = \frac{60^2}{4 \times 10k} = \underline{90 \text{ mW}}$$



$$P_6 = i^2 \cdot R = \left(\frac{60}{16k} \right)^2 \times 16k = \underline{84,375 \text{ mW}}$$


VRAAG/QUESTION 3 [16]

Question 3.1 [4]

- a) Calculate V_0 if $V_a = 2V$ and $V_b = 1V$.
 b) Calculate V_0 if $V_a = -3V$ and $V_b = 0V$.

Vraag 3.1 [4]

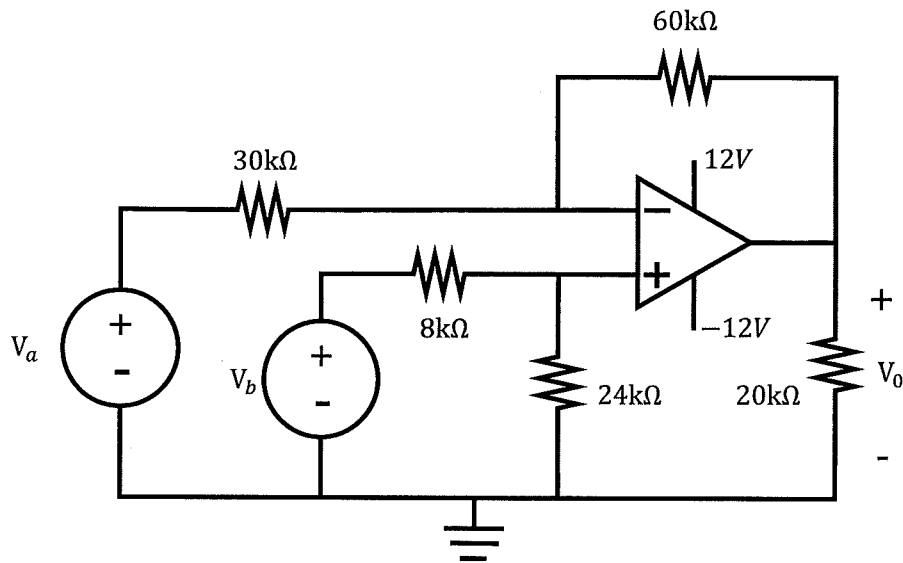- a) Bereken V_0 as $V_a = 2V$ en $V_b = 1V$.
 b) Bereken V_0 as $V_a = -3V$ en $V_b = 0V$.



$$a) \quad V_b = 1V \Rightarrow V^+ = \frac{24}{32} \times 1 = 0.75V$$

$$\text{KCL @ } V^-: \quad \frac{0.75 - 2}{30k} + \frac{0.75 - V_0}{60k} = 0$$

$$\times 60k: \quad 2(-1.25) + 0.75 - V_0 = 0$$

$$\Rightarrow V_0 = -1.75V \checkmark \checkmark$$


$$b) \quad V_0 = -\frac{60}{30} \times (-3) = 6V \checkmark \checkmark$$

Question 3.2 [4]

- a) Determine V_1 if $V_s = 4V$.
 b) Determine the range of values of V_s that will ensure that the op-amp operates in the linear region.

Vraag 3.2 [4]

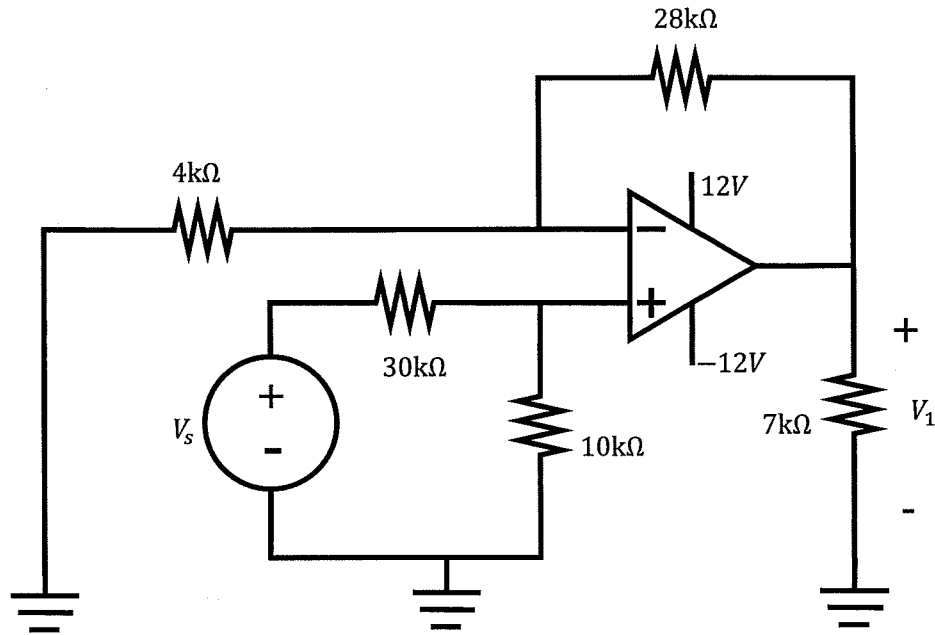- a) Bepaal V_1 as $V_s = 4V$.
 b) Bepaal die omvang van waardes van V_s wat sal verseker dat die operasionele versterker in sy lineêre gebied sal funksioneer.



$$a) \quad V_s = 4 \Rightarrow V^+ = \frac{10}{40} \times 4 = 1V$$

$$\text{KCL at } V^-: \quad \frac{1-0}{4k} + \frac{1-V_1}{28k} = 0$$

$$\times 28k: \quad 7 + 1 - V_1 = 0 \\ \Rightarrow \underline{V_1 = 8V} \checkmark \checkmark$$

$$b) \quad \frac{\frac{V_s}{4} - 0}{4k} + \frac{\frac{V_s}{4} - V_1}{28k} = 0 \Rightarrow V_1 = 2V_s$$


$$\Rightarrow \underline{-6 < V_s < 6} \checkmark \checkmark \\ \text{will imply } -12 < V_1 < 12$$

Question 3.3 [4]Determine values of R_b and R_f so that

$$V_0 = 2000i_b - 2000i_a.$$

Vraag 3.3 [4]Bepaal waardes vir R_b en R_f sodat

$$V_0 = 2000i_b - 2000i_a.$$

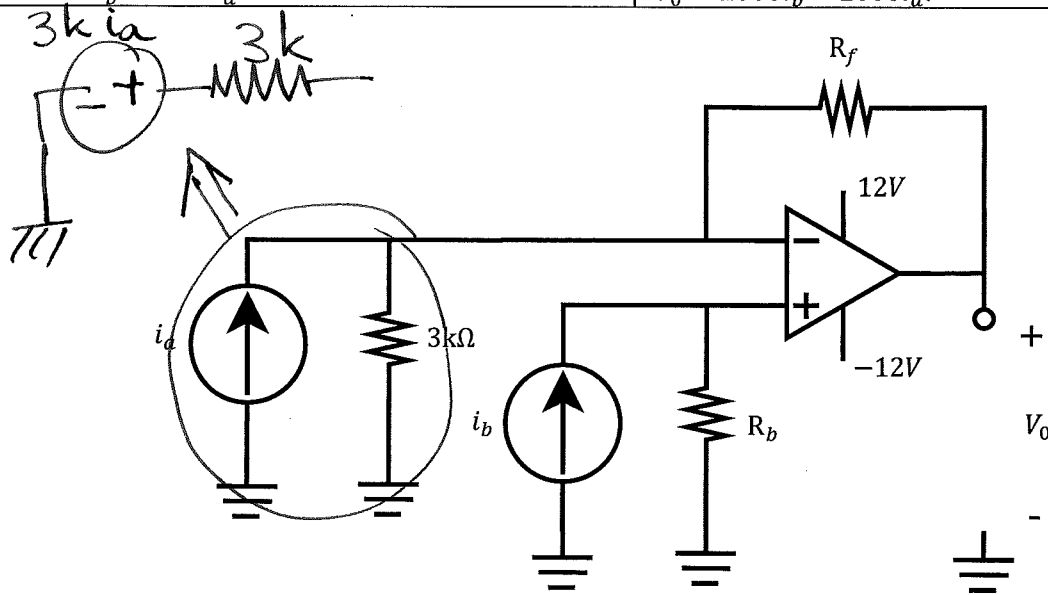

Superposition:

$$V_0 = i_b R_b \times \left(\frac{R_f}{3k} + 1 \right)$$

(non inverting)

$$- 3k i_a \cdot \frac{R_f}{3k}$$

(inverting)

$$= 2000 i_b - 2000 i_a$$

$$\Rightarrow R_f = 2000 \Omega \checkmark \checkmark$$

$$R_b \left(\frac{R_f}{3k} + 1 \right) = 2000 \Rightarrow R_b = \frac{2000}{\frac{2000}{3000} + 1}$$


$$= 1200 \Omega \checkmark \checkmark$$

Question 3.4 [4]

- a) Determine the amplification factor V_2/V_1 .
 b) Determine i_3 if $V_2 = 2V$.

Vraag 3.4 [4]

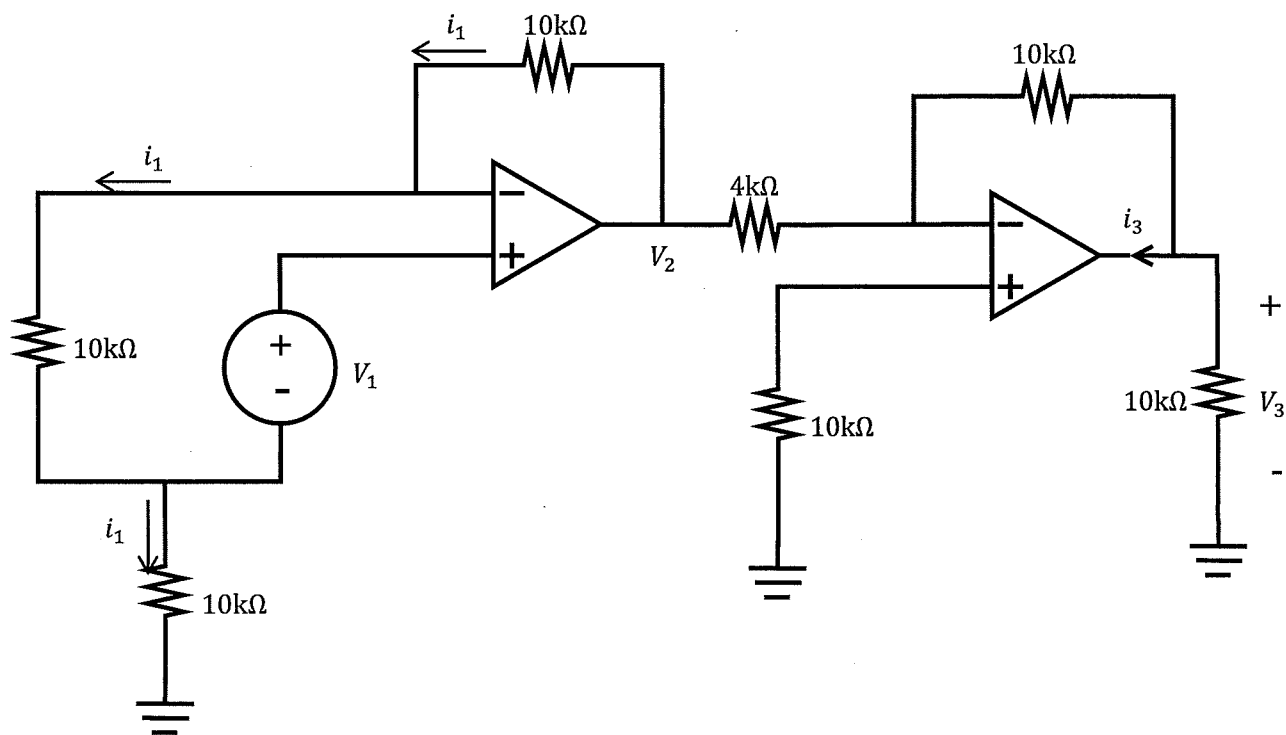- a) Bepaal die versterkingsfaktor V_2/V_1 .
 b) Bepaal i_3 as $V_2 = 2V$.



$$\begin{aligned}
 a) \quad V^+ &= i_1 \times 10k + V_1 \\
 V^- &= i_1 \times 10k + i_1 \times 10k = V^+ \\
 &\Rightarrow V_1 = i_1 \times 10k \\
 V_2 &= 3 \times i_1 \times 10k = 3V_1 \\
 &\Rightarrow \underline{V_2/V_1 = 3} \checkmark \checkmark
 \end{aligned}$$

$$\begin{aligned}
 b) \quad V_3 &= -2 \times \frac{10}{4} = -5V \\
 \underline{\text{KCL:}} \quad i_3 + \frac{(-5)}{10k} + \frac{(-5)}{10k} &= 0 \\
 &\Rightarrow \underline{i_3 = 1mA} \checkmark \checkmark
 \end{aligned}$$