

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Department of Electrical, Electronic and
Computer Engineering

Semestertoets 3

Kopiereg voorbehou

Semester Test 3

Copyright reserved

Module EBN122

Elektrisiteit en Elektronika

November 2016

Module EBN122

Electricity and Electronics

November 2016



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Exam information:

Eksamensinligting:

Maximum marks:	45	Full marks:	46
Maksimum punte:		Volpunte:	
Duration of paper:	90 minutes	Open / closed book:	Closed
Duur van vraestel:	90 minute	Oopboek / toeboek:	Toe
Total number of pages (including this page):	13		
Totale aantal bladsye (hierdie blad ingesluit):			

IMPORTANT - BELANGRIK

- The examination regulations of the University of Pretoria apply.*
Die eksamenregulasies van die Universiteit van Pretoria geld.
- All questions must be answered on the ANSWER SHEET.*
Alle vrae moet op die ANTWOORDBLAD beantwoord word.
- Students may do their own rough calculations on the question paper – the question paper will not be taken in.*
Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
- Answers must include units!*
Antwoorde moet eenhede insluit!
- Final answers must be written as real numbers, and not as fractions.*
Finale antwoorde moet as reële getalle geskryf word, en nie as breuke nie.

Dosent(e):
Lecturer(s):

1. D le Roux
2. R dos Santos
3. J Joubert

VRAAG/QUESTION 1 [4]

Given: $V_3 = 8 \text{ V}$ and $V_2 = 6 \text{ V}$.


a) Calculate V_1 .

b) Find the value of α for which $V_0 = -16 \text{ V}$.

Gegee: $V_3 = 8 \text{ V}$ en $V_2 = 6 \text{ V}$.

a) Bereken V_1 .

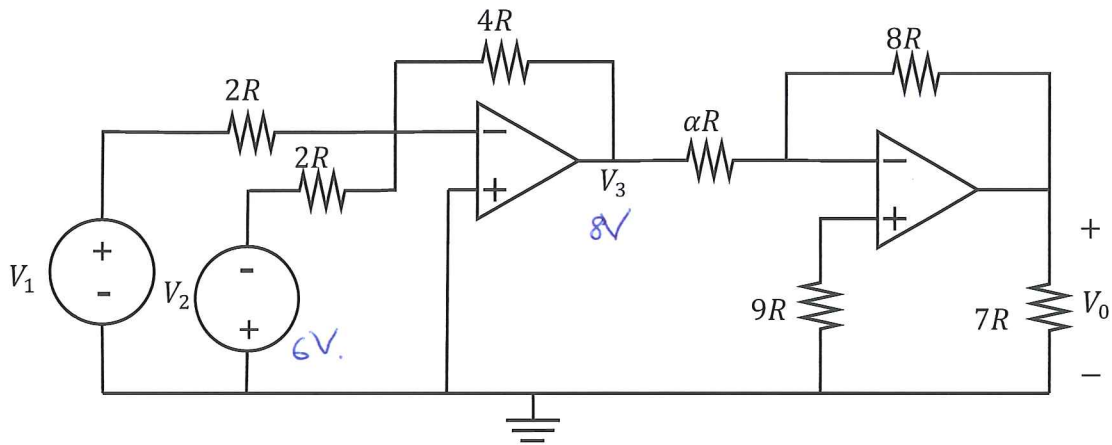b) Vind die waarde vir α sodat $V_0 = -16 \text{ V}$.



$$a) \quad V_3 = -4R \left(\frac{V_1}{2R} + \frac{(-V_2)}{2R} \right)$$

$$-8 = 2V_1 - 2V_2$$

$$-8 = 2V_1 - 2(6) \Rightarrow V_1 = +2 \text{ V} \quad \checkmark$$

$$b) \quad V_0 = -\frac{8R}{\alpha R} V_3$$

$$16 = \frac{8}{\alpha} (8)$$

$$\alpha = \frac{8}{16} (8)$$

$$\alpha = 4 \quad \checkmark$$

VRAAG/QUESTION 2 [10]

Question 2.1 [2]

The voltage across a 2 F capacitor is given as $v(t) = 8 - 3e^{-5t}V$. The current through the capacitor at $t = 0$ is given as 30 A. Determine the current at $t = 2$ s.

$$\begin{aligned} i_c &= C \frac{dv}{dt} \\ &= 2 \frac{dv}{dt} (8 - 3e^{-5t}) \\ &= 2(0 + 15e^{-5t}) \end{aligned}$$

$$i_c(t) = 30e^{-5t}$$

$$i(2) = 30e^{-10} = 1.36 \text{ mA} \checkmark$$

Vraag 2.1 [2]


Die spanning oor 'n 2 F kapasitor is $v(t) = 8 - 3e^{-5t}V$. Die stroom deur die kapasitor by $t = 0$ s is 30 A. Bepaal die stroom by $t = 2$ s.

Question 2.2 [2]

The graph below shows the voltage across a 10 H inductor. Assuming the initial current through the inductor is 4 A, what is the current between 0 and 6 seconds?

Vraag 2.2 [2]

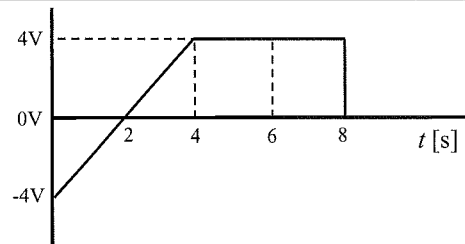
Onderstaande grafiek dui die spanning oor 'n 10 H induktor aan. Indien die aanvanklike stroom deur die induktor 4 A is, wat is die stroom tussen 0 en 6 sekondes?




$$\begin{aligned} i_L(t) &= \frac{1}{L} \int_{t_0}^t v(t) dt + i(0) \\ &= \frac{1}{10} \int_0^6 v(t) dt + 4 \\ &= \frac{1}{10} \int_0^4 v(t) dt + \frac{1}{10} \int_4^6 v(t) dt + 4 \\ &= 0 + \frac{1}{10} (4 \times 2) + 4 \\ &= 0.8 + 4 \\ &= \underline{4.8 \text{ A}} \checkmark \end{aligned}$$

Question 2.3 [2]
Calculate C_{eq} .


Vraag 2.3 [2]
Bepaal C_{eq} .

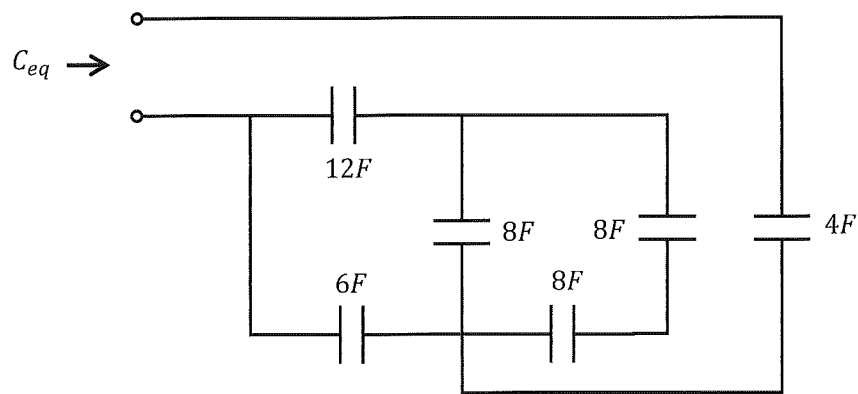

$$8//8 = 4F$$

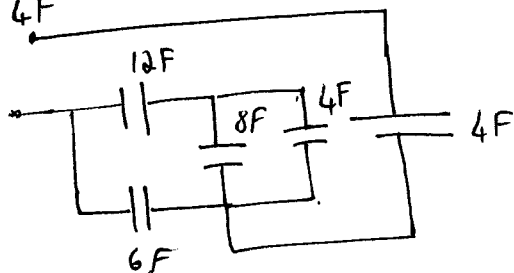

$$(8+4)//12 = 6F$$

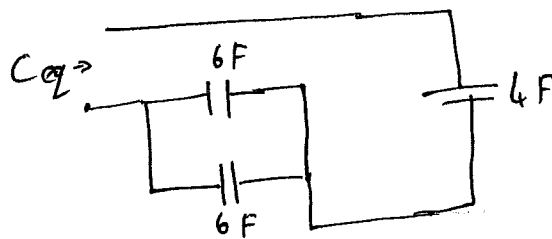

$$C_{eq} = (6+6)//4$$



$$= \frac{12 \times 4}{12+4} = 3F \checkmark$$

Question 2.4 [4]

Calculate the energy stored by the capacitor (w_C) and inductor (w_L). Assume direct current conditions.

Vraag 2.4 [4]

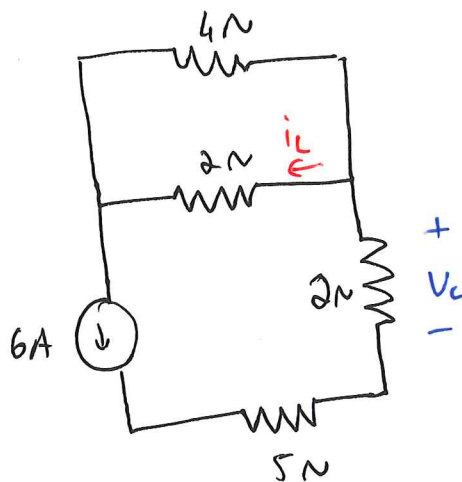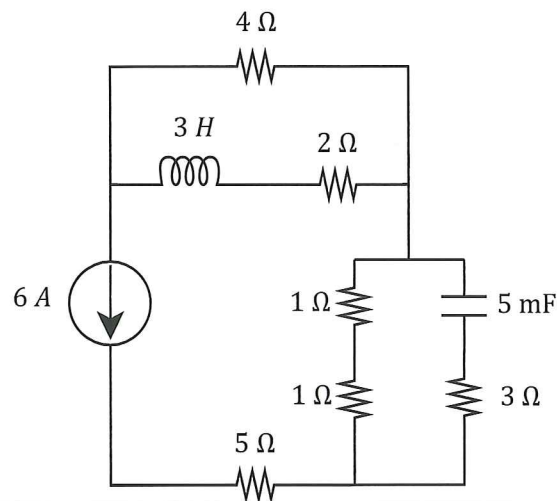Bepaal die energie gestoor in die kapasitor (w_C) en die inductor (w_L). Aanvaar gelykstroom toestande.



$$V_C = 6 \times 2 = 12V$$

$$\begin{aligned} w_C &= \frac{1}{2} C V_C^2 \\ &= \frac{1}{2} (5 \times 10^{-3}) (12)^2 \\ &= 0.36J \\ &= 360mJ \checkmark \end{aligned}$$

$$\begin{aligned} i_L &= \frac{4 \times 6}{2+4} \text{ (current division)} \\ &= 4A \end{aligned}$$

$$\begin{aligned} w_L &= \frac{1}{2} L i_L^2 \\ &= \frac{1}{2} (3) (4)^2 \\ &= 24J \checkmark \end{aligned}$$

VRAAG/QUESTION 3 [16]

Vraag 3.1 [6]


- a) Skryf $v(t)$ as 'n fasor in **reghoekige vorm**:
 $v(t) = 10\cos(\omega t - 90^\circ) - 30\sin(\omega t + 45^\circ)$ V
- b) Bepaal die las-impedansie as
 $v_L(t) = 300\cos(5000\pi t)$ V, en
 $i_L(t) = 6\sin(5000\pi t)$ A.
 Aanvaar dat die stroom by die + van die verwysingspanning oor die las invloei. Skryf die antwoord in **polêre vorm**.
- c) 'n 20Ω weerstand en 'n $2\mu\text{F}$ kapasitor is in parallel geskakel. 'n Spanningsbron $v(t) = 500\cos(5000t + 20^\circ)$ V word oor die parallel-kombinasie aangelê. Bereken die stroom $i_C(t)$ wat deur die kapasitor vloei. Aanvaar dat die stroom vanaf die bron by die + van die verwysingspanning gedefinieer oor die las-impedansie invloei.

Question 3.1 [6]

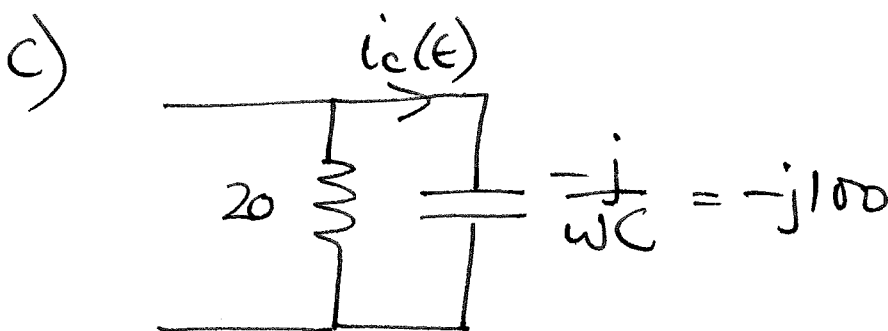- a) Write $v(t)$ as a phasor in **rectangular form**:
 $v(t) = 10\cos(\omega t - 90^\circ) - 30\sin(\omega t + 45^\circ)$ V
- b) Determine the load impedance if
 $v_L(t) = 300\cos(5000\pi t)$ V, and
 $i_L(t) = 6\sin(5000\pi t)$ A.
 Assume the current is flowing into the + of the reference voltage across the load. Write the answer in **polar form**.
- c) A 20Ω resistor and a $2\mu\text{F}$ capacitor are connected in parallel. A voltage source $v(t) = 500\cos(5000t + 20^\circ)$ V is connected across the parallel combination. Determine the current $i_C(t)$ that flows through the capacitor. Assume the current is flowing from the source into the + of the reference voltage defined across the load impedance.

$$\begin{aligned} \text{a) } \bar{V} &= 10 \angle -90^\circ - 30 \angle 45^\circ - 90^\circ \\ &= -j10 - (21.21 - j21.21) \\ &= \underline{-21.21 + j11.21} \quad \checkmark \end{aligned}$$

$$\text{b) } \bar{Z}_L = \frac{300}{6 \angle -90^\circ} \Omega = \underline{50 \angle 90^\circ \Omega} \quad \checkmark$$



$$\bar{I}_C = \frac{500 \angle 20^\circ}{100 \angle -90^\circ} = \underline{5 \angle 110^\circ \text{ A}}$$

$$\underline{i_C(t) = 5 \cos(5000t + 110^\circ) \text{ A}} \quad \checkmark$$

Vraag 3.2 [4]

a) Vereenvoudig en skryf die antwoord in **reghoekige vorm**:

$$\bar{I}_1 = \frac{(3 + j4) + 11\angle 90^\circ}{(2\angle 45^\circ)^2 + (3 - j4)}$$

b) Bepaal $\bar{V}_2$ in **polêre vorm**:

$$\begin{bmatrix} 2 + j4 & -j2 \\ -j2 & 2 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2\angle 90^\circ \end{bmatrix}$$

Question 3.2 [4]

a) Simplify and write the answer in **rectangular form**:

$$\bar{I}_1 = \frac{(3 + j4) + 11\angle 90^\circ}{(2\angle 45^\circ)^2 + (3 - j4)}$$

b) Determine $\bar{V}_2$ in **polar form**:

$$\begin{bmatrix} 2 + j4 & -j2 \\ -j2 & 2 \end{bmatrix} \begin{bmatrix} \bar{V}_1 \\ \bar{V}_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2\angle 90^\circ \end{bmatrix}$$

$$a) \frac{3 + j4 + j11}{j4 + 3 - j4} = \frac{3 + j15}{3}$$

$$\bar{I}_1 = 1 + j5 \checkmark \checkmark$$

$$b) \Delta = \begin{vmatrix} 2 + j4 & -j2 \\ -j2 & 2 \end{vmatrix} = 2(2 + j4) - (-j2)(-j2)$$

$$= 8 + j8$$

$$\Delta_2 = \begin{vmatrix} 2 + j4 & 0 \\ -j2 & j2 \end{vmatrix} = j2(2 + j4) = -8 + j4$$

$$\bar{V}_2 = \frac{-8 + j4}{8 + j8} = \frac{8.94 \angle 153.4^\circ}{11.31 \angle 45^\circ}$$


$$= 0.79 \angle 108.4^\circ \checkmark \checkmark \checkmark$$

Vraag 3.3 [2]

Bepaal die totale impedansie $\bar{Z}_{ab}$ tussen terminale a en b . Skryf die antwoord in **reghoekige vorm**.

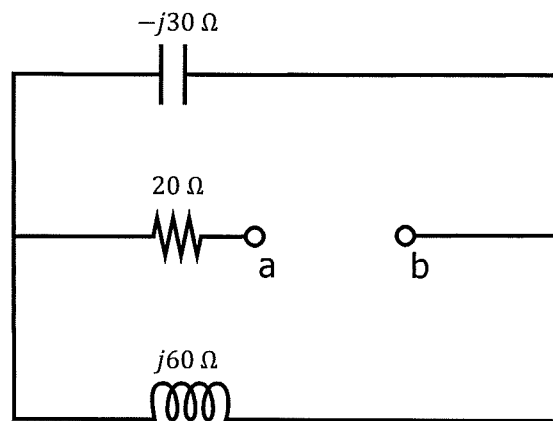Question 3.3 [2]

Determine the total impedance $\bar{Z}_{ab}$ between terminals a and b . Write the answer in **rectangular form**.



$$\bar{Z}_{ab} = 20 + j60 // (-j30)$$

$$= 20 + \frac{(j60)(-j30)}{j30}$$


$$= 20 + \frac{1800}{j30} = 20 - j60\ \Omega \checkmark \checkmark$$

Vraag 3.4 [4]

- a) Bepaal $\bar{I}_a$ as $\bar{I}_b = 1 \angle -90^\circ$ A. Skryf die antwoord in **reghoekige vorm**.
- b) Bepaal $\bar{I}_a$ as $\bar{V}_s = 2 \angle 60^\circ$ V. Skryf die antwoord in **polêre vorm**.

Question 3.4 [4]

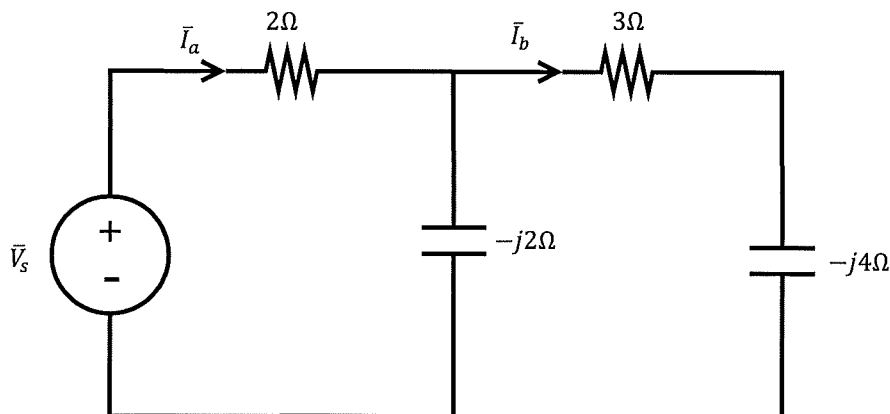- a) Determine $\bar{I}_a$ if $\bar{I}_b = 1 \angle -90^\circ$ A. Write the answer in **rectangular form**.
- b) Determine $\bar{I}_a$ if $\bar{V}_s = 2 \angle 60^\circ$ V. Write the answer in **polar form**.



$$a) \bar{I}_a = \bar{I}_b + \frac{\bar{I}_b(3-j4)}{-j2}$$

$$= 1 \angle -90^\circ + \frac{1 \angle -90^\circ \cdot 5 \angle -53^\circ}{2 \angle -90^\circ}$$

$$= 1 \angle -90^\circ + 2.5 \angle -53^\circ$$

$$= -j + 1.5 - j2 = \underline{1.5 - j3} \text{ A} \checkmark \checkmark$$

$$b) \bar{Z}_T = 2 + (3-j4) \parallel (-j2)$$

$$= 2 + \frac{-8-j6}{3-j6}$$

$$= 2.27 - j1.47 = 2.7 \angle -32.9^\circ$$

$$\bar{I}_a = \frac{2 \angle 60^\circ}{2.7 \angle -32.9^\circ} = \underline{0.74 \angle 92.9^\circ} \text{ A} \checkmark \checkmark$$

VRAAG/QUESTION 4 [16]

Question 4.1 [4]


Use nodal analysis to set up two equations of the following form:

$$\begin{aligned}(a_1 + ja_2)V_1 + (b_1 + jb_2)V_3 &= -24 \\ cV_1 + dV_3 &= 7\end{aligned}$$

Vraag 4.1 [4]

Gebruik node analyse om twee vergelykings van die volgende vorm op te stel:
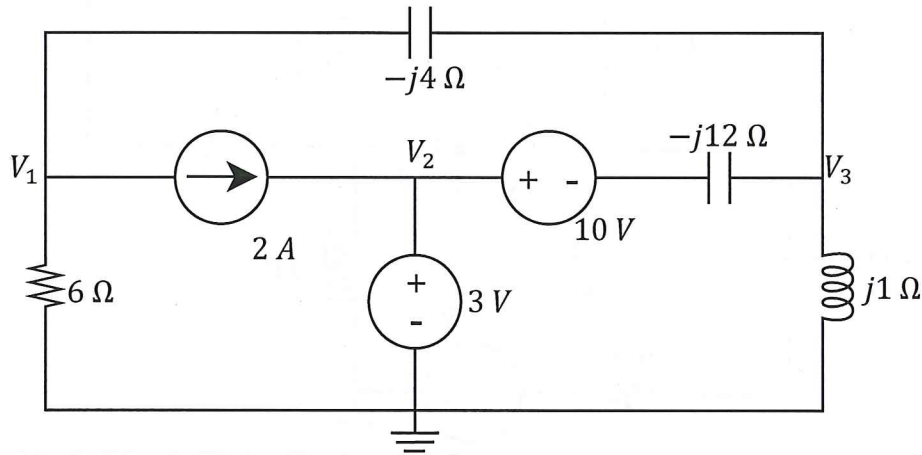
$$\begin{aligned}(a_1 + ja_2)V_1 + (b_1 + jb_2)V_3 &= -24 \\ cV_1 + dV_3 &= 7\end{aligned}$$



* $V_2 = 3V$

Node 1: $2 + \frac{V_1}{6} + \frac{V_1 - V_3}{-j4} = 0.$

$$2V_1 + \frac{3V_1}{j} - \frac{3V_3}{-j} = -24$$

$$2V_1 + 3jV_1 - 3jV_3 = -24$$

$$(2+3j)V_1 - 3jV_3 = -24 \quad \rightarrow$$

Node 3:

$$\frac{V_3 - V_1}{-j4} + \frac{V_3}{j1} + \frac{V_3 + 10 - 3}{-j12} = 0$$

$$\frac{jV_3 - jV_1}{4} - jV_3 + \frac{jV_3 + 7j}{12} = 0$$

$$3jV_3 - 3jV_1 - 12jV_3 + jV_3 + 7j = 0$$

$$-3V_1 - 8V_3 = -7$$

$$3V_1 + 8V_3 = 7 \quad \rightarrow$$

Question 4.2 [4]

Use mesh analysis to set up two equations of the following form:

$$(e_1 + je_2)\bar{I}_1 + (f_1 + jf_2)\bar{I}_2 = -3$$


$$g\bar{I}_1 + h\bar{I}_2 = 4$$

Vraag 4.2 [4]

Gebruik lusanalyse om twee vergelykings van die volgende vorm op te stel:

$$(e_1 + je_2)\bar{I}_2 + (f_1 + jf_2)\bar{I}_3 = -3$$

$$g\bar{I}_1 + h\bar{I}_2 = 4$$

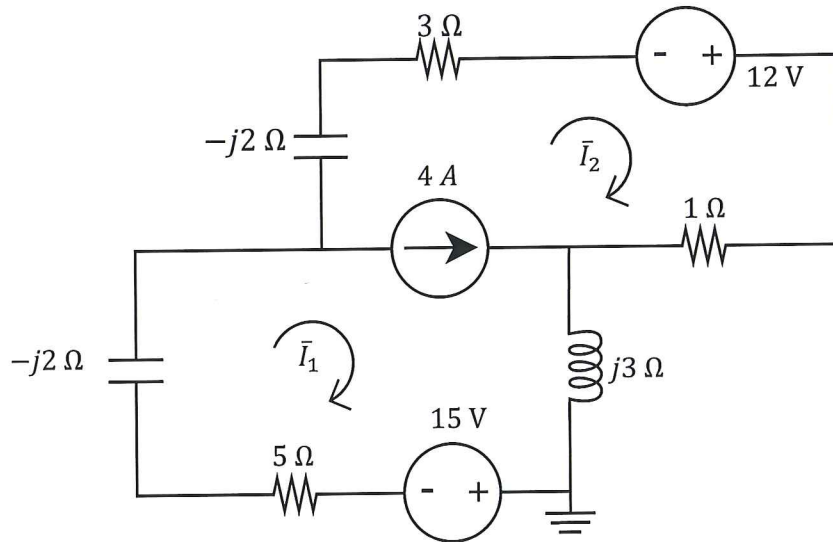

KCL * $\bar{I}_2 + 4 = \bar{I}_1 \Rightarrow 4 = \underline{\underline{\bar{I}_1 - \bar{I}_2}}$ ✓✓

KVL * $(j3 - j2 + 5)\bar{I}_1 + (15 + (-j2 + 3 + 1))\bar{I}_2 - 12 = 0$

$$\underline{\underline{(5+j)\bar{I}_1}} + \underline{\underline{(4-j2)\bar{I}_2}} = -3$$

✓ ✓

Question 4.3 [4]

Find the Thevenin equivalent of the circuit with respect to terminals a - b .

a) $\bar{V}_{TH}$ in rectangular form


b) Z_{TH} in rectangular form

Vraag 4.3 [4]


Vind die Thevenin ekwivalent met verwysing tot terminale.

a) $\bar{V}_{TH}$ in reghoekige vorm

b) Z_{TH} in reghoekige vorm.

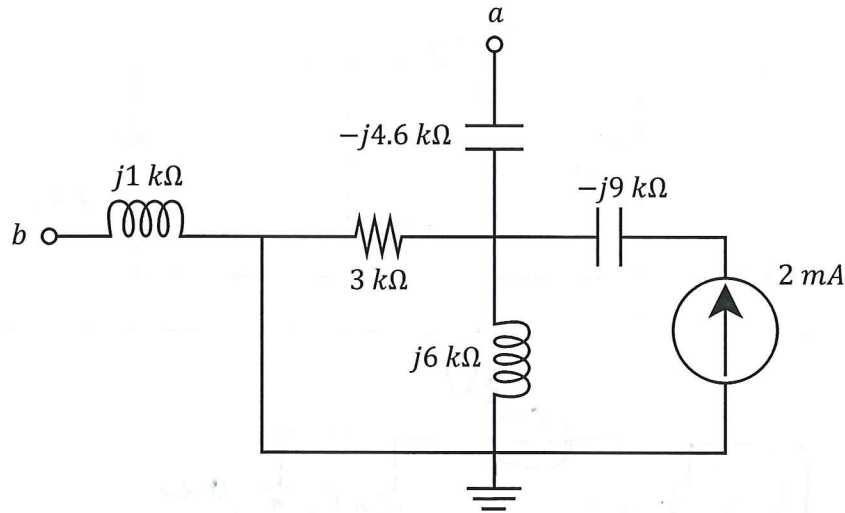


a) $\underline{V_{TH}} = V_{ab}$

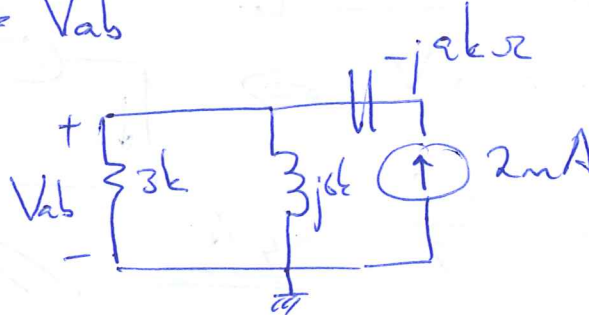

$$\frac{V_{ab}}{3k} + \frac{V_{ab}}{j6k} = 2m$$

$$j2V_{ab} + V_{ab} = j12$$
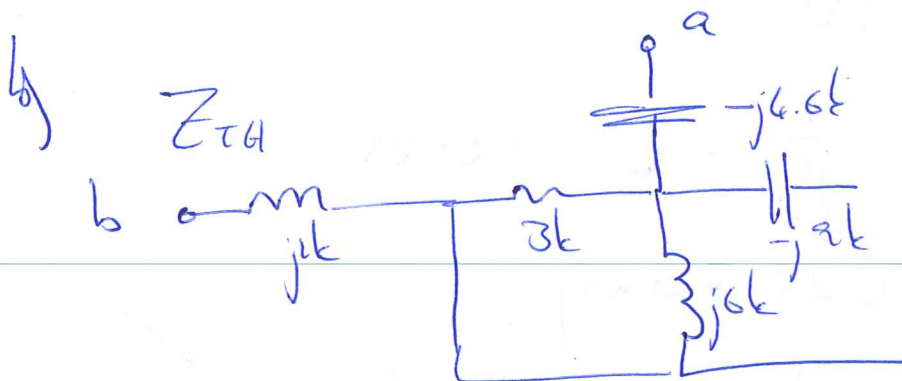
$$V_{ab} = V_{TH} = \frac{j12}{1+j2} = \underline{\underline{4.8 + 2.4j \text{ V}}}$$



$$Z_{TH} = (j1 + (-j4.6) + \frac{3 \times j6}{3 + j6}) k$$

$$= -j3.6 k + 2.4k + 1.2jk = \underline{\underline{(2.4 - j2.4) k\Omega}}$$

Question 4.4 [4]


Find the Norton equivalent of the circuit with respect to terminals a - b .

- a) $\bar{I}_N$ in rectangular form
b) Z_N in polar form


Vraag 4.4 [4]

Vind die Norton ekwivalent met verwysing tot terminale a - b .

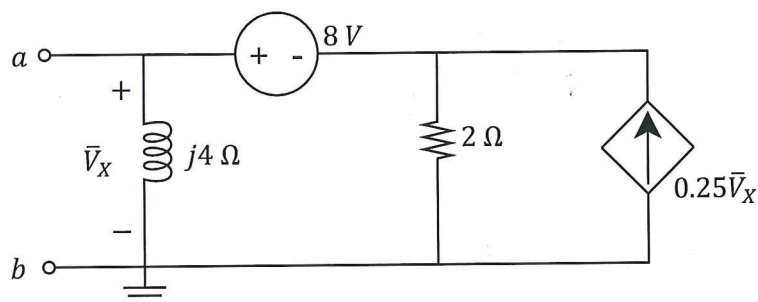
- a) $\bar{I}_N$ in reghoekige vorm
b) Z_N in polêre vorm.



$\bar{I}_N$

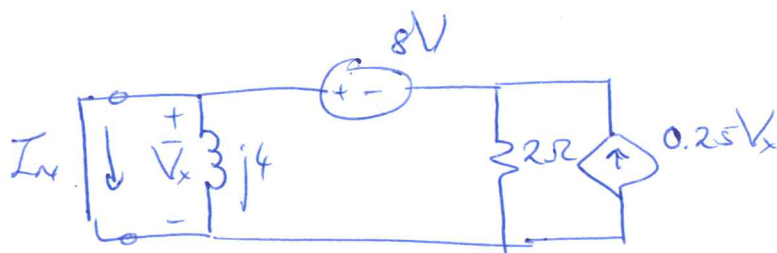


* $\bar{V}_x = 0 \text{ V} \Rightarrow$

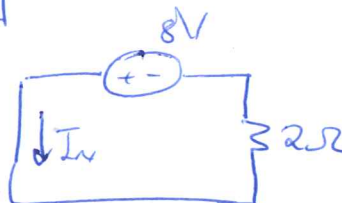

* $\bar{I}_N = \frac{+8}{2} = \underline{\underline{+4 \text{ A}}}$ ✓✓

Z_N

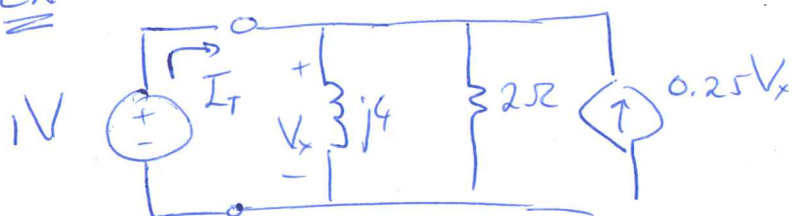

* $V_x = 1 \text{ V}$

* $I_T = \frac{1}{j4} + \frac{1}{2} - 0.25$
 $= 0.25 \angle -90^\circ + 0.25 \angle 0^\circ$

* $Z_N = \frac{1}{0.25 \angle -90^\circ + 0.25 \angle 0^\circ} = \underline{\underline{2.828 \angle +45^\circ \Omega}}$ ✓✓

EBN122 SEMESTER TEST/ TOETS 2 (NOV 2016)

ANSWER SHEET / ANTWOORDBLAD

Surname: Van:		Student number: Studentennummer:							
Initials: Voorletters:		Group: Groep:	ENGLISH (Eng 3-1)	ENGLISH (Eng 3-6)	AFR				

Q1+2	14	Q3	16	Q4	16	Tot:	46	/45
------	----	----	----	----	----	------	----	-----

VRAAG 1 – QUESTION 1 (4)

1	a) $V_1 = 2V \checkmark$	b) $\alpha = 4 \checkmark$
---	--------------------------	----------------------------

QUESTION 2 - VRAAG 2 (10)

2.1	$i_{C(2s)} = 1.36mA \checkmark$	
2.2	$i_{L(0 \text{ to } 6s)} = 4.8A \checkmark$	
2.3	$C_{eq} = 3F \checkmark$	
2.4	$w_C = 0.36J = 360mJ \checkmark$	$w_L = 24J \checkmark$

VRAAG 3 – QUESTION 3 (16)

3.1	a) $\bar{V} = -21.21 + j11.21V \checkmark$ (rectangular)	
	b) $\bar{Z}_L = 50 \angle 90^\circ \Omega \checkmark$ (polar)	
	c) $i_C(t) = 5 \cos(5000t + 110^\circ) A \checkmark$	
3.2	a) $\bar{I}_1 = 1 + j5A \checkmark$ (rectangular)	b) $\bar{V}_2 = 0.79 \angle 108.4^\circ V \checkmark$ (polar)
3.3	$\bar{Z}_{ab} = 20 - j60 \Omega \checkmark$ (rectangular)	
3.4	a) $\bar{I}_a = 1.5 - j3A \checkmark$ (rectangular)	b) $\bar{I}_a = 0.74 \angle 92.9^\circ A \checkmark$ (polar)

VRAAG 4 – QUESTION 4 (16)

4.1	$a_1 + ja_2 = 2 + j3 \checkmark$	$b_1 + jb_2 = 0 + j(-3) \checkmark$
	$c = 3 \checkmark$	$d = 8 \checkmark$
4.2	$e_1 + je_2 = 5 + j \checkmark$	$f_1 + jf_2 = 4 + j(-2) \checkmark$
	$g = 1 \checkmark$	$h = -1 \checkmark$
4.3	$\bar{V}_{TH} = 4.8 + j2.4V \checkmark$ (rectangular)	$Z_{TH} = (2.4 - j2.4)k\Omega \checkmark$ (rectangular)
4.4	$\bar{I}_N = 4A \checkmark$ (rectangular)	$Z_N = 2.828 \angle 45^\circ \Omega \checkmark$ (polar)