

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Department of Electrical, Electronic and
Computer Engineering

Semestertoets 3

VRAESTEL

Kopiereg voorbehou

Semester Test 3
QUESTION PAPER

Copyright reserved

Module EBN122

Elektrisiteit en Elektronika

Oktober 2017

Module EBN122

Electricity and Electronics

October 2017



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Memo.

Eksamensinligting:

Exam information:

Maksimum punte: <i>Maximum marks:</i>	46	Volpunte: <i>Full marks:</i>	45
Duur van vraestel: <i>Duration of paper:</i>	90 min + 10 min to complete OCR form <i>90 min + 10 min om OKH vorm te voltooi</i>	Oopboek / toeboek: <i>Open / closed book:</i>	Toe <i>Closed</i>
Totale aantal bladsye (hierdie blad ingesluit): <i>Total number of pages (including this page):</i>		19 + OCR	




BELANGRIK- IMPORTANT

- Die eksamenregulasies van die Universiteit van Pretoria geld.
The examination regulations of the University of Pretoria apply.
- Alle vrae moet op die ANTWOORDBLAD en op die Optiese Karakter Herkenning (OKH) vorm ingevul word.**
All questions must be answered on the ANSWER SHEET and on the Optical Character Recognition (OCR) form.
- Neem noukeurig kennis van die instruksies op die OKH vorm.
Take careful consideration of the instructions on the OCR form.

Dosent(e): <i>Lecturer(s):</i>	1. D le Roux
	2. D Ramotsoela
	3. X Ye

SECTION / AFDELING 1 [10]

Question 1 [2]		Vraag 1 [2]	
01	Calculate C_{ab} .	01	Bereken C_{ab} .

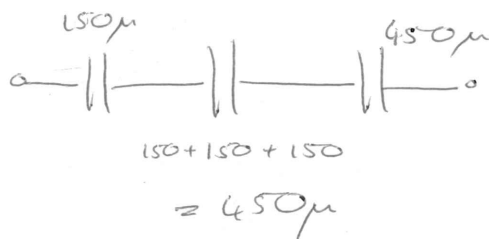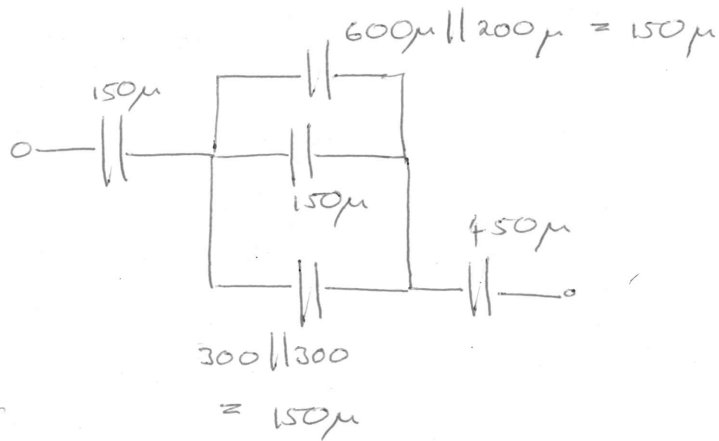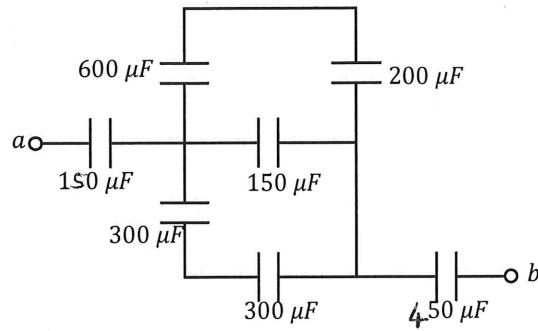

$\hookrightarrow C_{ab} = 150\mu \parallel 450\mu \parallel 450\mu$
 $= 90\mu F. \checkmark$

Question 2 & 3 [4]		Vraag 2 & 3 [4]	
For the circuit below, calculate the voltage across the capacitor and the voltage across the inductor when $t = 0.1$ s. Assume $v_L(0) = -20$ V, and $v_C(0) = 0$ V.		Vir onderstaande kringbaan, bereken die spanning oor die kapasitor en die spanning oor die induktor vir $t = 0.1$ s. Aanvaar $v_L(0) = -20$ V, en $v_C(0) = 0$ V.	
02	$v_C(0.1\text{s})$	02	$v_C(0.1\text{s})$
03	$v_L(0.1\text{s})$	03	$v_L(0.1\text{s})$

The circuit diagram shows a current source $i_s(t) = 10e^{-t} \text{ A}$ connected in series with a capacitor of 100 mF and an inductor of 2 H . The voltage across the capacitor is labeled $v_C(t)$ with the positive terminal at the top. The voltage across the inductor is labeled $v_L(t)$ with the positive terminal at the top.



$$\begin{aligned}
 * \quad v_L &= L \frac{di}{dt} \\
 &= 2 \frac{d}{dt} (10e^{-t}) \\
 &= -20e^{-t}
 \end{aligned}$$

$$\begin{aligned}
 v_L(0.1) &= -20e^{-0.1} \\
 &= \underline{-18.097 \text{ V}}
 \end{aligned}$$

$$\begin{aligned}
 * \quad v_C &= \frac{1}{C} \int_0^t i \, dt + v_C(0) \\
 &= \frac{1}{0.1} \int_0^t 10e^{-t} \, dt \\
 &= 100 \int_0^t e^{-t} \, dt \\
 &= 100 \left[-e^{-t} \right]_0^t \\
 &= 100 (1 - e^{-t})
 \end{aligned}$$

$$v_C(0.1) = \underline{9.516 \text{ V}}$$

Question 4 & 5 [4]		Vraag 4 & 5 [4]	
Assume steady-state conditions (Direct Current) for the circuit below. What is the energy stored by the capacitor w_C and inductor w_L ?		Aanvaar gestadigde toestand (Gelykstroom) vir onderstaande kringbaan. Wat is die energie gestoor deur die kapasitor w_C en induktor w_L ?	
04	w_C	04	w_C
05	w_L	05	w_L

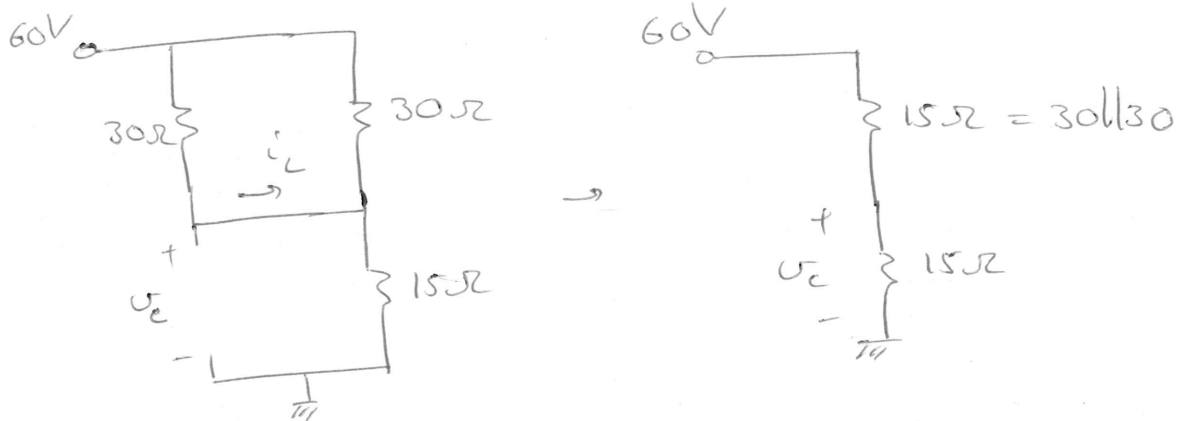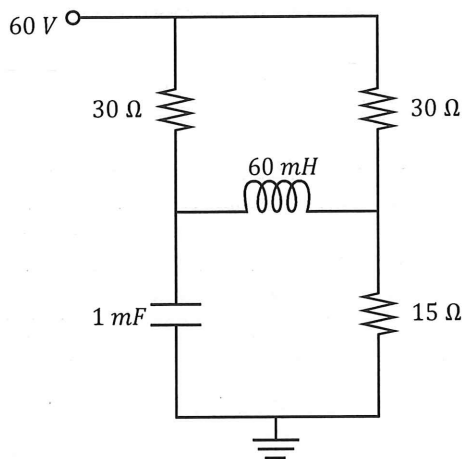

* The 60V splits equally over the two 15Ω resistors.

$$\therefore V_C = 30V$$

$$w_C = \frac{1}{2}(1m)(30)^2$$

$$= \underline{450mJ}$$


$$i_L = \frac{30V}{30\Omega} = 1A$$

$$w_L = \frac{1}{2}(60m)(1)^2$$

$$= \underline{30mJ}$$

SECTION / AFDELING 2 [18]

Questions 6 & 7 [4]		Vraag 6 & 7 [4]	
The following sinusoid is given: $v_1 = 16 \cos(\omega t - 110^\circ) \text{ V}$ It is known that:		Die volgende sinusied word gegee: $v_1 = 16 \cos(\omega t - 110^\circ) \text{ V}$ Dit is bekend dat:	
- v_1 leads v_2 by 50°. - v_1 lags v_3 by 100°.		- v_1 loop voor v_2 met 50°. - v_1 loop agter v_3 met 100°.	
06	Choose the correct statement: 1. v_2 leads v_3 2. v_3 leads v_2 (Write 1 if statement 1 is correct, and 2 if statement 2 is correct.)	06	Kies die korrekte stelling: 1. v_2 loop voor v_3 2. v_3 loop voor v_2 (Skryf 1 indien stelling 1 korrek is, en 2 indien stelling 2 korrek is.)
07	If $v_2 = 6 \cos(\omega t + \theta) \text{ V}$, what is θ ? (Give the angle in the range of -180° to 180° .)	07	Indien $v_2 = 6 \cos(\omega t + \theta) \text{ V}$, wat is θ ? (Gee die hoek in die bereik van -180° tot 180° .)

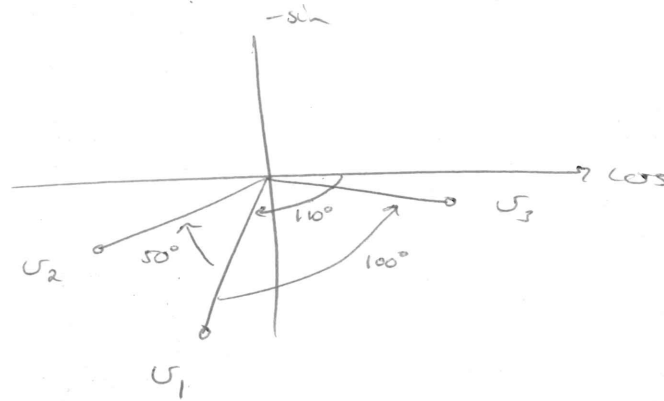


$\therefore v_3$ leads v_2 .

$$\theta = -160^\circ$$

Questions 8 & 9 [4]		Vraag 8 & 9 [4]	
08	Solve for z: $z = \frac{\sqrt{-j4}}{(1.732 - j)^*}$ (Write the final answer in polar form .)	08	Los op vir z: $z = \frac{\sqrt{-j4}}{(1.732 - j)^*}$ (Skryf die finale antwoord in polêre vorm .)
09	The following sinusoids are given: $v_1 = 6 \sin(\omega t - 20.05^\circ) \text{ V}$ $v_2 = 5.46 \cos(\omega t + 40.07^\circ) \text{ V}$ Determine the phasor value of $\bar{V}_T = \bar{V}_1 + \bar{V}_2$. Give the answer in polar form .	09	Die volgende sinusiede word gegee: $v_1 = 6 \sin(\omega t - 20.05^\circ) \text{ V}$ $v_2 = 5.46 \cos(\omega t + 40.07^\circ) \text{ V}$ Bepaal die fasor waarde van $\bar{V}_T = \bar{V}_1 + \bar{V}_2$. Gee die antwoord in polêre vorm .

$$\begin{aligned}
 * \quad z &= \frac{\sqrt{4 \angle -90^\circ}}{1.732 + j} \\
 &= \frac{2 \angle -45^\circ}{2 \angle 30^\circ}
 \end{aligned}$$
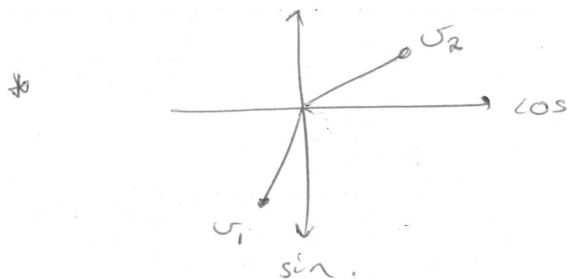
$$\begin{aligned}
 &= \frac{2 \angle -45^\circ}{\sqrt{1.732^2 + 1^2} \angle \tan^{-1}\left(\frac{1}{1.732}\right)} \\
 &= 1 \angle -75^\circ \quad \checkmark
 \end{aligned}$$



$$v_1 = 6 \cos(\omega t - 20.05^\circ - 90^\circ)$$


$$\therefore V_1 = 6 \angle -110.05^\circ$$

$$v_2 = 5.46 \cos(\omega t + 40.07^\circ)$$

$$\therefore V_2 = 5.46 \angle +40.07^\circ$$


$$\begin{aligned}
 V_T &= V_1 + V_2 = 3 \angle -45^\circ \text{ V} \\
 &\quad \checkmark
 \end{aligned}$$

Question 10 [2]		Vraag 10 [2]	
The following three elements are all connected in series: a $3 \cos(2000t - 15^\circ) \text{ V}$ voltage source, a $1.732 \text{ k}\Omega$ resistor, and a 500 mH inductor. What is the total current through the circuit? (Give the answer in rectangular form .)		Die volgende drie elemente word in series gekoppel: 'n $3 \cos(2000t - 15^\circ) \text{ V}$ spanningsbron, 'n $1.732 \text{ k}\Omega$ resistor, en 'n 500 mH induktor. Wat is die totale stroom deur die kringbaan? (Skryf die antwoord in reghoekige vorm .)	
10	$\bar{I}_T$ polar	10	$\bar{I}_T$ polar

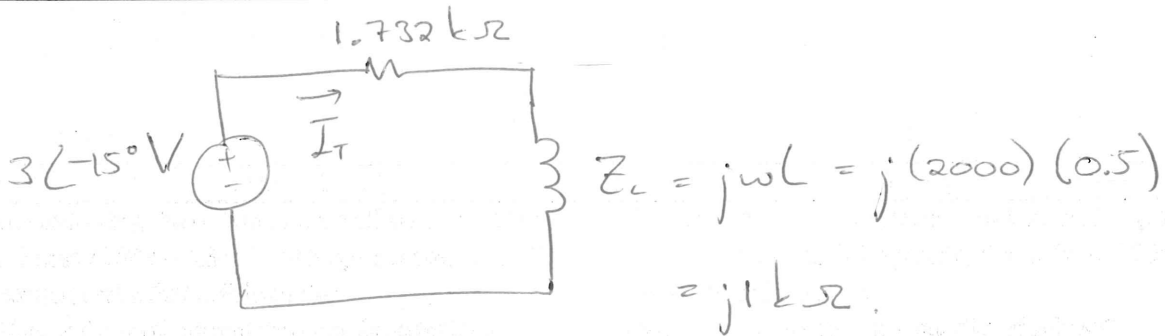


$$\begin{aligned}
 \bar{I}_T &= \frac{3 \angle -15^\circ}{1.732 \text{ k} + j1 \text{ k}} = \frac{3 \angle -15^\circ}{(2 \angle 30^\circ) \text{ k}} \\
 &= \underline{1.5 \angle -45^\circ \text{ mA}} \quad \checkmark
 \end{aligned}$$

Question 11 & 12 [4]		Vraag 11 & 12 [4]	
11	If $\bar{V}_S = 0\text{ V}$ and $\bar{I}_S = 8\angle 90^\circ\text{ A}$, determine $\bar{I}_0$. (Write the answer in rectangular form .)	11	Indien $\bar{V}_S = 0\text{ V}$ en $\bar{I}_S = 8\angle 90^\circ\text{ A}$, bepaal $\bar{I}_0$. (Skryf die antwoord in reghoekige vorm .)
12	If $\bar{V}_S = 8\angle 90^\circ\text{ V}$ and $\bar{I}_S = 0\text{ A}$, determine $\bar{V}_0$. (Write the answer in polar form .)	12	If $\bar{V}_S = 8\angle 90^\circ\text{ V}$ en $\bar{I}_S = 0\text{ A}$, bepaal $\bar{V}_0$. (Skryf die antwoord in polêre vorm .)

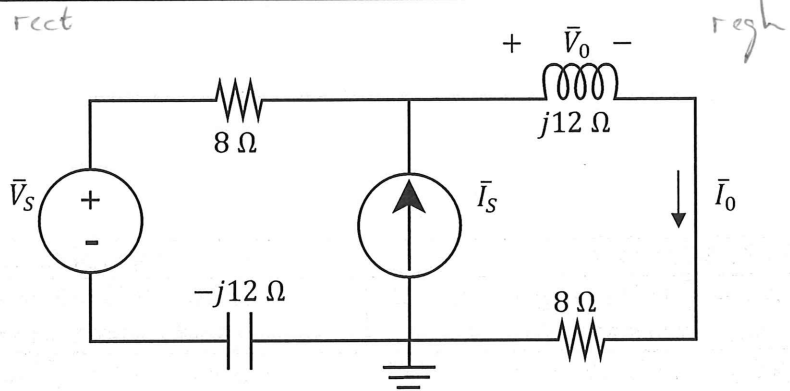

11

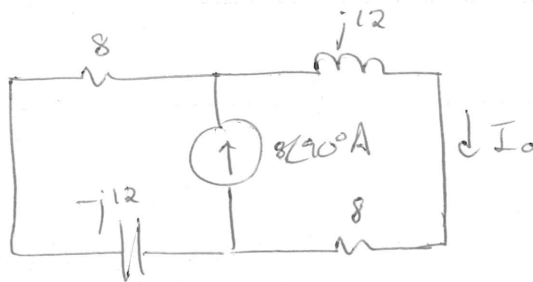


* I-division:

$$\begin{aligned} \bar{I}_0 &= \frac{8\angle 90^\circ (8 - j12)}{(8 - j12) + (8 + j12)} \\ &= \frac{8j(8 - j12)}{16} \end{aligned}$$

$$= \underline{\underline{8 + j4\text{ A}}}$$


12

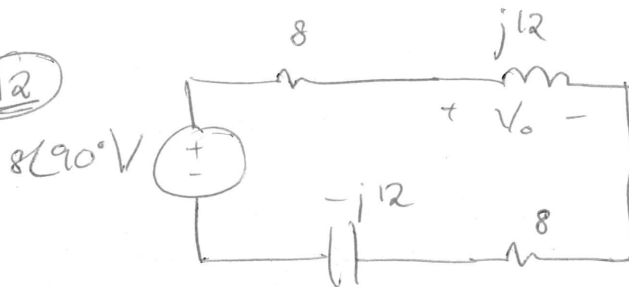

* V-division:

$$\begin{aligned} \bar{V}_0 &= \frac{8\angle 90^\circ \times j12}{8 + 8 + j12 - j12} \\ &= \frac{8j \times j12}{16} \end{aligned}$$

$$= \underline{\underline{-6\text{ V}}}$$

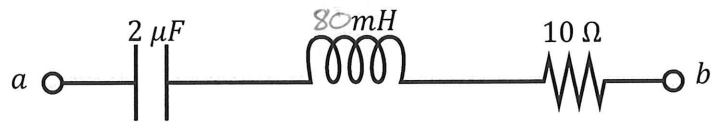Question 13 [2]		Vraag 13 [2]	
13	For wat value of ω will Z_{ab} only be real? (I.e. $Z_{ab} = R + j0 \Omega$)	13	Vir watter waarde van ω sal Z_{ab} slegs reël wees? (M.a.w. $Z_{ab} = R + j0 \Omega$)
			

$$Z_{ab} = Z_C + Z_L + Z_R$$

$$= \frac{-j}{\omega C} + j\omega L + R$$

But Z_{ab} must only be equal to R


$$\therefore \frac{-j}{\omega C} + j\omega L = 0$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{L \times C}$$

$$\omega = \frac{1}{\sqrt{80\text{m} \times 2\mu\text{F}}}$$

$$= 2.5 \text{ krad/s.}$$

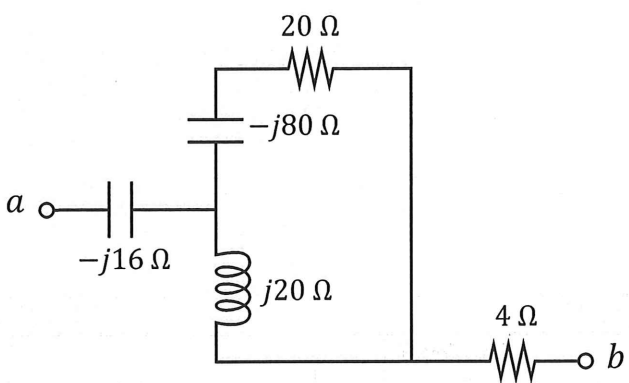Question 14 [2]		Vraag 14 [2]	
14	Calculate Z_{ab} . (Give the answer in rectangular form .)	14	Bereken Z_{ab} . (Skryf die antwoord in reghoekige vorm .)
			

$$Z_{ab} = -j16 + (j20) \parallel (-j80 + 20) + 4$$


$$= 4 - j16 + \frac{(j20)(20 - j80)}{20 - j60}$$

$$= 4 - j16 + 2 + 26j$$

$$= \underline{6 + 10j \, \Omega} \quad \checkmark$$

SECTION / AFDELING 3 [18]

Question 15-18 [4]				Vraag 15-18 [4]			
Use nodal analysis to set up two equations of the following form $a\bar{V}_1 + b\bar{V}_2 = j12$ $c\bar{V}_1 + d\bar{V}_2 = -180$ Give the coefficients in rectangular form .				Gebruik node analise om twee vergelykings van die volgende vorm op te stel: $a\bar{V}_1 + b\bar{V}_2 = j12$ $c\bar{V}_1 + d\bar{V}_2 = -180$ Gee die koëffisiënte in reghoekige vorm .			
15	a	16	b	15	a	16	b
17	c	18	d	17	c	18	d

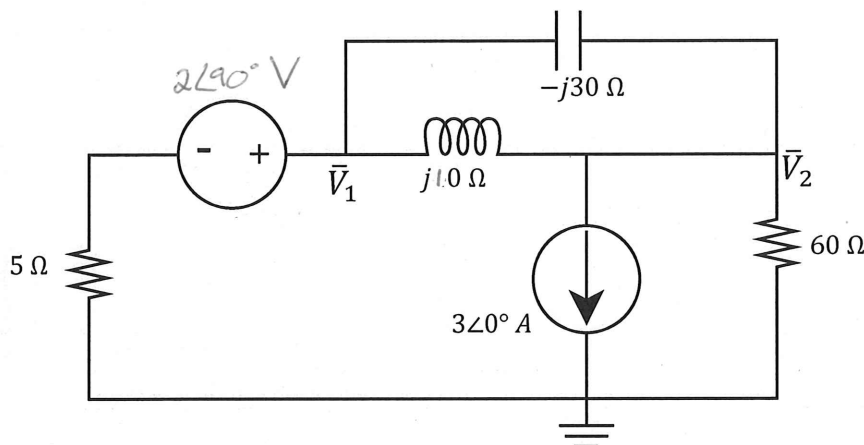

$$\textcircled{1} \quad \frac{V_1 - 2\angle 90^\circ}{5} + \frac{V_1 - V_2}{j10} + \frac{V_1 - V_2}{-j30} = 0$$

$$(\times 30) \quad 6V_1 - j12 - j3V_1 + j3V_2 + jV_1 - jV_2 = 0$$

$$V_1(6 - j2) + V_2(j2) = j12$$


$$\textcircled{2} \quad 3 + \frac{V_2}{60} + \frac{V_2 - V_1}{j10} + \frac{V_2 - V_1}{-j30} = 0$$

$$(\times 60) \quad V_2 - j6V_2 + j6V_1 + j2V_2 - j2V_1 = -180$$

$$(+j4)V_1 + (1 - j4)V_2 = -180$$

$$(\text{Remember: } \frac{1}{j} = -j \text{ and } \frac{1}{-j} = j)$$

Question 19-22 [4]			Vraag 19-22 [4]		
Use mesh analysis to set up two equations of the following form: $e\bar{I}_1 + f\bar{I}_2 = 16 - j12$ $g\bar{I}_1 + h\bar{I}_2 = 2 A$ Give the coefficients in rectangular form .			Gebruik lusanalyse om twee vergelykings in die volgende vorm op te stel: $e\bar{I}_1 + f\bar{I}_2 = 16 - j12$ $g\bar{I}_1 + h\bar{I}_2 = 2 A$ Gee die koëffisiënte in reghoekige vorm .		
19	e	20	f	19	e
21	g	22	h	21	g
				22	h

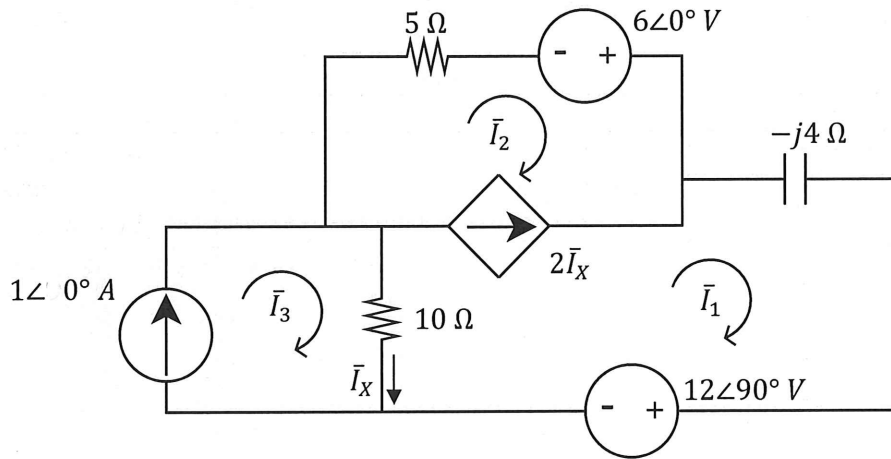

$$* \quad I_3 = 1 A \quad I_x = I_3 - I_1$$

$$* \text{ Supermesh: } 5I_2 - 6 + (-j4)I_1 + j12 + 10I_1 - 10I_3 = 0$$

$$(10 - j4)I_1 + 5I_2 = 6 - j12 + 10(1)$$

$$\underline{\underline{(10 - j4)I_1 + 5I_2 = 16 - j12}}$$





$$* \text{ KCL: } 2I_x = I_1 - I_2$$

$$2(I_3 - I_1) = I_1 - I_2$$

$$2 = I_1 + 2I_3 - I_2$$

$$\underline{\underline{2 = 3I_1 - I_2}}$$


Question 23 & 24 [2]		Vraag 23 & 24 [2]	
Using source transformation, transform the circuit on the left into the circuit on the right. Give the unknown values for the circuit on the right.		Transformeer die kringbaan aan die linkerkant na die kringbaan aan die regterkant d.m.v. brontransformasie. Gee die onbekende waardes vir die regterkantste kringbaan.	
23	k (rectangular form)	23	k (reghoekige vorm)
24	Z (rectangular form)	24	Z (reghoekige vorm)

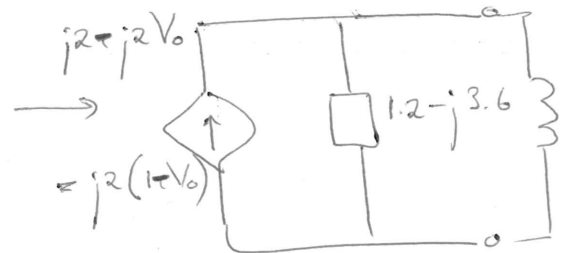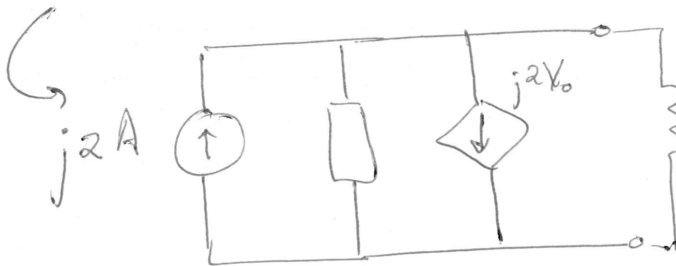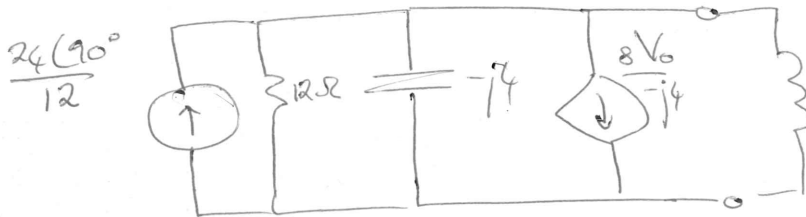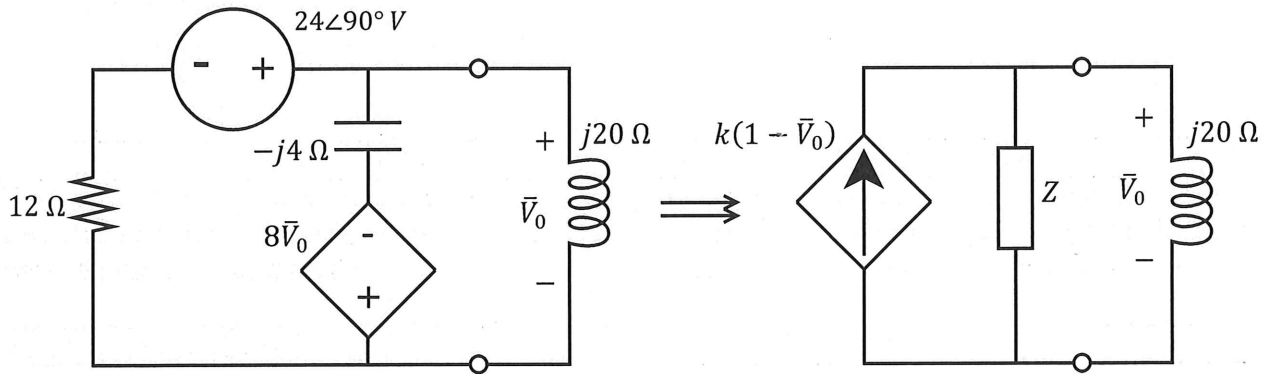

$$\begin{aligned}
 Z_{in} &= 12 \Omega - j4 \\
 &= \frac{12(-j4)}{12 - j4} \\
 &= 1.2 - j3.6 \Omega
 \end{aligned}$$

$$\therefore k = j2$$

Question 25 & 26 [4]		Vraag 25 & 26 [4]	
Calculate the Thevenin equivalent with respect to terminals a-b. <i>rect</i>		Bereken die Thevenin ekwivalent met verwysing tot terminale a-b. <i>rech</i>	
25	$\bar{V}_{TH}$ (polar form)	25	$\bar{V}_{TH}$ (polar vorm)
26	Z_{TH} (rectangular form)	26	Z_{TH} (reghoekige vorm)

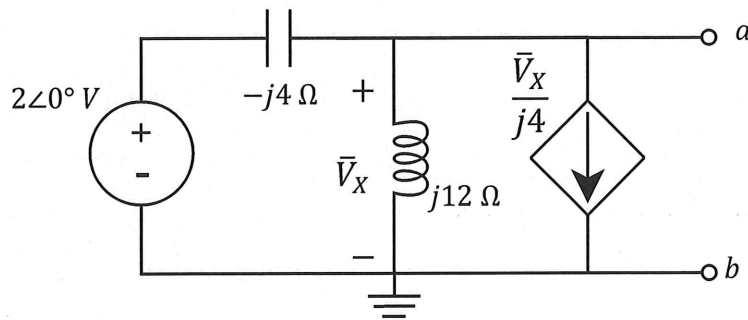

$\bar{V}_{TH}$

$$\frac{V_x - 2}{-j4} + \frac{V_x}{j12} + \frac{V_x}{j4} = 0$$

$$\cancel{\frac{jV_x}{4}} - \cancel{j\frac{2}{4}} - \cancel{j\frac{V_x}{12}} - \cancel{j\frac{V_x}{4}} = 0$$


→ Note: $\frac{1}{j} = -j$

$$\frac{1}{2} = -j\frac{V_x}{12}$$

$$V_x = -6V = V_{TH}$$

$$= 6\angle 180^\circ V$$

Z_{TH}

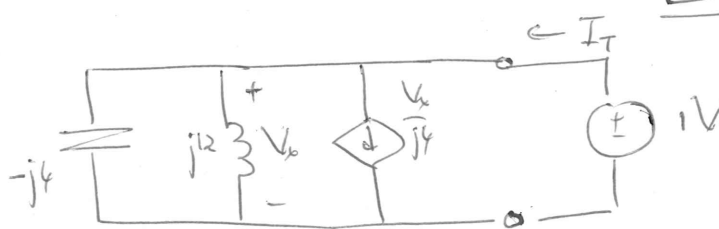


(Test source)

$$V_x = 1$$


$$\begin{aligned} \rightarrow I_T &= \cancel{\frac{V_x}{j4}} + \frac{V_x}{j12} + \cancel{\frac{V_x}{-j4}} \\ &= \frac{V_x}{j12} = \frac{1}{j12} \end{aligned}$$

$$Z_{TH} = j12 \Omega$$

Question 27 & 28 [4]		Vraag 27 & 28 [4]	
Calculate the Norton equivalent with respect to terminals a-b.		Bereken die Norton ekwivalent met verwysing tot terminale a-b.	
27	$\bar{I}_N$ (polar form) <i>rectangular</i>	27	$\bar{I}_N$ (polêre vorm) <i>reghoekig</i>
28	Z_N (rectangular form)	28	Z_N (reghoekige vorm)

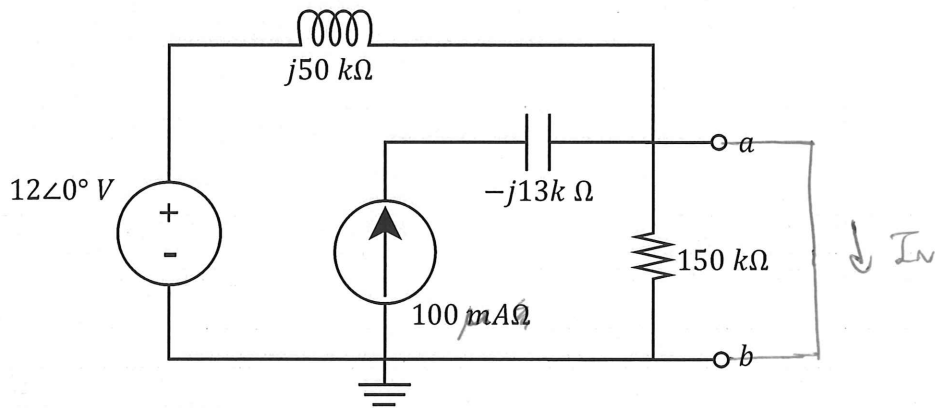


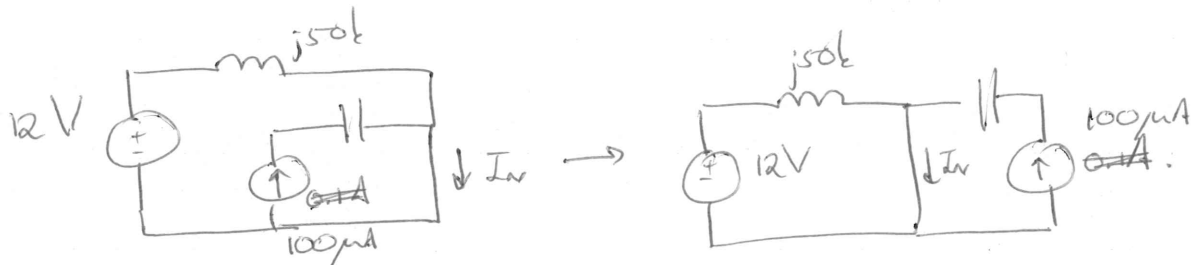I_N * Short circuit means $150\text{ k}\Omega$ can be removed since $0\text{ A} \parallel 150\text{ k}\Omega = 0\text{ A}$.



$$I_N = 0.1\text{ mA} + \frac{12}{j50\text{ k}} \\ = 100 - j240\text{ }\mu\text{A}$$

Z_N

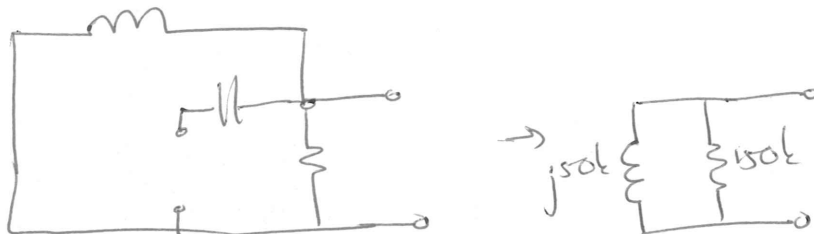

$$Z_N = (j50 \parallel 150)\text{ k} = \left(\frac{150 \times j50}{150 + j50} \right)\text{ k} = (15 + j45)\text{ k}\Omega$$

PRACTICE PAGE / OEFENBLAD 1

Assessment ID

2	0	1	7	E	B	N	1	2	2	S	3		
---	---	---	---	---	---	---	---	---	---	---	---	--	--

Answer

Unit

✓✓	01	$C_{ab} = 90$		μF
✓✓	02	$v_C(t = 0.1s) = -18.097$		V
✓✓	03	$v_L(t = 0.1s) = 9.516$		V
✓✓	04	$w_C = 450$		mJ
✓✓	05	$w_L = 30$		mJ
✓✓	06	Statement #: 2		No unit required
✓✓	07	$\theta = -160$		°
✓✓	08	$z = 1\angle -75^\circ$		No unit required
✓✓	09	$\bar{V}_T = 3\angle -45^\circ$	(polar)	V.
✓✓	10	$\bar{I}_T = 1.5\angle -45^\circ$	(polar)	mA
✓✓	11	$\bar{I}_0 = 6 + j4$	(rectangular)	A
✓✓	12	$\bar{V}_0 = -6$	(rectangular)	V
✓✓	13	$\omega = 2.5$		rad/s
✓✓	14	$Z_{ab} = 6 + j10$	(rectangular)	Ω
✓	15	$a = 6 - j2$	(rectangular)	No units required.
✓	16	$b = j2$	(rectangular)	
✓	17	$c = j4$	(rectangular)	
✓	18	$d = 1 - j4$	(rectangular)	
✓	19	$e = 10 - j4$	(rectangular)	
✓	20	$f = 35$	(rectangular)	
✓	21	$g = 3$	(rectangular)	
✓	22	$h = -1$	(rectangular)	

PRACTICE PAGE / OEFENBLAD 2

Assessment ID

2	0	1	7	E	B	N	1	2	2	S	3		
---	---	---	---	---	---	---	---	---	---	---	---	--	--

Answer

Unit

✓ 23	$k = j2$	(rectangular)	No unit required
✓ 24	$Z = 1.2 - j3.6$	(rectangular)	Ω
✓ 25	$\bar{V}_{TH} = -6$	(polar) rectangular	V
✓ 26	$Z_{TH} = j12$	(rectangular)	Ω
✓ 27	$\bar{I}_N = 100 - j240$	(polar) rectangular	μA
✓ 28	$Z_N = 15 + j45$	(rectangular)	$k\Omega$