

Departement Elektriese, Elektroniese en
Rekenaar-Ingenieurswese

Department of Electrical, Electronic and
Computer Engineering

Semestertoets 3

Kopiereg voorbehou

Semester Test 3

Copyright reserved

Module EBN122

Elektrisiteit en Elektronika

November 2016

Module EBN122

Electricity and Electronics

November 2016



UNIVERSITEIT VAN PRETORIA
UNIVERSITY OF PRETORIA
YUNIBESITHI YA PRETORIA

Exam information:

Eksamensinligting:

Maximum marks:	45	Full marks:	46
Maksimum punte:		Volpunte:	
Duration of paper:	90 minutes	Open / closed book:	Closed
Duur van vraestel:	90 minute	Oopboek / toeboek:	Toe
Total number of pages (including this page):	13		
Totale aantal bladsye (hierdie blad ingesluit):			

IMPORTANT - BELANGRIK

- The examination regulations of the University of Pretoria apply.*
Die eksamenregulasies van die Universiteit van Pretoria geld.
- All questions must be answered on the ANSWER SHEET.*
Alle vrae moet op die ANTWOORDBLAD beantwoord word.
- Students may do their own rough calculations on the question paper – the question paper will not be taken in.*
Studente mag hul eie rowwe berekeninge op die vraestel doen – die vraestel word nie ingeneem nie.
- Answers must include units!*
Antwoorde moet eenhede insluit!
- Final answers must be written as real numbers, and not as fractions.*
Finale antwoorde moet as reële getalle geskryf word, en nie as breuke nie.

Dosent(e):
Lecturer(s):

1. D le Roux
2. R dos Santos
3. J Joubert

EBN122 SEMESTER TEST/ TOETS 2 (NOV 2016)

ANSWER SHEET / ANTWOORDBLAD

Surname: Van:		Student number: Studentennummer:							
Initials: Voorletters:		Group: Groep:	ENGLISH (Eng 3-1)	ENGLISH (Eng 3-6)	AFR				

Q1+2	14	Q3	16	Q4	16	Tot:	46	/45
------	----	----	----	----	----	------	----	-----

VRAAG 1 – QUESTION 1 (4)

1	a) $V_1 = 2V \checkmark$	b) $\alpha = 4 \checkmark$
---	--------------------------	----------------------------

QUESTION 2 - VRAAG 2 (10)

2.1	$i_{C(2s)} = 1.36mA \checkmark$	
2.2	$i_{L(0 \text{ to } 6s)} = 4.8A \checkmark$	
2.3	$C_{eq} = 3F \checkmark$	
2.4	$w_C = 0.36J = 360mJ \checkmark$	$w_L = 24J \checkmark$

VRAAG 3 – QUESTION 3 (16)

3.1	a) $\bar{V} = -21.21 + j11.21V \checkmark$ (rectangular)	
	b) $\bar{Z}_L = 50 \angle 90^\circ \Omega \checkmark$ (polar)	
	c) $i_C(t) = 5 \cos(5000t + 110^\circ) A \checkmark$	
3.2	a) $\bar{I}_1 = 1 + j5A \checkmark$ (rectangular)	b) $\bar{V}_2 = 0.79 \angle 108.4^\circ V \checkmark$ (polar)
3.3	$\bar{Z}_{ab} = 20 - j60 \Omega \checkmark$ (rectangular)	
3.4	a) $\bar{I}_a = 1.5 - j3A \checkmark$ (rectangular)	b) $\bar{I}_a = 0.74 \angle 92.9^\circ A \checkmark$ (polar)

VRAAG 4 – QUESTION 4 (16)

4.1	$a_1 + ja_2 = 2 + j3 \checkmark$	$b_1 + jb_2 = 0 + j(-3) \checkmark$
	$c = 3 \checkmark$	$d = 8 \checkmark$
4.2	$e_1 + je_2 = 5 + j \checkmark$	$f_1 + jf_2 = 4 + j(-2) \checkmark$
	$g = 1 \checkmark$	$h = -1 \checkmark$
4.3	$\bar{V}_{TH} = 4.8 + j2.4V \checkmark$ (rectangular)	$Z_{TH} = (2.4 - j2.4)k\Omega \checkmark$ (rectangular)
4.4	$\bar{I}_N = 4A \checkmark$ (rectangular)	$Z_N = 2.828 \angle 45^\circ \Omega \checkmark$ (polar)