
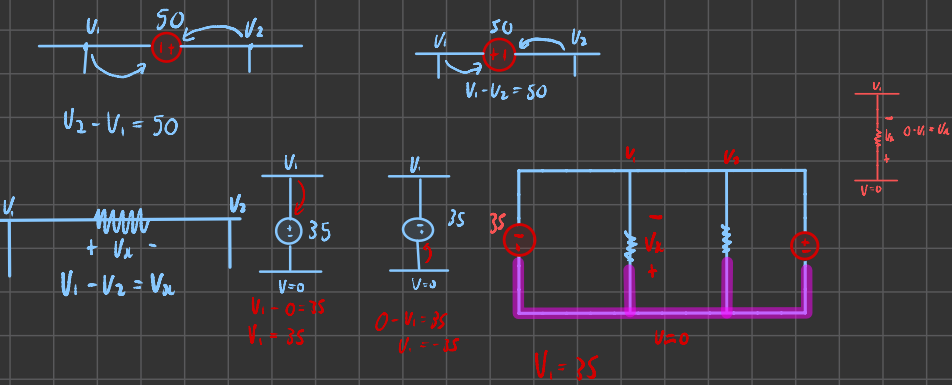


Recap

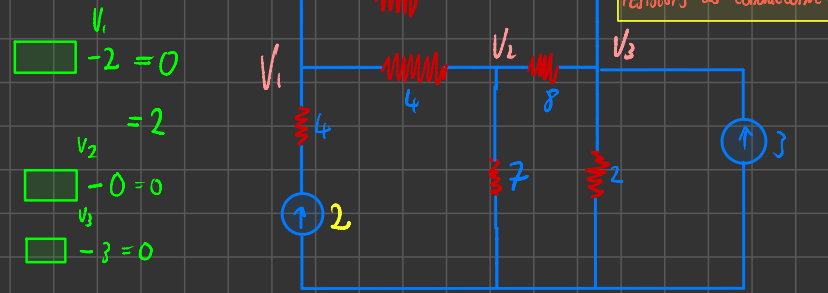

Inspection by Nodal



When we do inspection by nodal, we are using resistors as conductance ($G = \frac{1}{R}$)

$$\begin{bmatrix} 1 & 2 & 3 \\ 1 & 7/12 & -1/4 & -1/3 \\ 2 & -1/4 & 29/56 & -1/8 \\ 3 & -1/3 & -1/8 & 23/24 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 3 \end{bmatrix}$$

$$\frac{1}{4} + \frac{1}{3} = \frac{7}{12}$$

$$\frac{1}{4} + \frac{1}{7} + \frac{1}{8} = \frac{29}{56}$$

$$\frac{1}{8} + \frac{1}{3} + \frac{1}{2} = \frac{23}{24}$$

Add all conductance attached to V_1
multiply upper lower triangle with negative

$$\begin{bmatrix} 1 & 2 & 3 \\ 1 & R & -1/4 & 0 \\ 2 & -1/4 & 29/56 & -1/8 \\ 3 & -1/3 & -1/8 & 23/24 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ P \end{bmatrix}$$

$$R = \frac{1}{4} + \frac{1}{3} = \frac{7}{12}$$

4 below is not added, current is present

$$\frac{V_1}{4} + \frac{V_1 - V_2}{3} = 2$$

$$\frac{7V_1}{12} - \frac{V_2}{4} - \frac{V_3}{3} = 2$$

$$\frac{7}{12}V_1 - \frac{1}{4}V_2 - \frac{1}{3}V_3 = 2$$

$$0 = -\frac{1}{3}$$


symmetric

$$K = -\frac{1}{8}$$

$$P = 3$$

$$\frac{V_2 - V_1}{6} + \frac{V_2}{7} + \frac{V_2 - V_3}{8} = 0$$
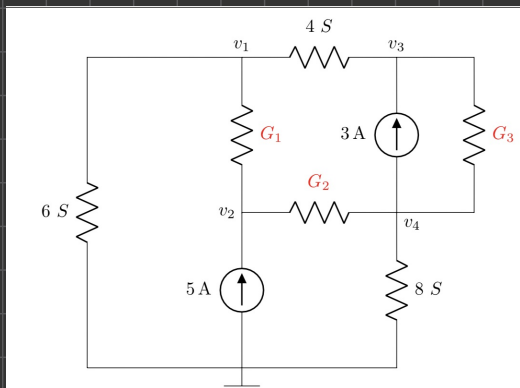
$$-\frac{1}{6}V_1 + \frac{29}{56}V_2 - \frac{1}{8}V_3 = 0$$



$$V = -G_2$$

$$W = G_3 + 8 + G_2$$


$$Y = 3$$

$$G_1 = 10$$

$$G_2 = 6$$

$$G_3 = 9$$

$$G_1 + G_2 =$$

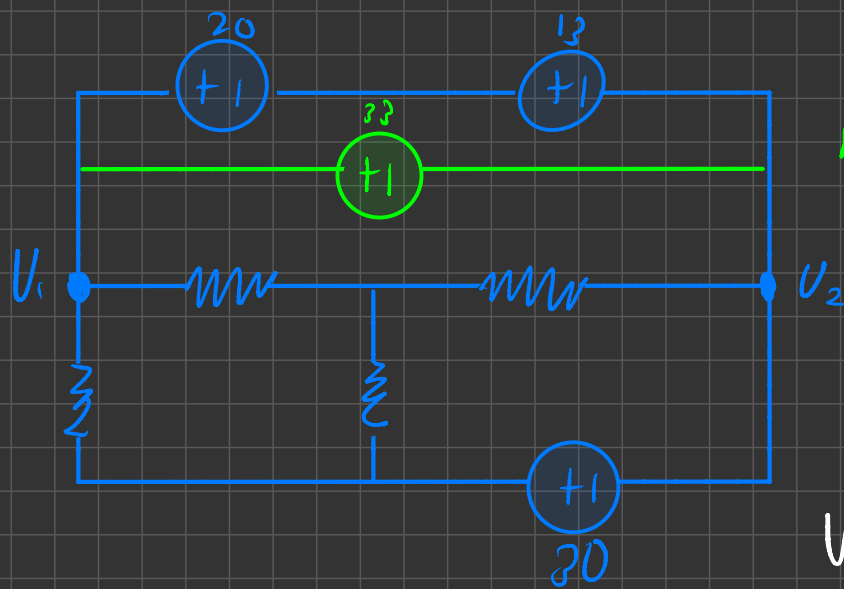

new line

$$V_2 = -30$$

$$V_1 - V_2 = 33$$


$$V_1 - (-30) = 33$$

Some polarity



take the larger value

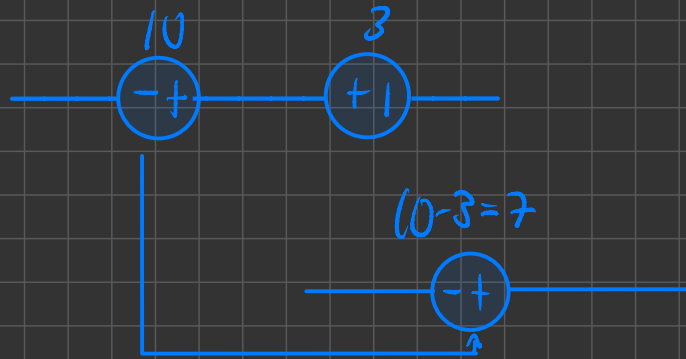and add the smaller value, maintaining polarity and shape of the bigger value



$$10 - 3 = 7$$

23 August 2019 Semester Test 1, Page 15 of 18 2019EBN122S01

Questions 28 to 31 [4]

Use inspection to compile a matrix equation of the form below

$$\begin{bmatrix} 9 & -3 & -2 & 0 \\ -3 & v & -1 & 0 \\ -2 & -1 & 7 & w \\ 0 & 0 & w & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 15 \\ x \\ -15 \\ y \end{bmatrix}$$

and provide the values of the matrix elements v, w, x and y .


28 v [1] 29 w [1] 30 x [1] 31 y [1]

$$V = 4$$

$$W = -4$$

$$X = -10$$

$$Y = -20$$

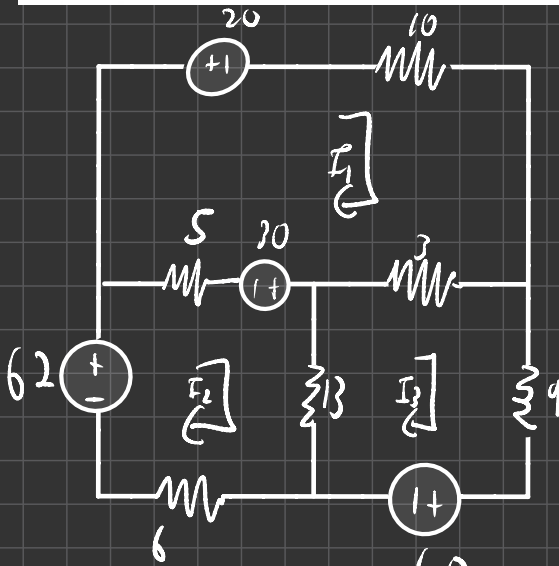

$$\begin{bmatrix} 18 & -5 & -3 \\ -5 & 24 & -13 \\ -3 & -13 & 25 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -50 \\ 92 \\ -40 \end{bmatrix}$$