

27/08/2023

$$q = 2e^{-4t}$$

current when $t = 5s$

$$i = ?$$

$$i = \frac{dq}{dt}$$


press shift then integral button to differentiate

$$\rightarrow \frac{d}{dx} 2e^{-4x} \Big|_{x=5}$$


$$q = -16.49 \text{ nA}$$

use $i = \frac{q}{t}$ when given constant values
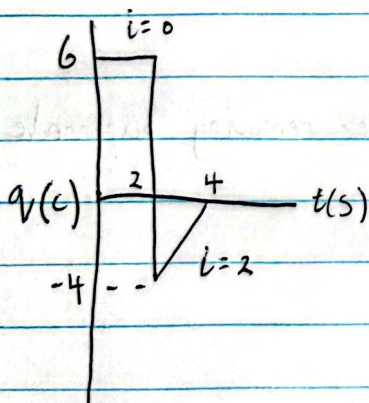
$$\Rightarrow \text{i.e. } q = 7C \quad t = 6s$$



calculate power

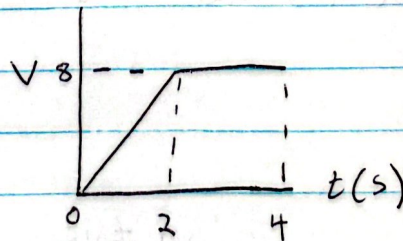


Calculate power $0 \leq t \leq 4$

- $i = 0 \quad 0 \leq t \leq 2 \quad (\text{gradient})$
- $\frac{-4 - 0}{2 - 4} = 2 \quad i = 2 \quad 2 < t \leq 4$

$$V_{\text{total}} = \text{area} \\ \frac{1}{2}(2)(8) + (2 \times 8) \\ = 24 \text{ V}$$

$$i \text{ between } 0 - 4 = 0 + 2 = 2$$
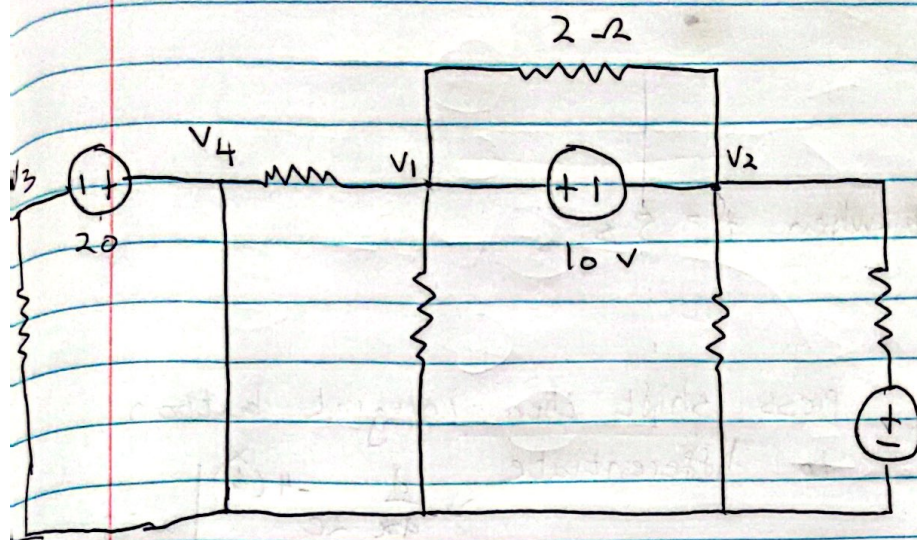
$$P = VI \\ = 24 \times 2 \\ = 48 \text{ W}$$



Supernode $\Rightarrow$ voltage source between 2 node points without a resistor inbetween


$$v_1 - v_2 = 10 \quad (1)$$

remove supernode

$$\text{node 1} + \text{node 2} = 0 \quad (2)$$

$$v_4 - v_3 = 20 \quad (3)$$
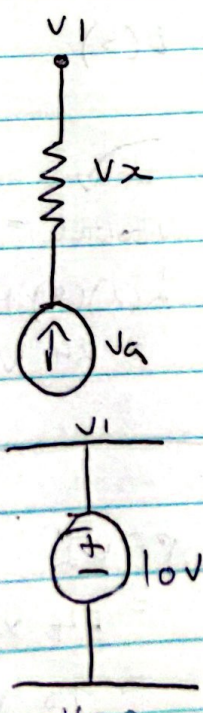
$$\text{node 4} + \text{node 3} = 0 \quad (4) \quad (\text{after removing supernode})$$




$$v_1 \neq v_2$$

current source has voltage

$$v_1 = v_x + v_a$$

$$v_1 = 10 \text{ V}$$

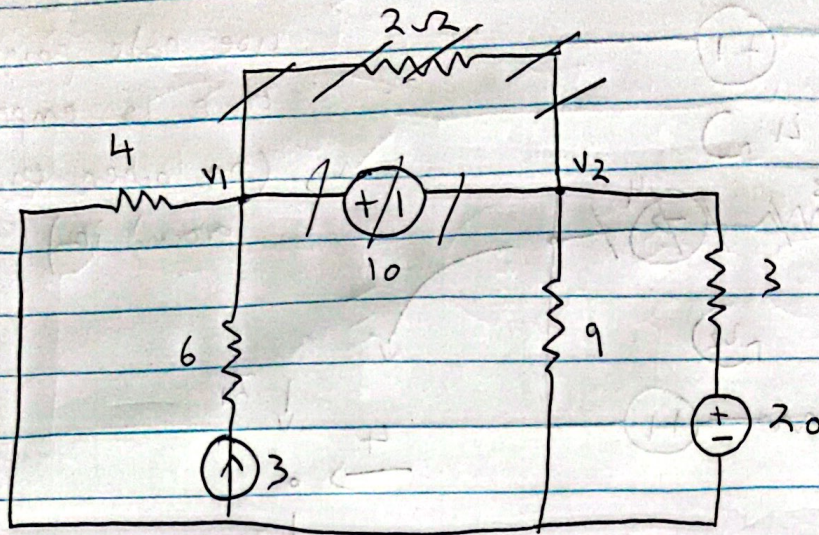

$$\bullet \quad v_1 - v_2 = 10$$

remove supernode AND 2Ω resistor

↓
because it is in
parallel w v_1 and v_2

$$\text{Node 1} + \text{Node 2} = 0$$


$$\frac{v_1}{4} + (-3) + \frac{v_2}{9} + \frac{v_2 - 20}{3} = 0$$

If you forgot to remove 2Ω resistor


$$\frac{v_1}{4} - 3 + \left[\frac{v_1 - v_2}{2} + \frac{v_2 - v_1}{2} \right] + \frac{v_2}{9} + \frac{v_2 - 20}{3} = 0$$

$$\leftarrow \quad 0v_1 + 0v_2$$
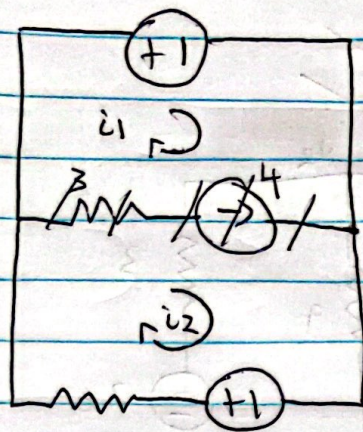
$$\frac{v_1}{4} - 3 + \frac{v_2}{9} + \frac{v_2 - 20}{3} = 0$$



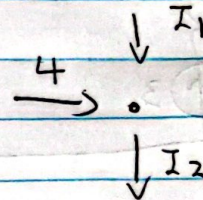
use node point
that is empty
(no other things
around it)



$$I_n = \text{out}$$

$$4 + I_1 = I_2$$

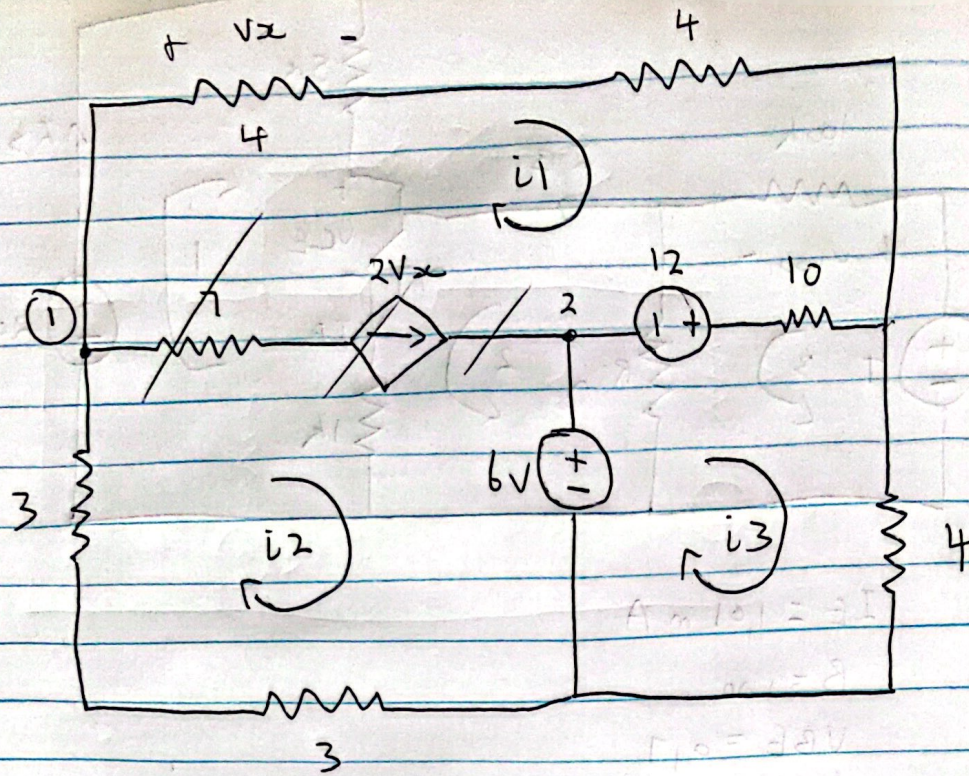when you remove supermesh, also remove the
3 Ω resistor



$$\textcircled{2} a_{i1} + b_{i2} + c_{i3} = -18$$

$$\textcircled{1} * d_{i1} - i_2 = 0$$

$$\textcircled{3} -10i_2 + 14i_3 = 18 \quad \text{Point 1}$$

~~Loop 1~~

Supermesh

$I_n = \text{out}$

$\textcircled{1}$

$$I_2 = I_1 + 2V_x$$

$$I_2 = 9I_1$$

$$* 9I_1 - I_2 = 0 \quad \textcircled{1}$$

take out supermesh

$$\begin{aligned} V_x &= \frac{1}{4} \int I_R \\ &= + I_1 \times 4 \\ V_x &= 4I_1 \end{aligned}$$


loop 1 + loop 2 = 0

$$18I_1 - 10I_3 + 6I_2 + 6 + 12 = 0$$

$$18I_1 - 10I_3 + 6I_2 = -18 \quad \textcircled{2}$$

Loop 3
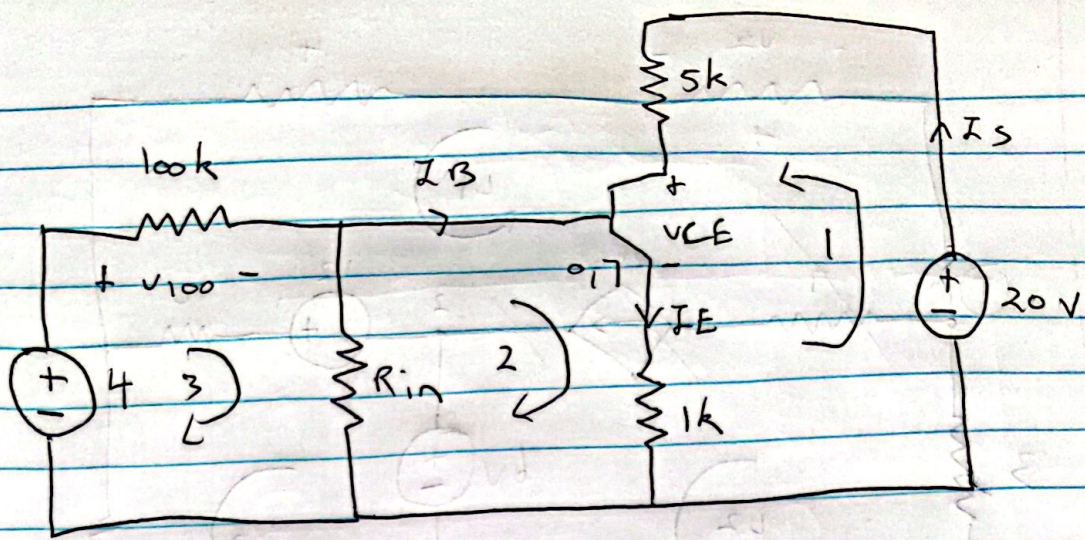
$$14I_3 - 10I_1 = 18 \quad \textcircled{3}$$



$$I_E = 1.01 \text{ mA}$$

$$\beta = 100$$

$$V_{BE} = 0.7$$

$$I_E = (1 + \beta) I_B = 101 I_B$$

$$1.01 \times 10^{-3} = 101 I_B$$

$$I_B = \frac{1.01 \times 10^{-3}}{101} = 10 \times 10^{-6} \text{ A}$$

$$I_C = I_E = 1.01 \text{ mA}$$

1 KVL

$$-20 + 5000 I_C + V_{CE} + 1000 I_E = 0$$

2 KVL

$$-V_R + 0.7 + 1000 I_E = 0$$

3 KVL

$$-4 + V_{100} + V_R = 0$$