

2.22) Power delivered?

b)

Voltage division:

$$V_o = \frac{-4}{6+4} \cdot V_{oc}$$

$$V_o = -0.4 V_{oc}$$

$$\therefore V_{oc} = \frac{-4.44}{-0.4}$$

$$\underline{V_{oc} = 11.1 \text{ V}} \rightarrow$$

Thus

$$p = V_{oc} I_2$$

$$p = (11.1)(2 V_o)$$

$$\underline{p = -98.57 \text{ W}} \rightarrow$$