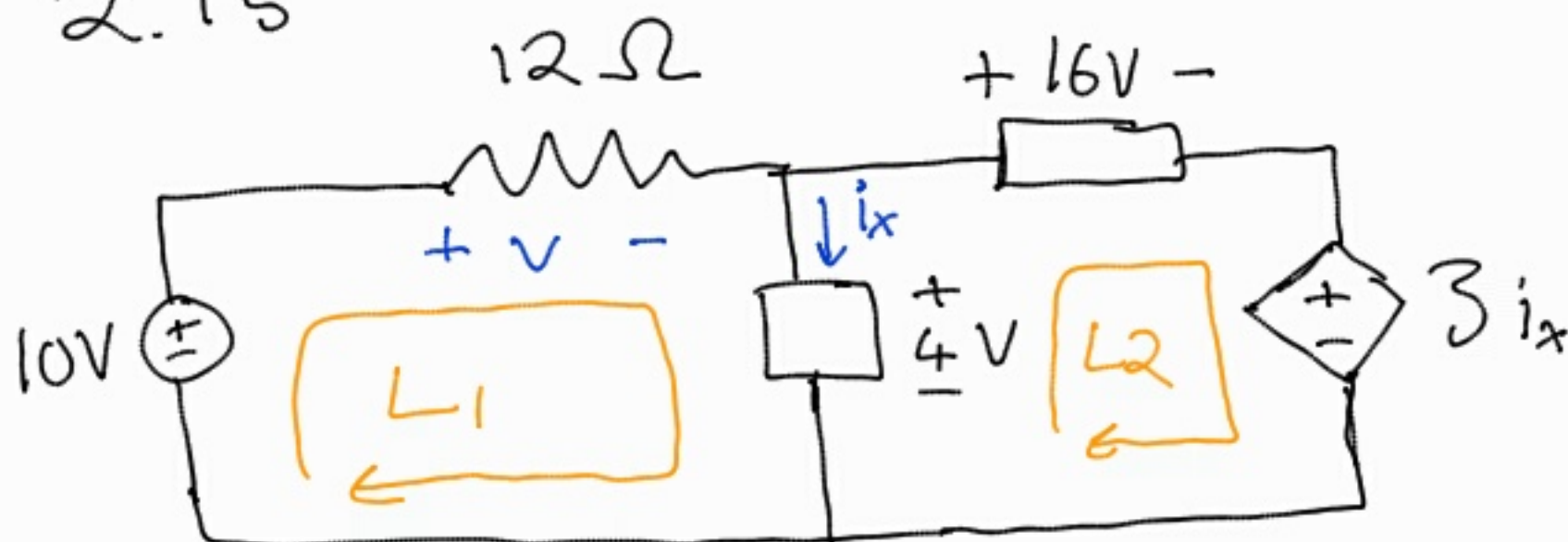


Tutorial 2

2.15



$$\text{KVL: } \sum V_i = 0$$

Loop 1:

$$-10 + v + 4 = 0$$

$$v = 10 - 4$$


$$v = 6 \text{ V}$$

Loop 2:

$$-4 + 16 + 3i_x = 0$$

$$3i_x = -12$$

$$i_x = -4 \text{ A}$$

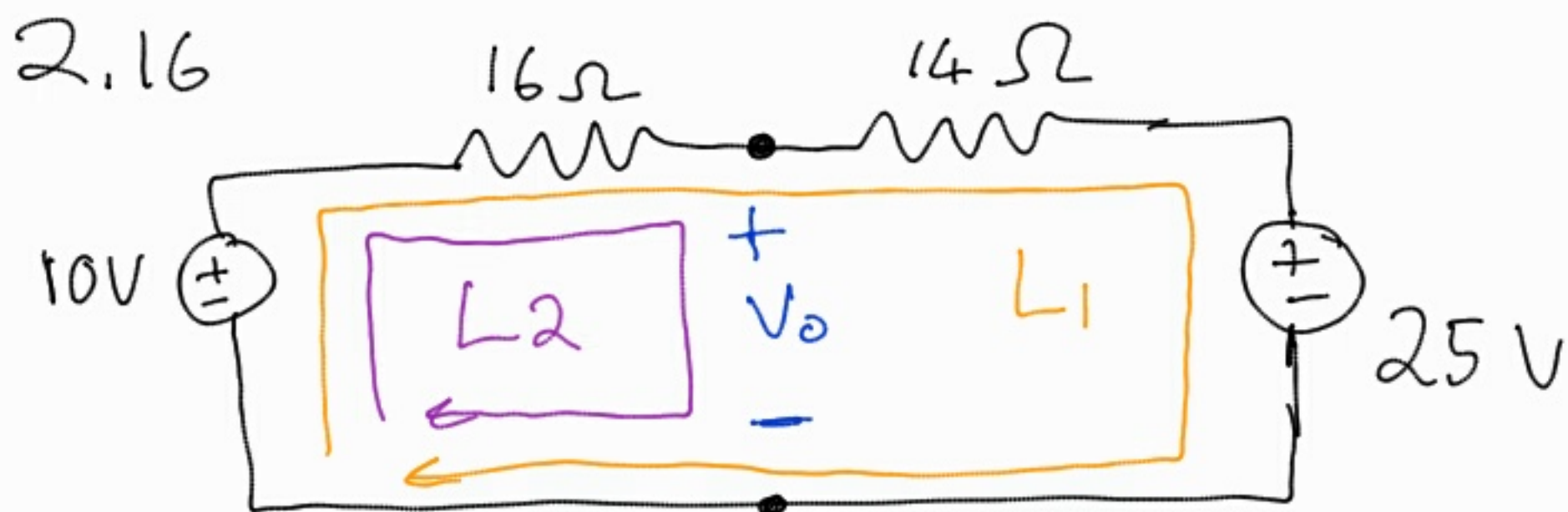

Loop 1: Use KVL and Ohm's Law to find the current.

$$-10 + 16I + 14I + 25 = 0$$

$$30I = -15$$

$$I = -0,5 \text{ A}$$


Loop 2: Use KVL & I

$$-10 + 16I + V_0 = 0$$

$$-10 - 8 + V_0 = 0$$

$$V_0 = 18 \text{ V}$$

2.22

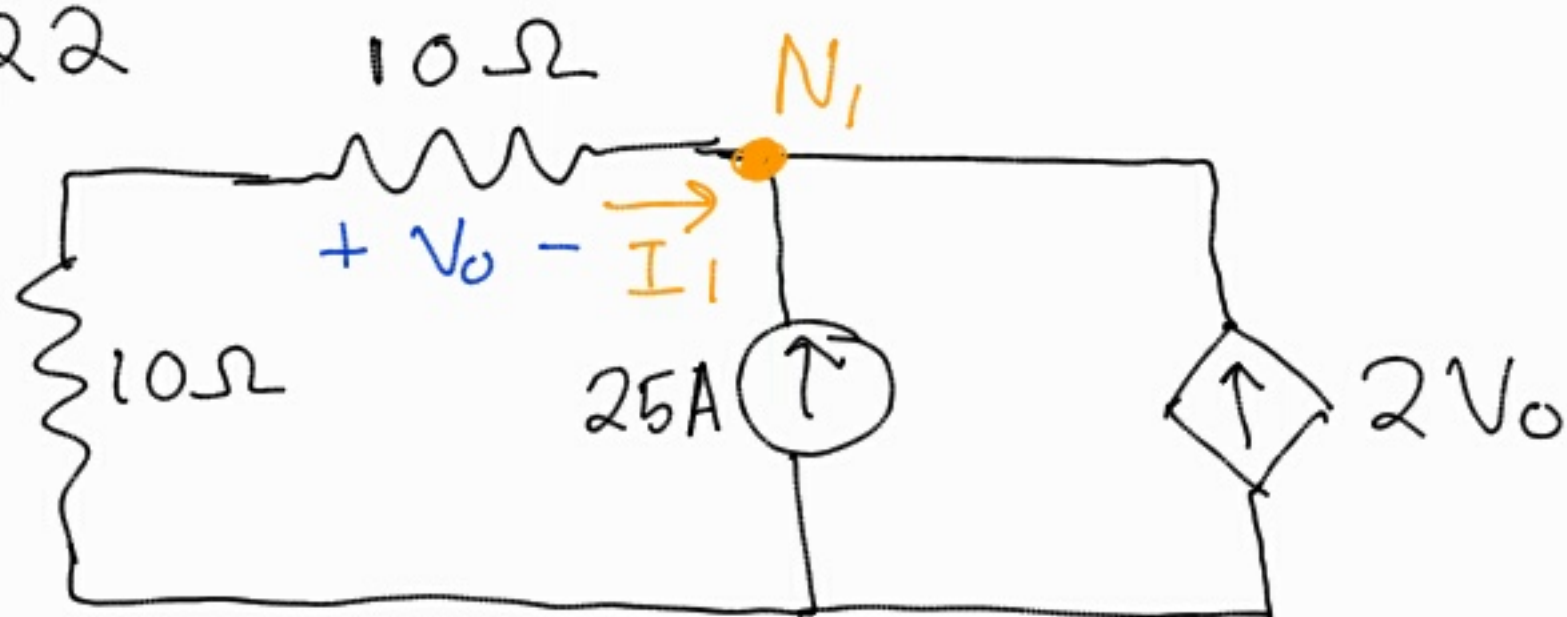

Apply KCL at node 1

$$\sum I_n = 0$$

$$25 + 2V_0 + I_1 = 0$$

$$I_1 = -25 - 2V_0$$

Use ohm's Law at V_0

$$V = I \cdot R$$


$$V_0 = (-25 - 2V_0) \cdot 10$$

$$V_0 = -250 - 20V_0$$


$$21V_0 = -250$$

$$V_0 = 11,9 \text{ V}$$

2,23

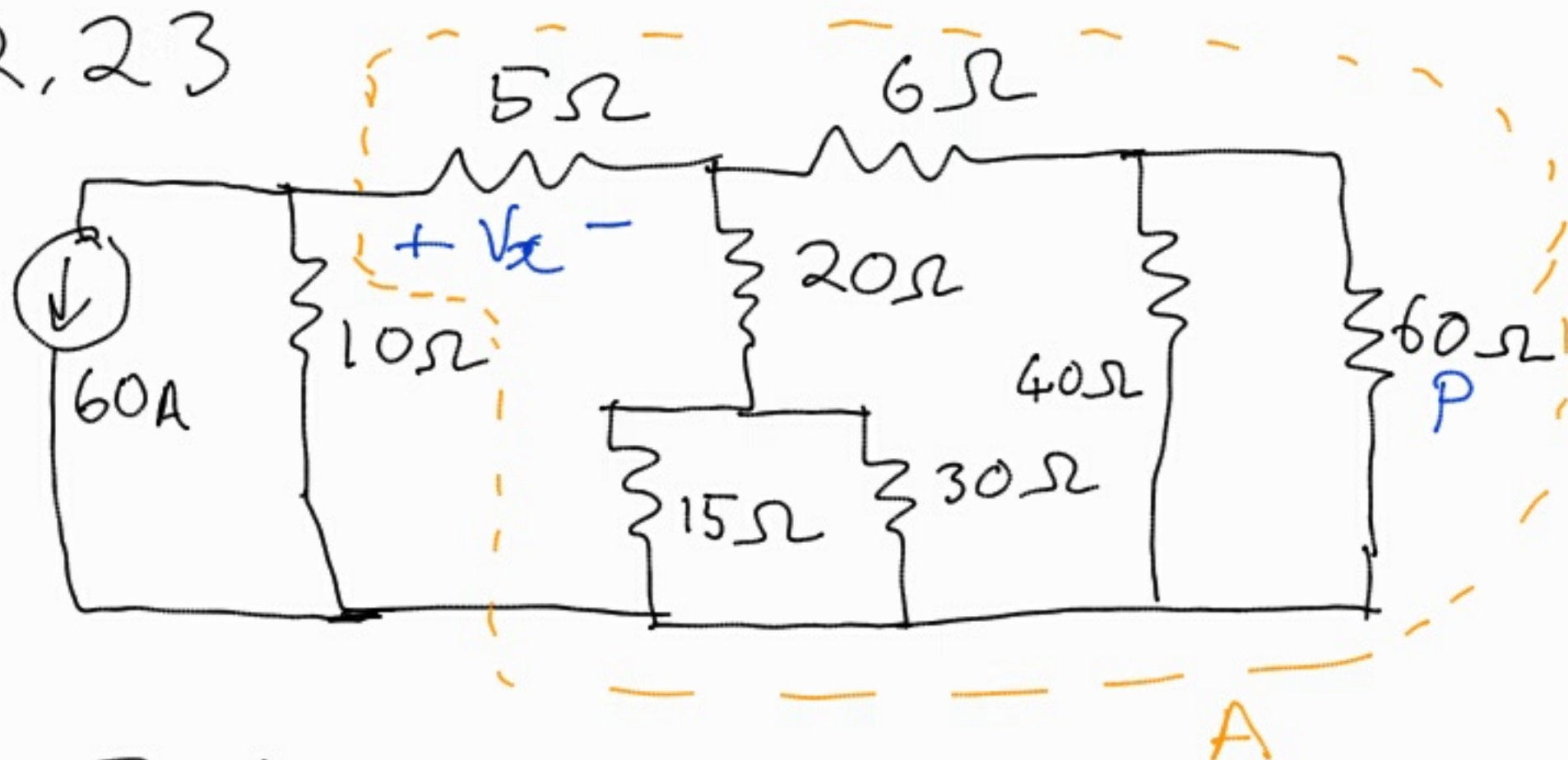

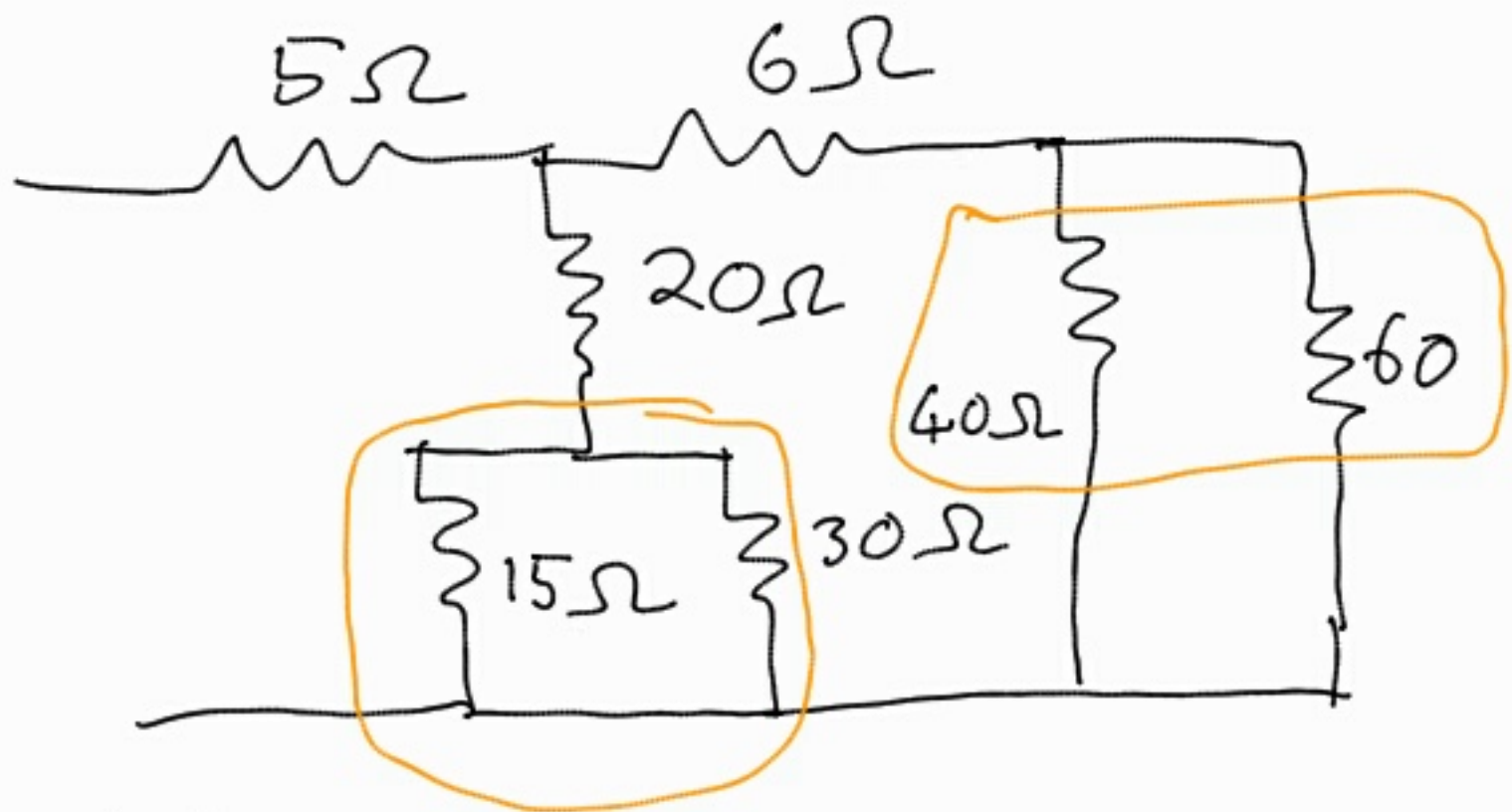
1. Find the current going to part A of the circuit vs the current going to the 10Ω resistor. By collapsing the resistor network,



Parallel Resistors

$$15 \parallel 30 = \frac{15 \times 30}{15 + 30}$$
$$= 10\Omega$$

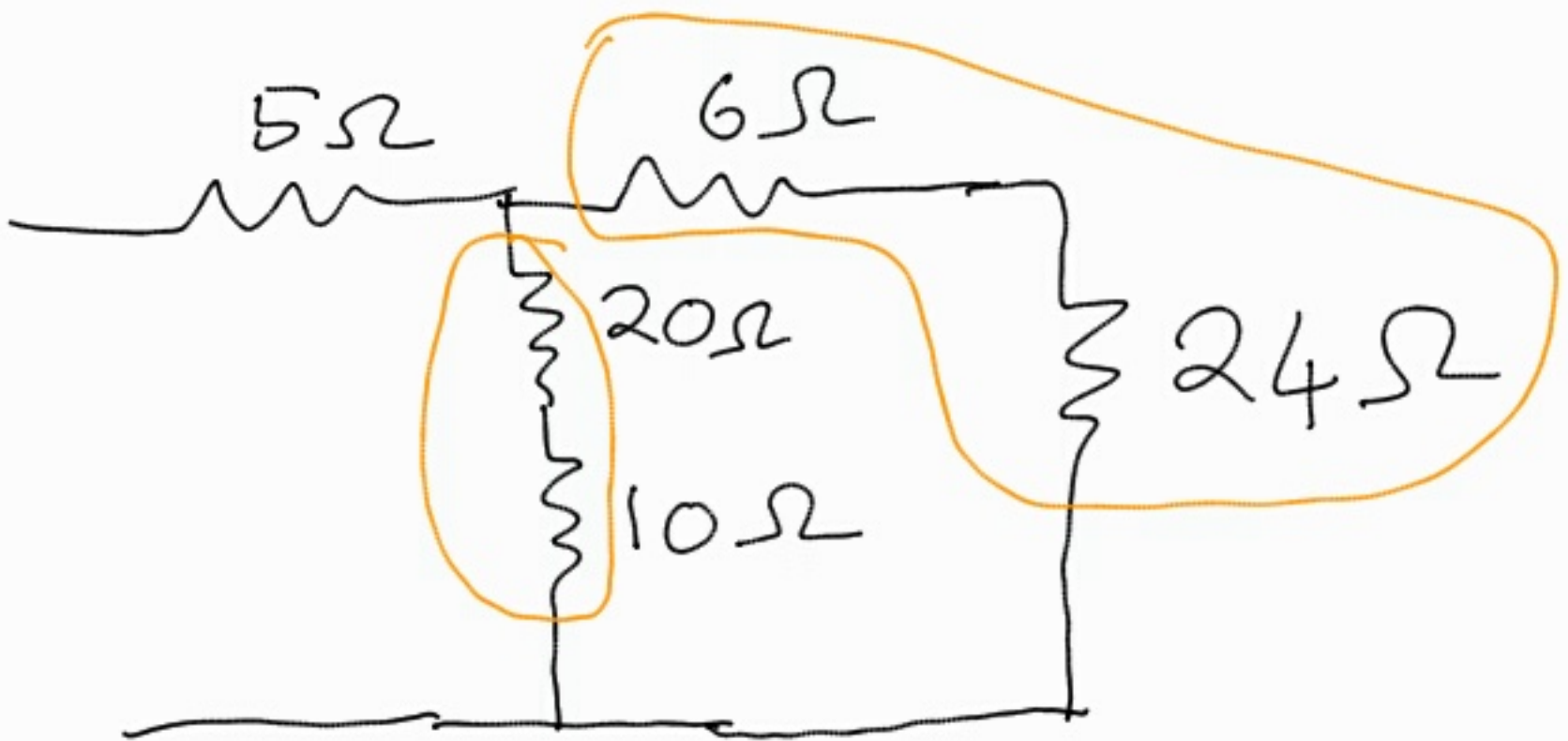
$$40 \parallel 60 = \frac{40 \times 60}{40 + 60}$$
$$= 24\Omega$$



Add series resistors.

$$20 + 10 = 30\Omega$$


$$6 + 24 = 30\Omega$$

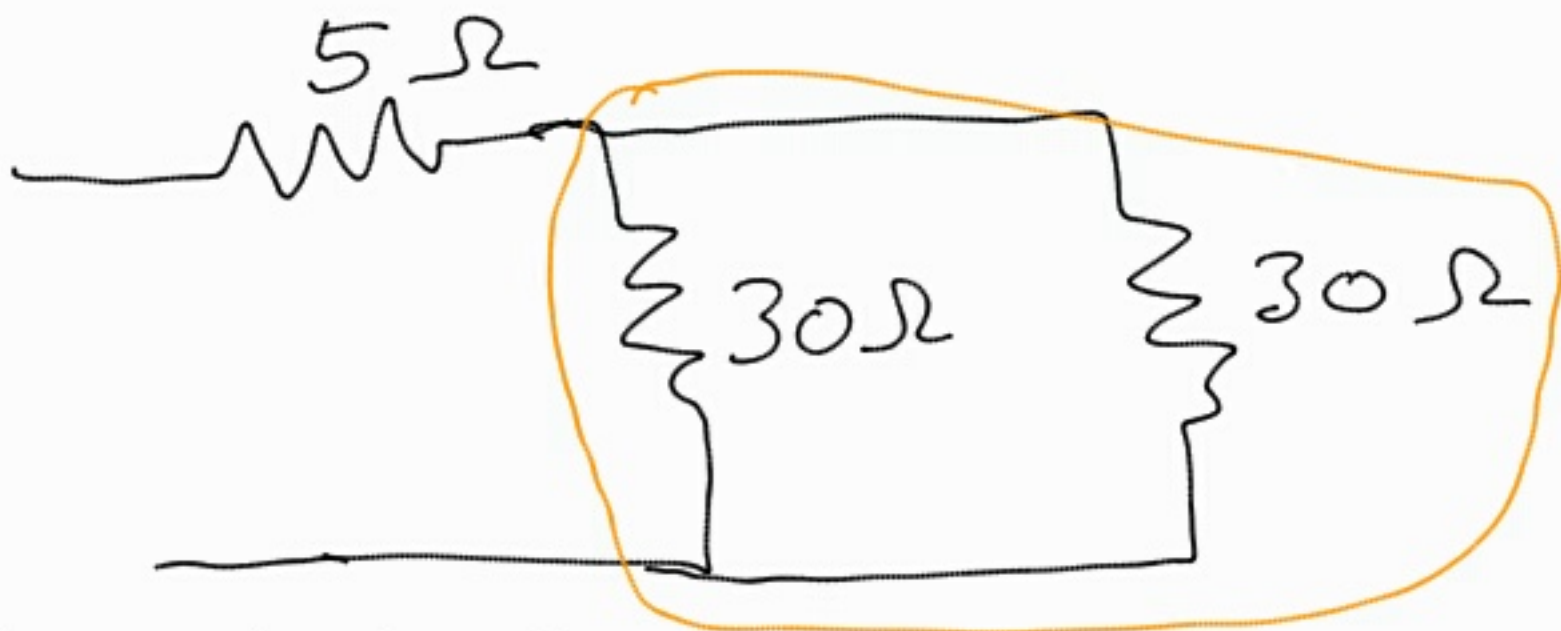

Parallel Resistors

$$30 \parallel 30 = \frac{30 \times 30}{30 + 30} = 15\Omega$$

The complete circuit

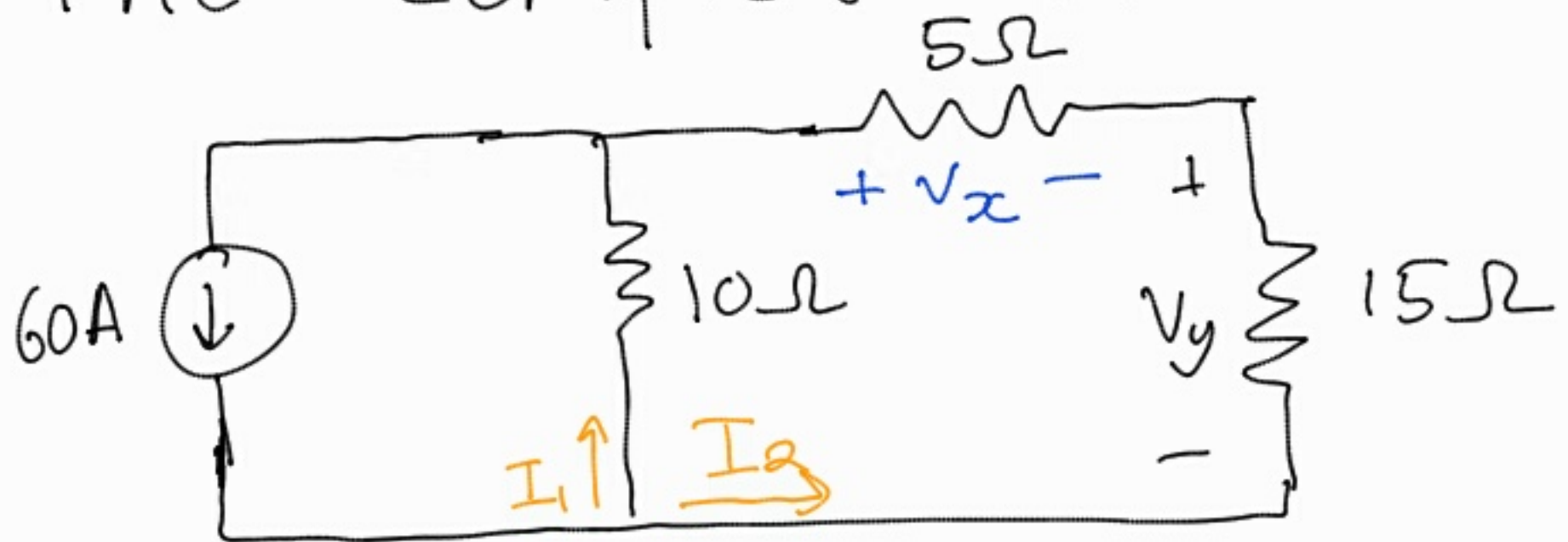

The $[5\Omega + 15\Omega]$ pair is in parallel with the 10Ω resistor.

Using current division,

$$I_2 = \frac{I \times R_1}{R_1 + R_2}$$

$$I_2 = \frac{60 \times 10}{10 + (5 + 15)}$$

$$= 20 \text{ A}$$

Using Ohm's Law to find

$$V_x$$

$$V = I \cdot R$$

$$V_x = -20 \times 5$$

$$V_x = -100 \text{ V} \text{ [Since } I_2 \text{ enters from negative terminal of } V_x \text{]}$$


The voltage across the 15Ω resistor.

$$V = I \cdot R$$

$$V_y = -20 \times 15$$

$$V_y = -300 \text{ V}$$

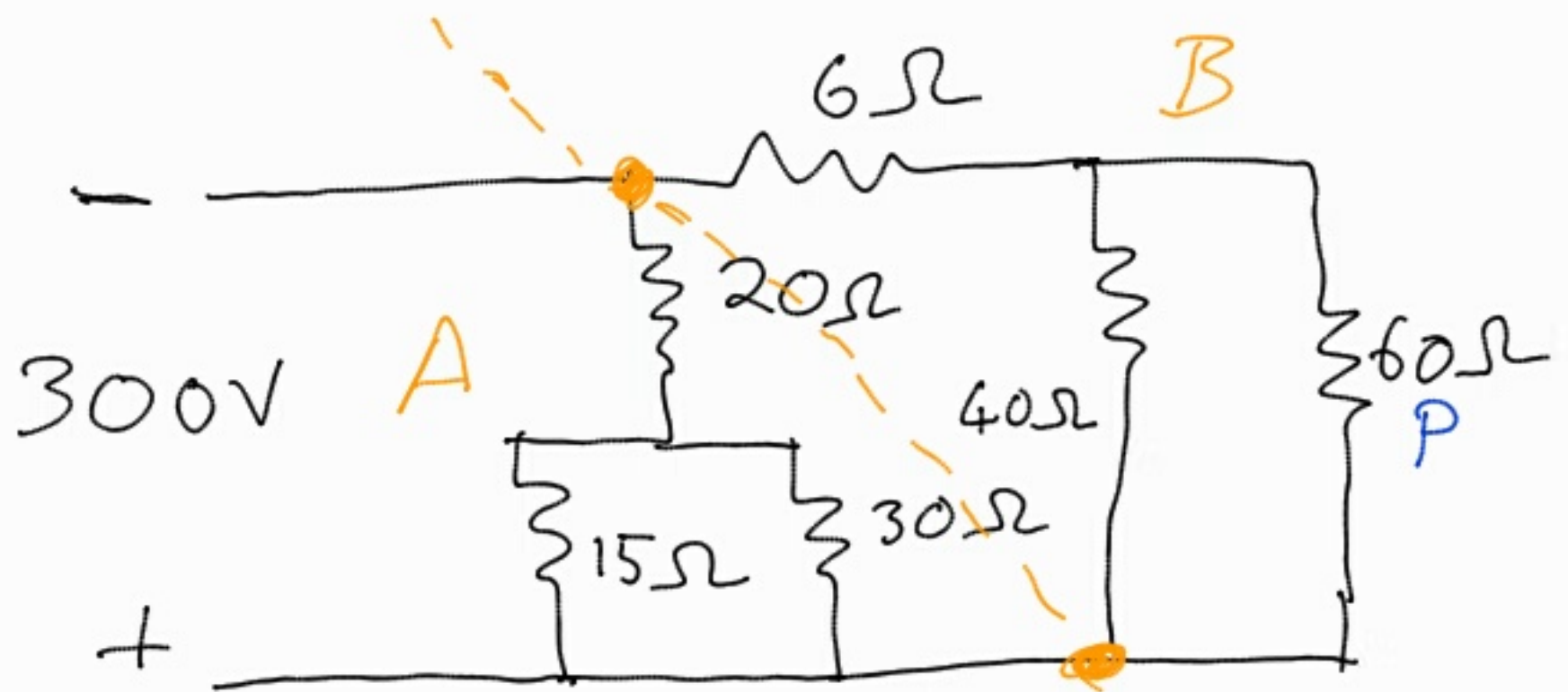To find P expand 15Ω resistor into original network



Since parts A and B are parallel, they share the same voltage.



To find I, notice that

$$40 \parallel 60 = \frac{40 \times 60}{40 + 60}$$

$$= 24$$




Apply Ohm's Law

$$I = \frac{V}{R}$$

$$I = \frac{300}{30}$$

$$= 10A$$

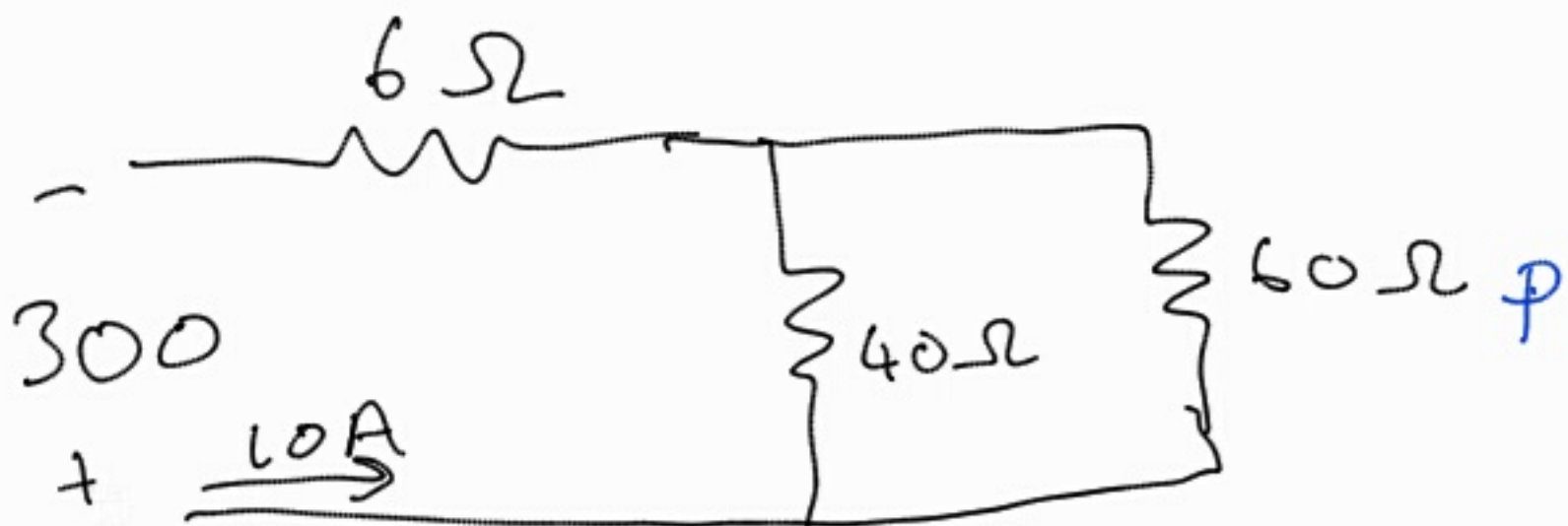

Finally use current division
to find current through
60Ω

$$I_{60} = \frac{I R_1}{R_1 + R_2}$$

$$I_{60} = \frac{10 \cdot 40}{40 + 60}$$

$$I_{60} = 4 \text{ A}$$

Ohm's law for the voltage

$$V = I \cdot R$$

$$V_{60} = 4 \times 60$$

$$V_{60} = 240 \text{ V}$$

$$\begin{aligned} P &= V \cdot I \\ &= 240 \times 4 \\ &= 960 \text{ W} \end{aligned}$$

2,24



Apply KVL at loop 1. ($\sum v = 0$)

$$-V_s + I_o R_1 + I_o R_2 = 0 \quad (V = IR)$$

$$I_o (R_1 + R_2) = V_s$$

$$I_o = \frac{V_s}{R_1 + R_2} \quad (1)$$

Apply KCL at node 1 ($\sum I = 0$)

$$\alpha I_o + \frac{V_o}{R_3} + \frac{V_o}{R_4} = 0 \quad (I = \frac{V}{R})$$

$$\alpha I_o = -V_o \left(\frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$I_o = \frac{-V_o}{\alpha} \left(\frac{1}{R_3} + \frac{1}{R_4} \right) \quad (2)$$

setting ① = ②

$$\frac{V_s}{R_1 + R_2} = \frac{-V_o}{\alpha} \left(\frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$\frac{V_s}{R_1 + R_2} = \frac{-V_o}{\alpha} \left(\frac{R_4 + R_3}{R_3 R_4} \right)$$

$$-\frac{\alpha R_3 R_4}{R_4 + R_3} \cdot \left(\frac{1}{R_1 + R_2} \right) = \frac{V_o}{V_s}$$

let $R_1 = R_2 = R_3 = R_4 = R$

$$\frac{-\alpha R \cdot R}{(R + R)(R + R)} = \frac{V_o}{V_s}$$

$$\frac{-\alpha R^2}{2R \cdot 2R} = \frac{V_o}{V_s}$$

$$\frac{-\alpha R^2}{4R^2} = \frac{V_o}{V_s}$$

$$\frac{-\alpha}{4} = \frac{V_o}{V_s}$$


$$\text{let } \left| \frac{V_o}{V_s} \right| = 10$$

$$\left| \frac{\alpha}{-4} \right| = \left| \frac{V_o}{V_s} \right|$$

$$\frac{\alpha}{4} = 10$$

$$\alpha = 40$$

2,25

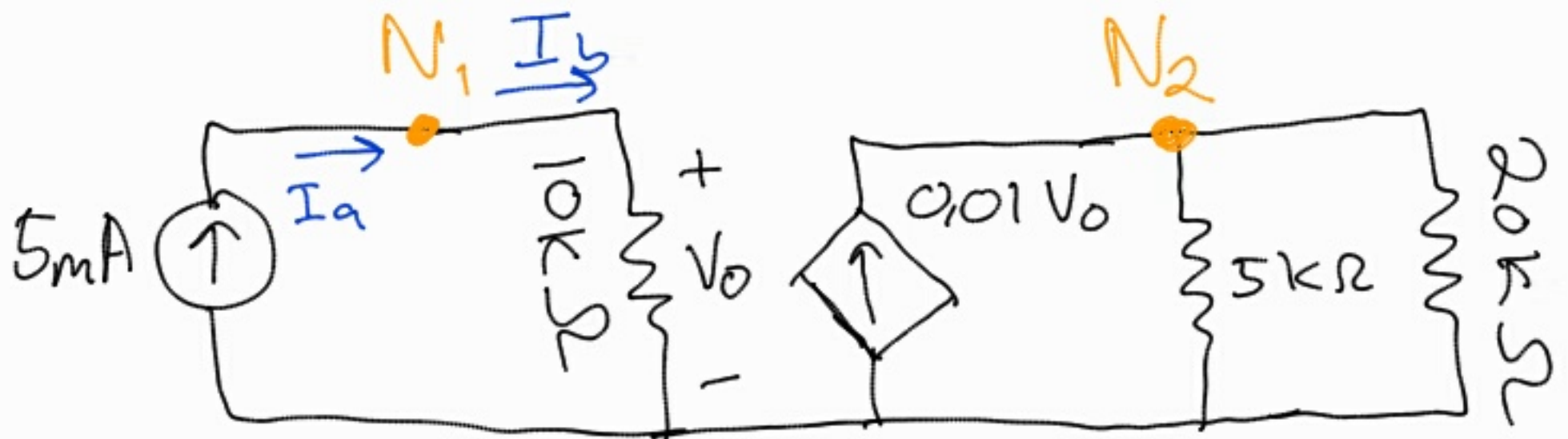

Apply KCL and Ohm's Law
at node 1, $\sum I = 0$, $I = \frac{V}{R}$

$$I_a - I_b = 0$$

$$5 \times 10^{-3} - \frac{V_0}{10 \times 10^3} = 0$$

$$-\frac{V_0}{10 \times 10^3} = -5 \times 10^{-3}$$

$$V_0 = (-5 \times 10^{-3})(-10 \times 10^3)$$

$$V_0 = 50 \text{ V}$$

Apply current division at node

$$2. \quad I_2 = \frac{I \cdot R_1}{R_1 + R_2}$$

$$I = \frac{0,01V_0 \times 5 \times 10^3}{5 \times 10^3 + 20 \times 10^3}$$

$$I = \frac{0,01 \times 50 \times 5 \times 10^3}{5 \times 10^3 + 20 \times 10^3}$$

$$I = 0,1 \text{ A}$$

$$I = 100 \text{ mA}$$

Ohm's Law

$$V = IR$$

$$V = 0,1 \times 20 \times 10^3$$

$$V = 2000 \text{ V}$$


$$V = 2 \text{ kV}$$

$$P = V \cdot I$$

$$P = 2000 \times 0.1$$

$$P = 200 \text{ W}$$

2,29

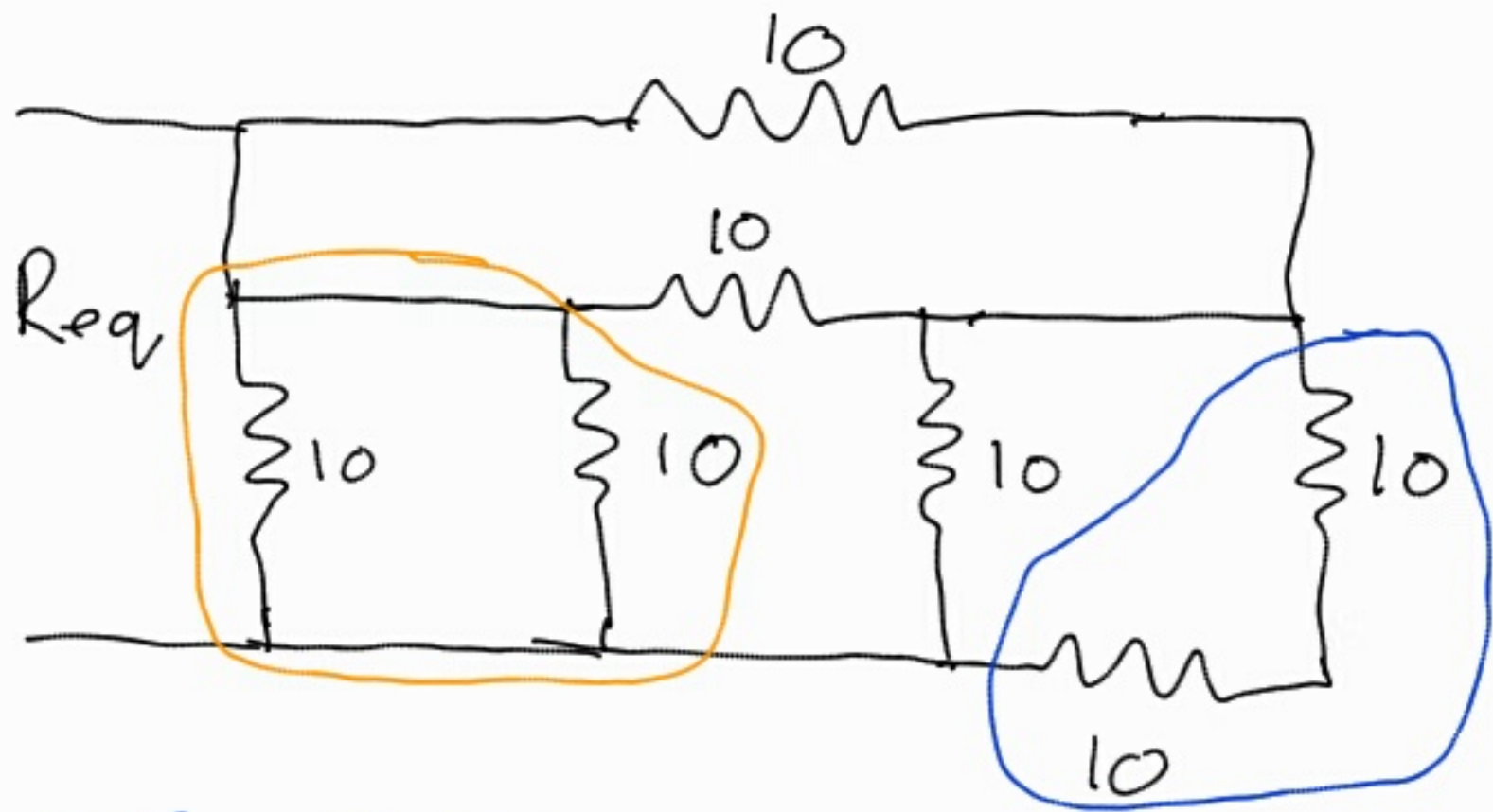

- Series


$$R_{eq} = R_1 + R_2$$

- Parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$10 + 10 = 20 \Omega$$


$$10 || 10 = \frac{10 \times 10}{10 + 10}$$
$$= 5 \Omega$$

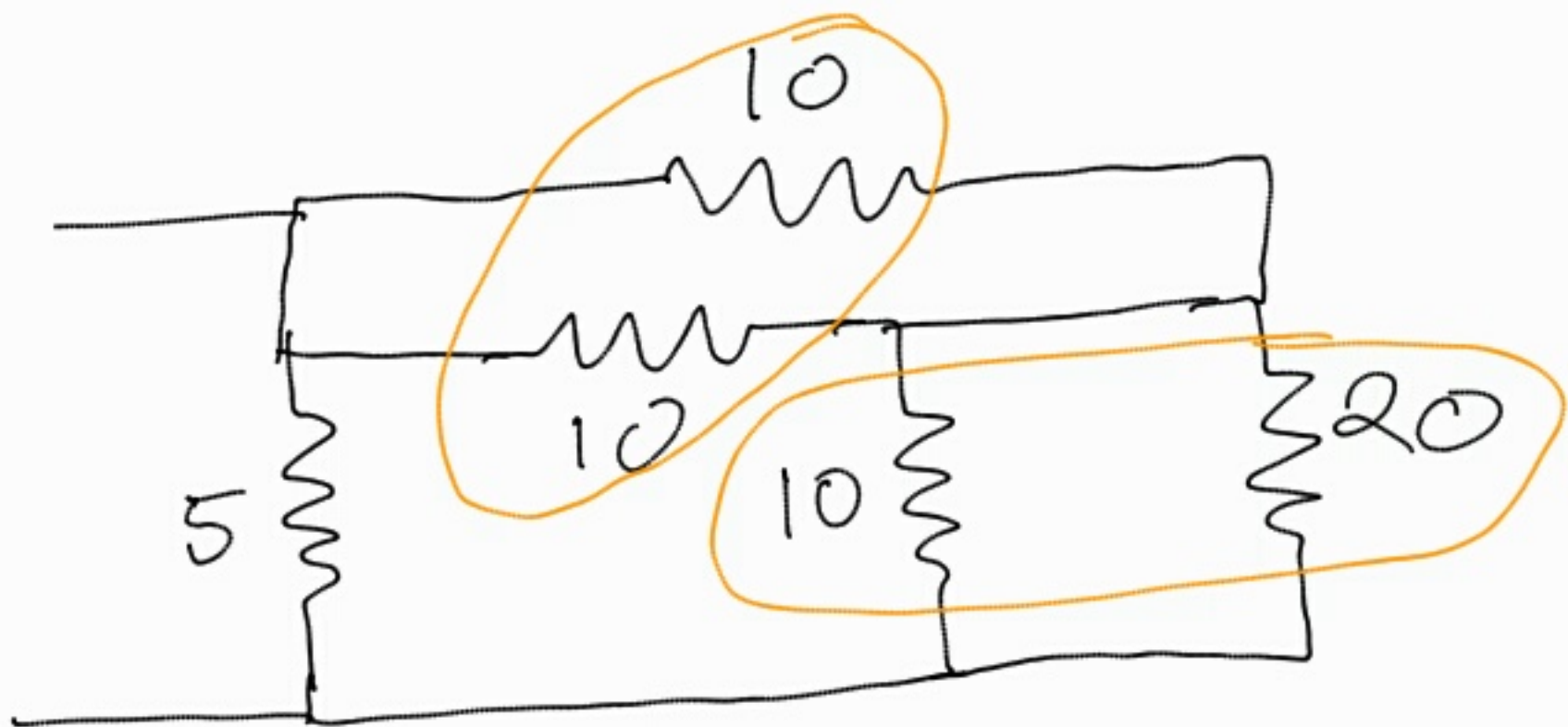


$$10 || 20 = \frac{10 \times 20}{10 + 20}$$

$$= \frac{20}{3} = 6,67 \Omega$$

$$10 || 10 = 5 \Omega$$

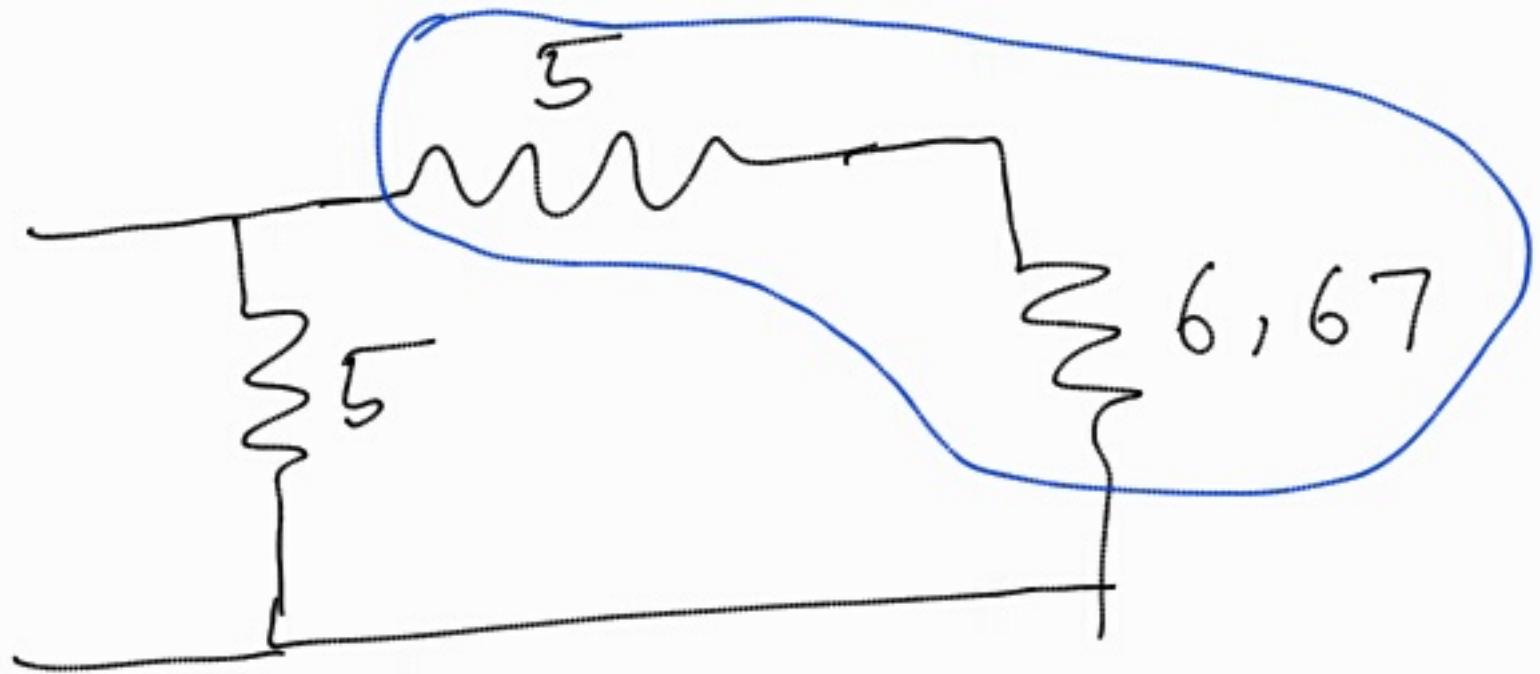


$$5 + 6,67 = 11,67 \Omega$$

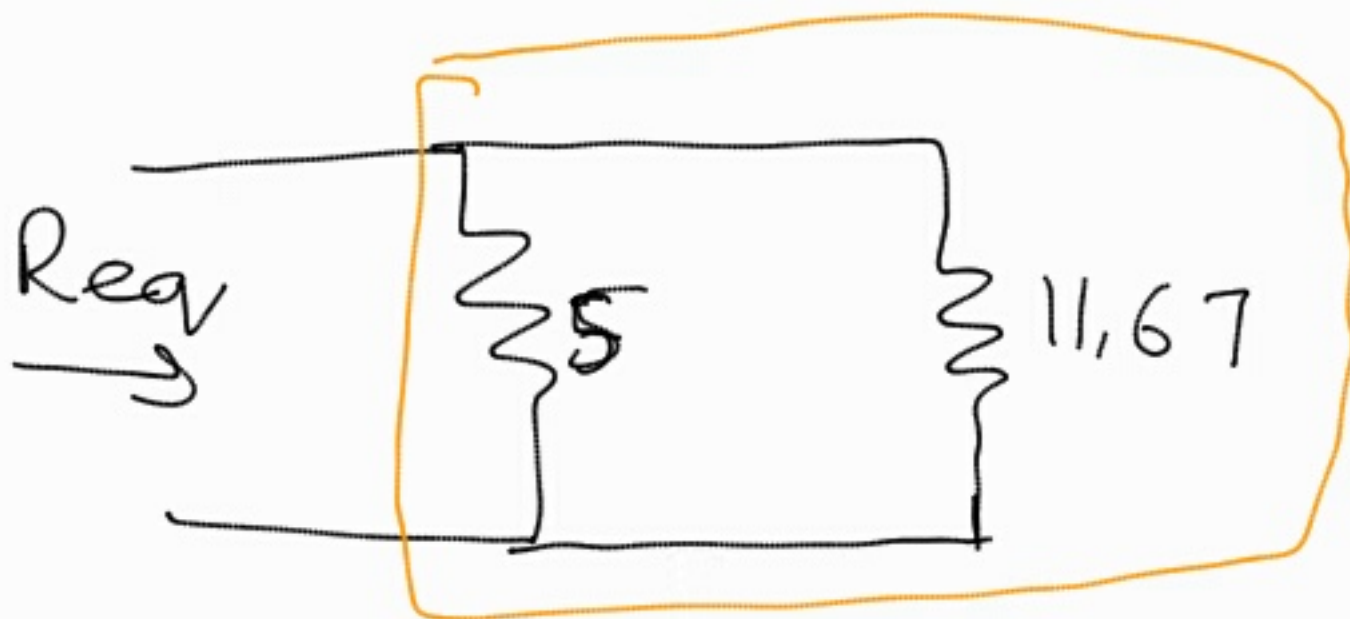

$$5 \parallel 11,67 = \frac{5 \times 11,67}{5 + 11,67}$$
$$= 3,50 \Omega$$

2,32

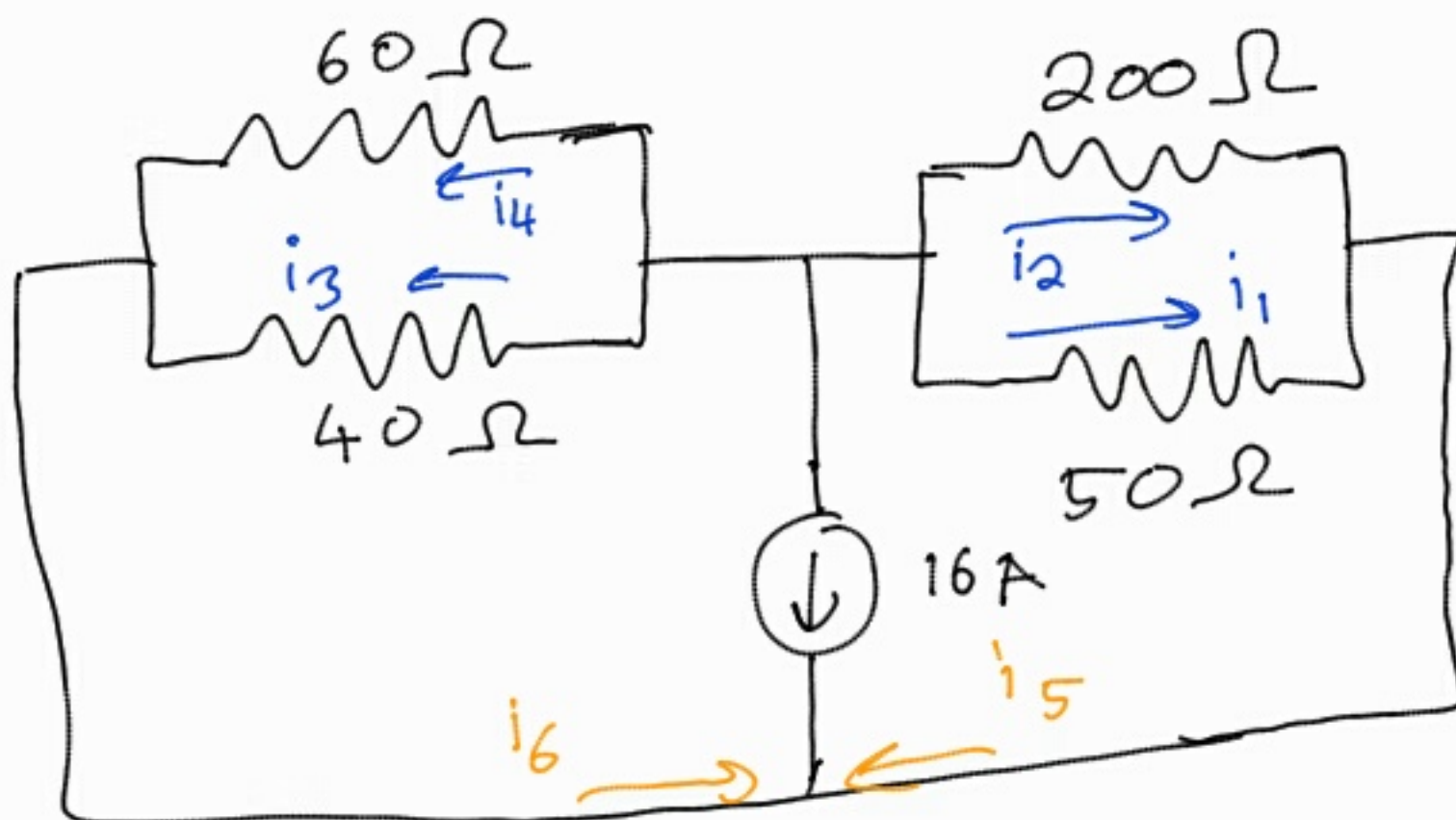

$$\begin{aligned} \text{let } R_a &= 60 \parallel 40 \\ &= \frac{40 \times 60}{60 + 40} \\ &= 24 \, \Omega \end{aligned}$$

$$\begin{aligned} R_b &= 200 \parallel 50 \\ &= \frac{200 \times 50}{200 + 50} \\ &= 40 \, \Omega \end{aligned}$$

Apply current division to find i_5 & i_6 .

- Note $16 + i_5 + i_6 = 0$

$$16 = -i_5 - i_6$$

i_5 & i_6 are negative

$$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

$$i_5 = -16 \times \frac{24}{24 + 40}$$

$$= -6 \text{ A}$$

$$i_6 = -16 \times \frac{40}{24 + 40}$$

$$= -10 \text{ A}$$


$$\begin{aligned}
 i_1 &= i_5 \times \frac{200}{200+50} \\
 &= -6 \times \frac{200}{200+50} \\
 &= -4.8 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 i_2 &= i_5 \times \frac{50}{200+50} \\
 &= -6 \times \frac{50}{200+50} \\
 &= -1.2 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 i_3 &= i_6 \times \frac{60}{40+60} \\
 &= -10 \times \frac{60}{40+60} \\
 &= -6 \text{ A}
 \end{aligned}$$

$$\begin{aligned}
 i_4 &= i_6 \times \frac{40}{40+60} \\
 &= -10 \times \frac{40}{40+60} \\
 &= -4 \text{ A}
 \end{aligned}$$

2.45

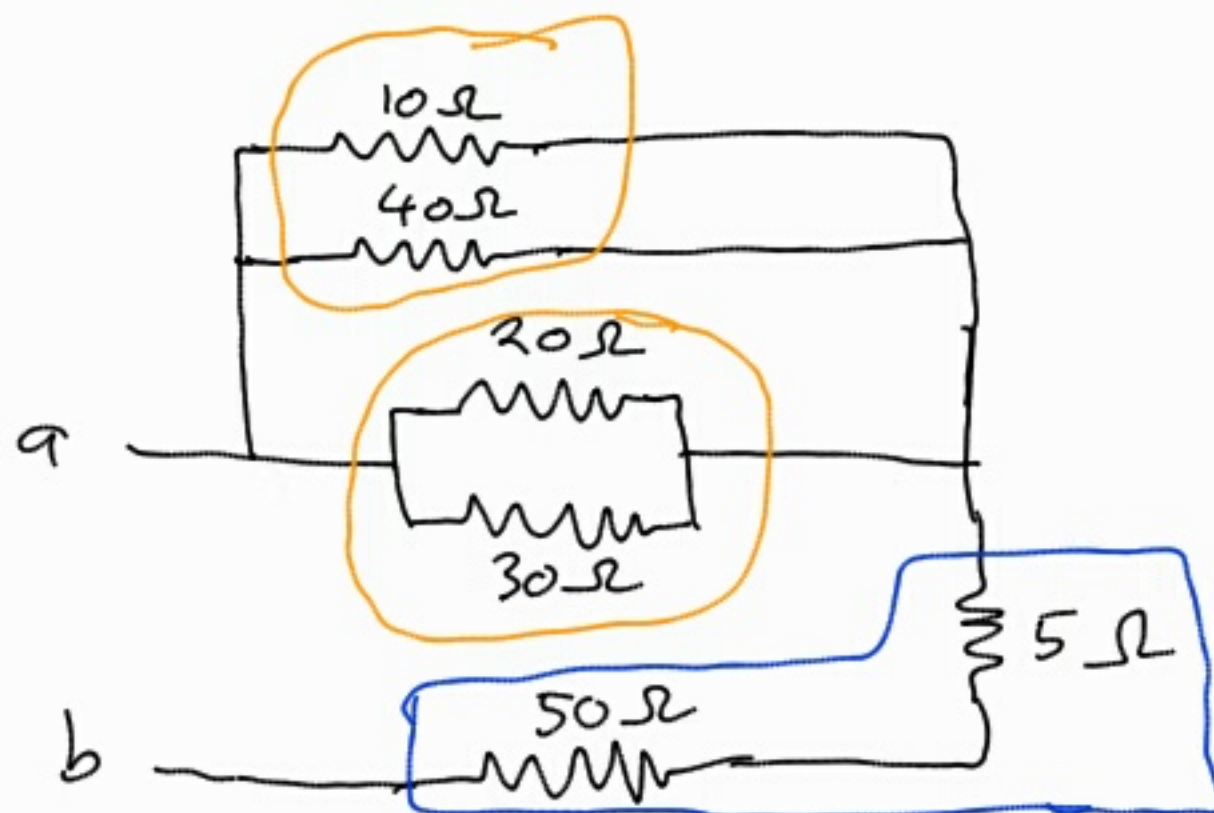

- Series

$$R_{eq} = R_1 + R_2$$

- Parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


$$10 || 40 = \frac{10 \times 40}{10 + 40}$$

$$= 8 \Omega$$

$$20 || 30 = \frac{20 \times 30}{20 + 30}$$


$$= 12$$

$$5 + 50 = 55 \Omega$$

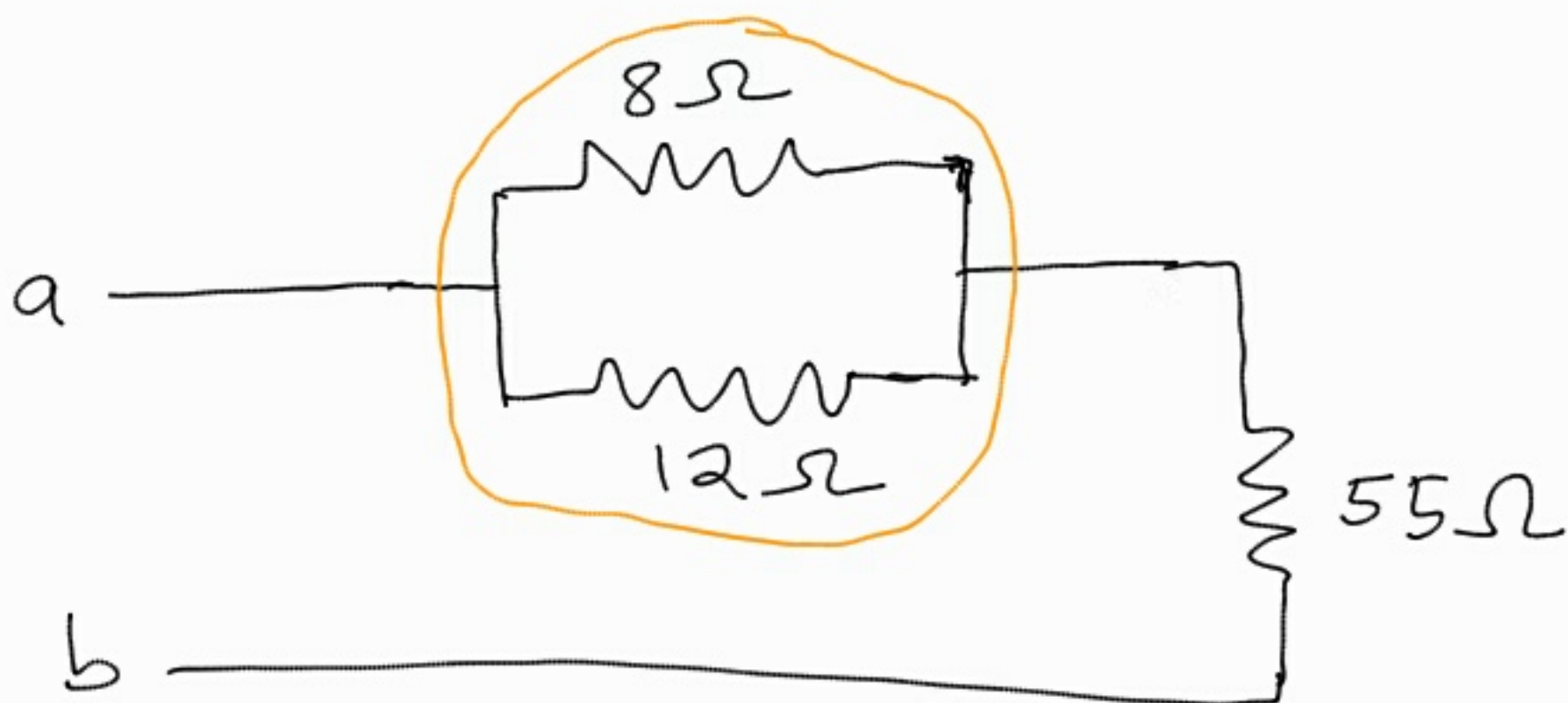


$$8 \parallel 12 = \frac{8 \times 12}{8 + 12}$$

$$= 4.8\Omega$$

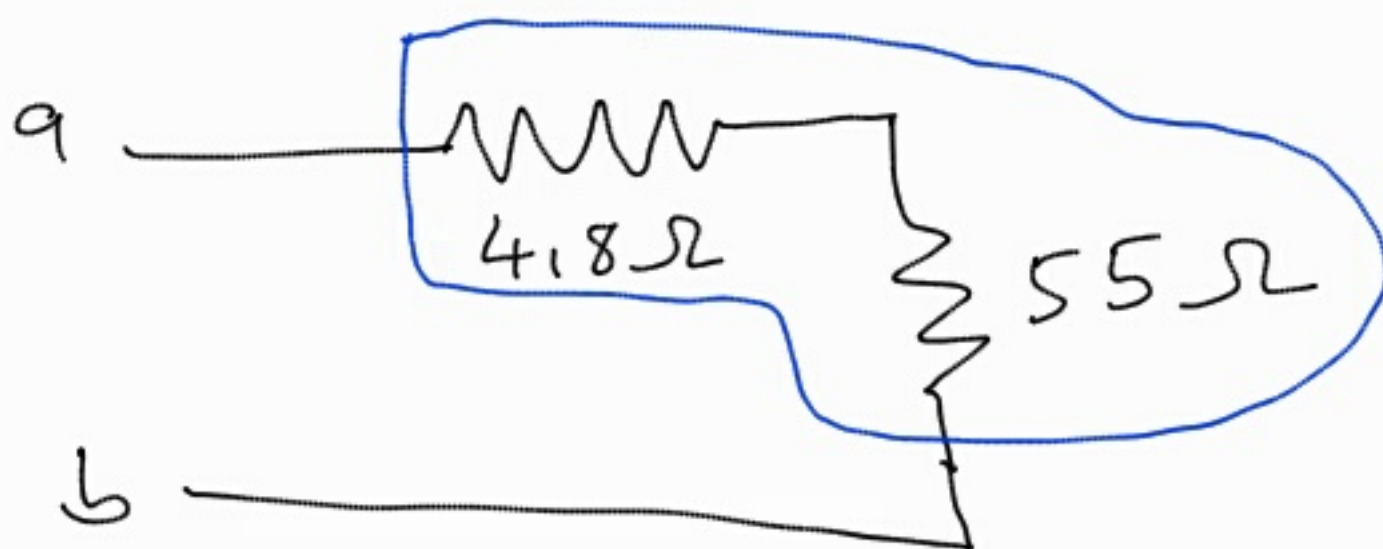


$$4.8 + 55 = 59.8\Omega$$

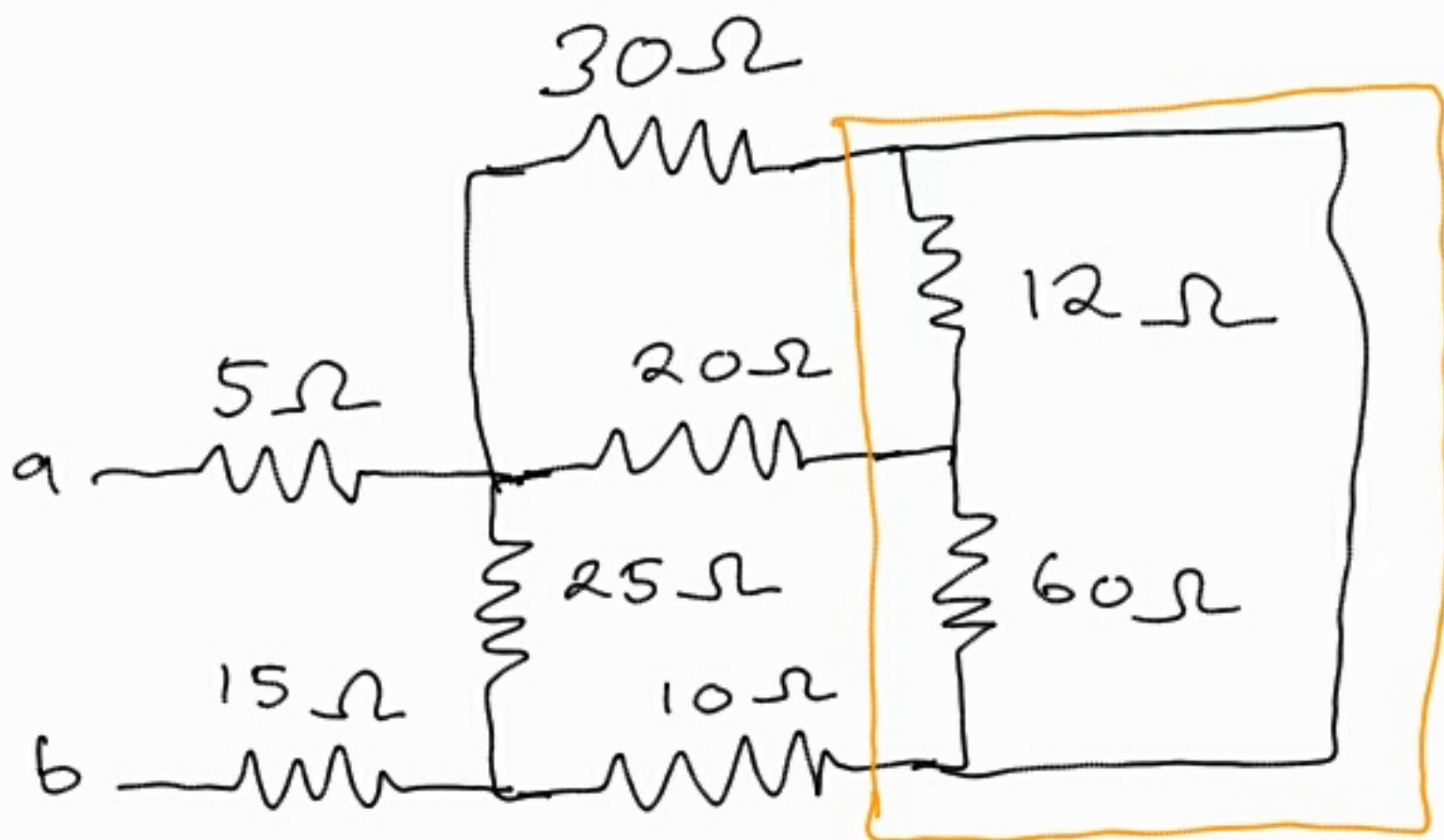

$$12 || 60 = \frac{12 \times 60}{12 + 60}$$


$$= 10\Omega$$

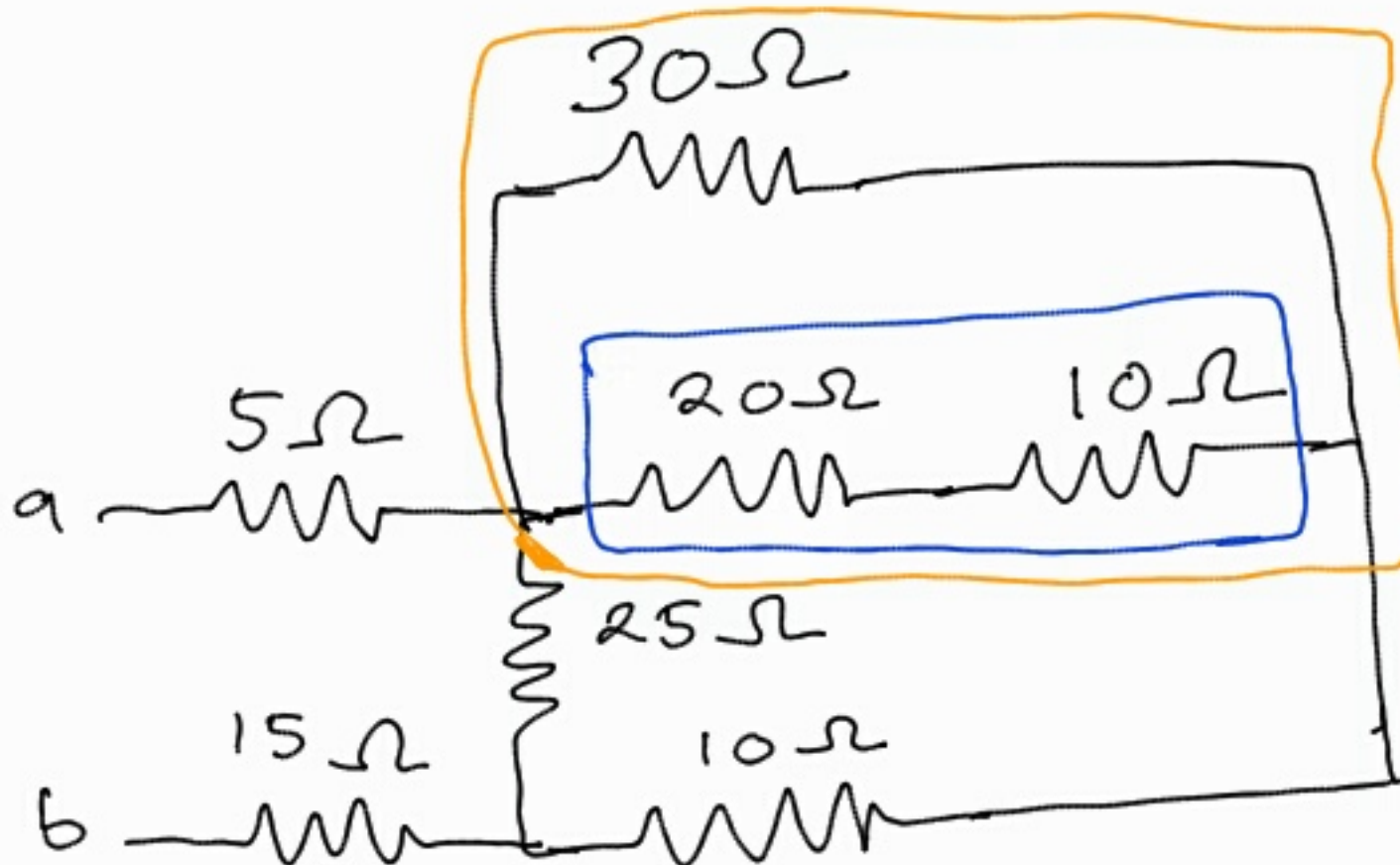

$$10 + 20 = 30 \Omega$$

$$30 || 30 = \frac{30 \times 30}{30 + 30}$$


$$= 15 \Omega$$

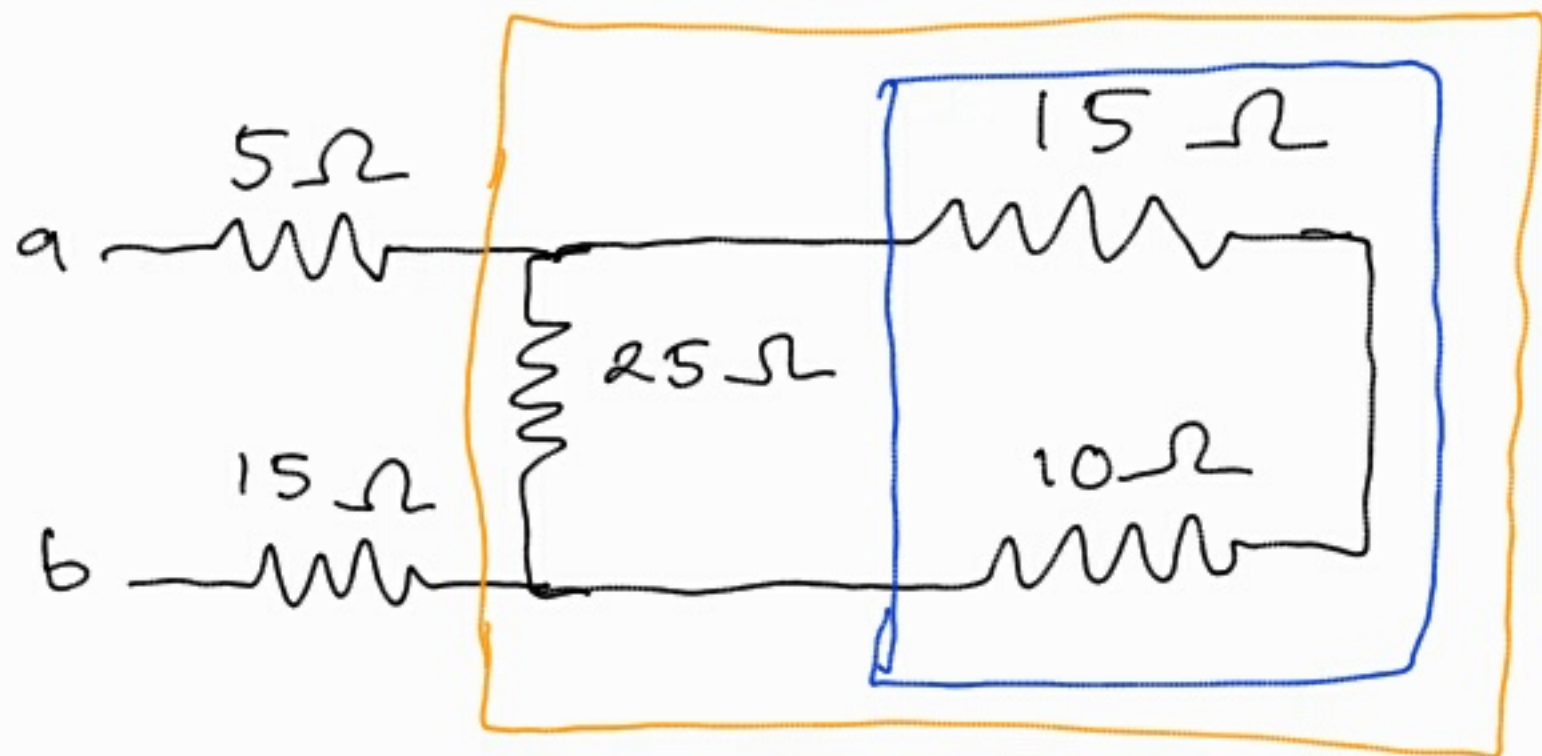

$$10 + 15 = 25 \Omega$$


$$25 || 25 = \frac{25 \times 25}{25 + 25}$$

$$= 12,5 \Omega$$

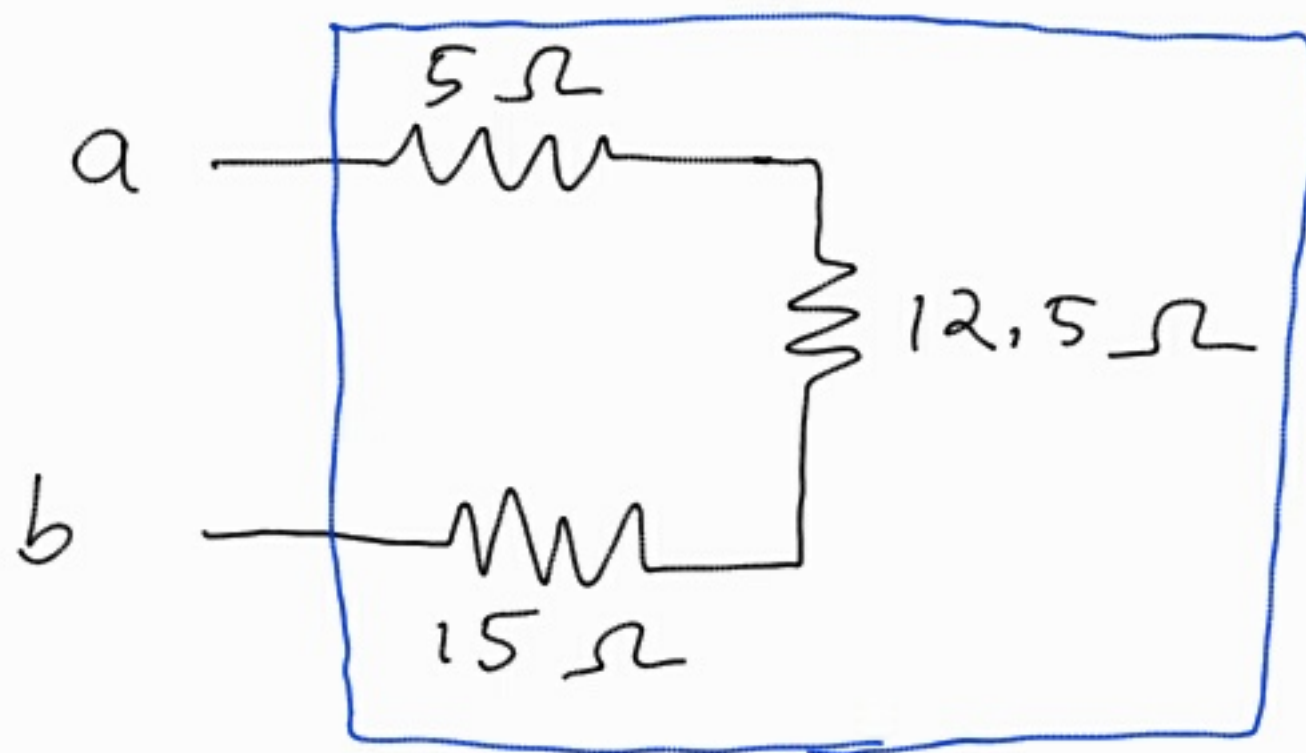

$$\begin{aligned} R_{eq} &= 5 + 12,5 + 15 \\ &= 32,5\ \Omega \end{aligned}$$

2,51

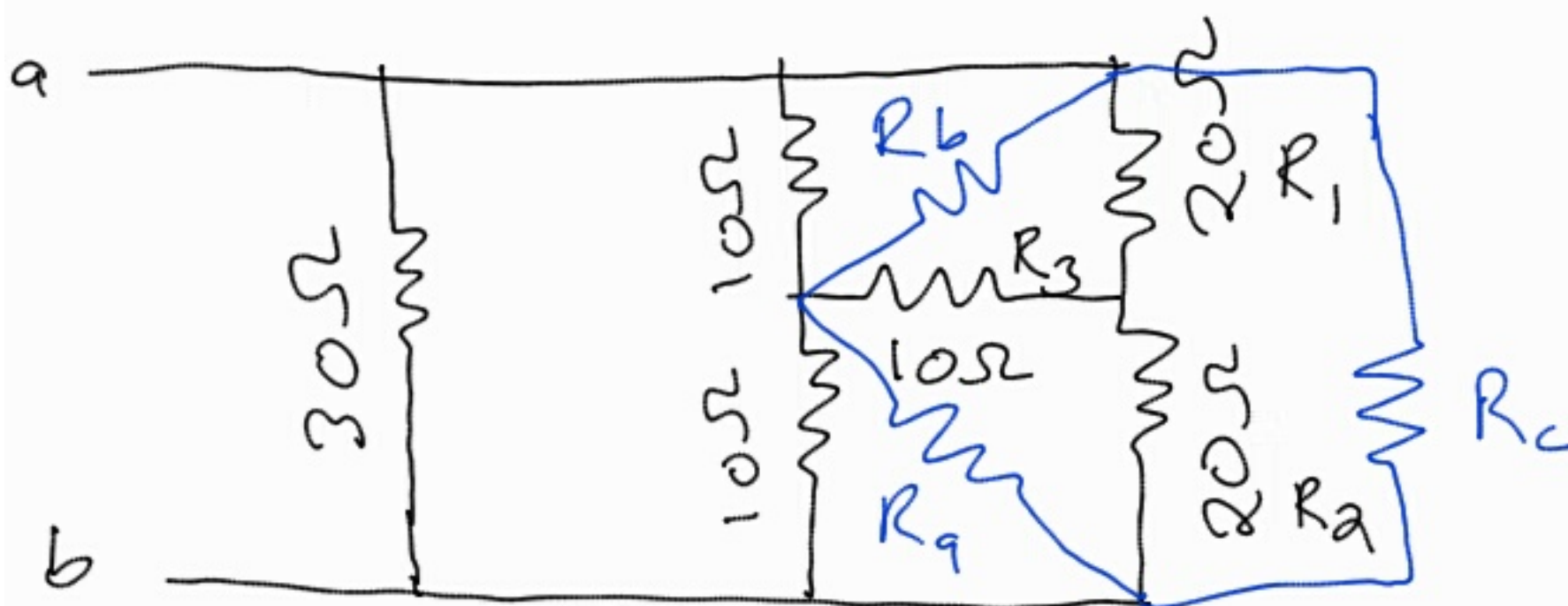


$$\begin{aligned}
 S &= R_1 R_2 + R_2 R_3 + R_3 R_1 \\
 &= 20 \times 20 + 20 \times 10 + 10 \times 20 \\
 &= 800 \Omega
 \end{aligned}$$

$$R_a = \frac{S}{R_1} = \frac{800}{20} = 40 \Omega$$

$$R_b = \frac{S}{R_2} = \frac{800}{20} = 40 \Omega$$
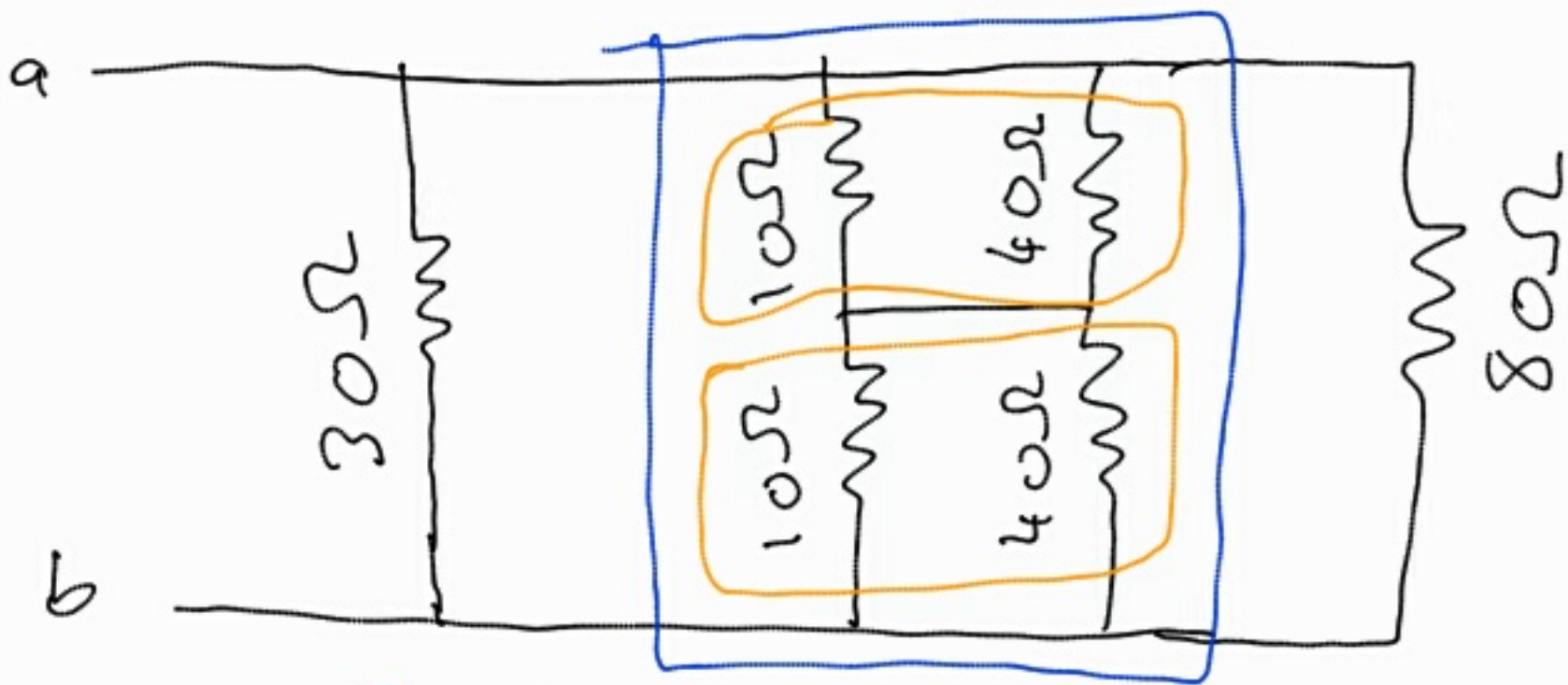
$$R_c = \frac{S}{R_3} = \frac{800}{10} = 80 \Omega$$



- Series

$$R_{eq} = R_1 + R_2$$


- Parallel

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$10 || 40 = \frac{10 \times 40}{10 + 40}$$

$$= 8 \Omega$$

$$8 + 8 = 16 \Omega$$

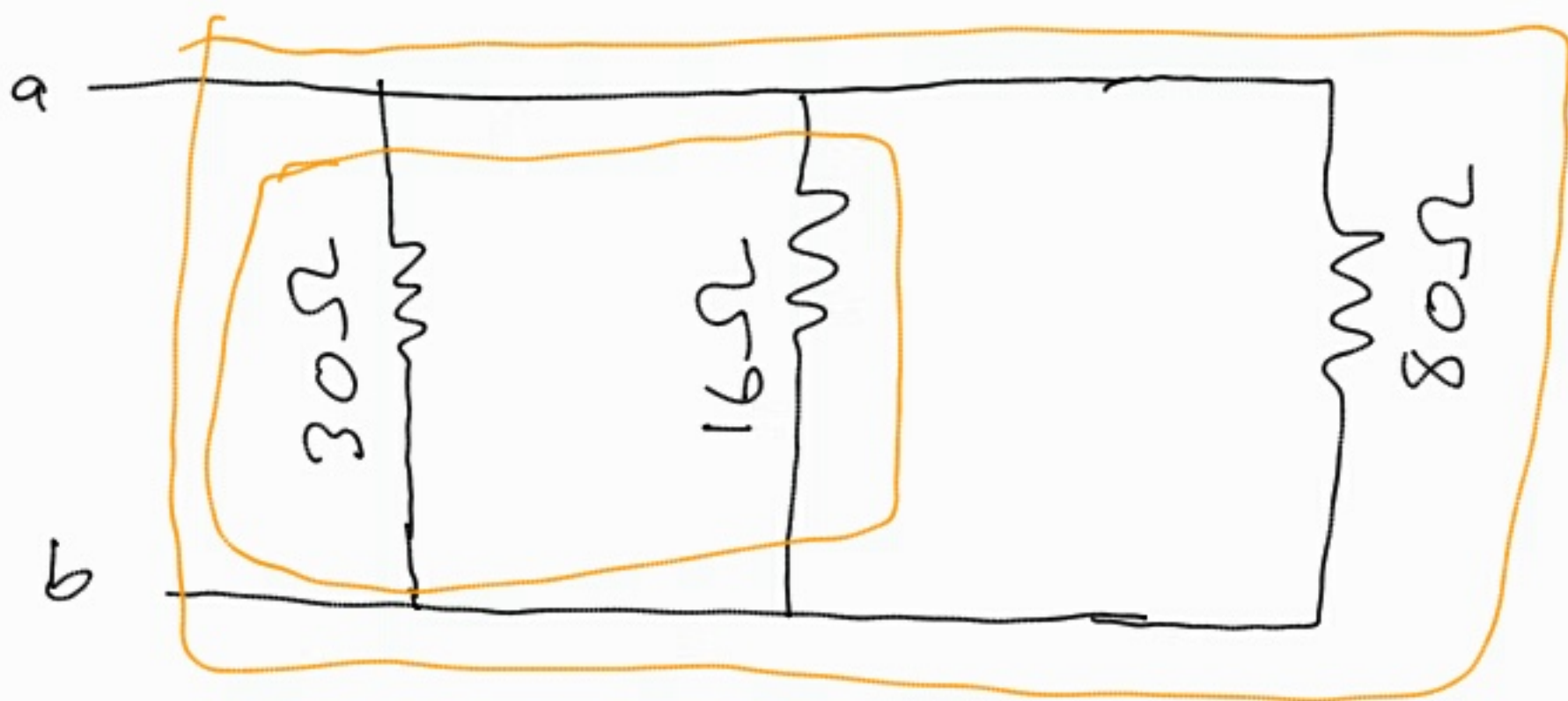


$$16 \parallel 30 = \frac{16 \times 30}{16 + 30}$$


$$= 10,4348\Omega$$

$$10,4348 \parallel 80 = \frac{10,4348 \times 80}{10,4348 + 80}$$

$$R_{eq} = 9,231\Omega$$

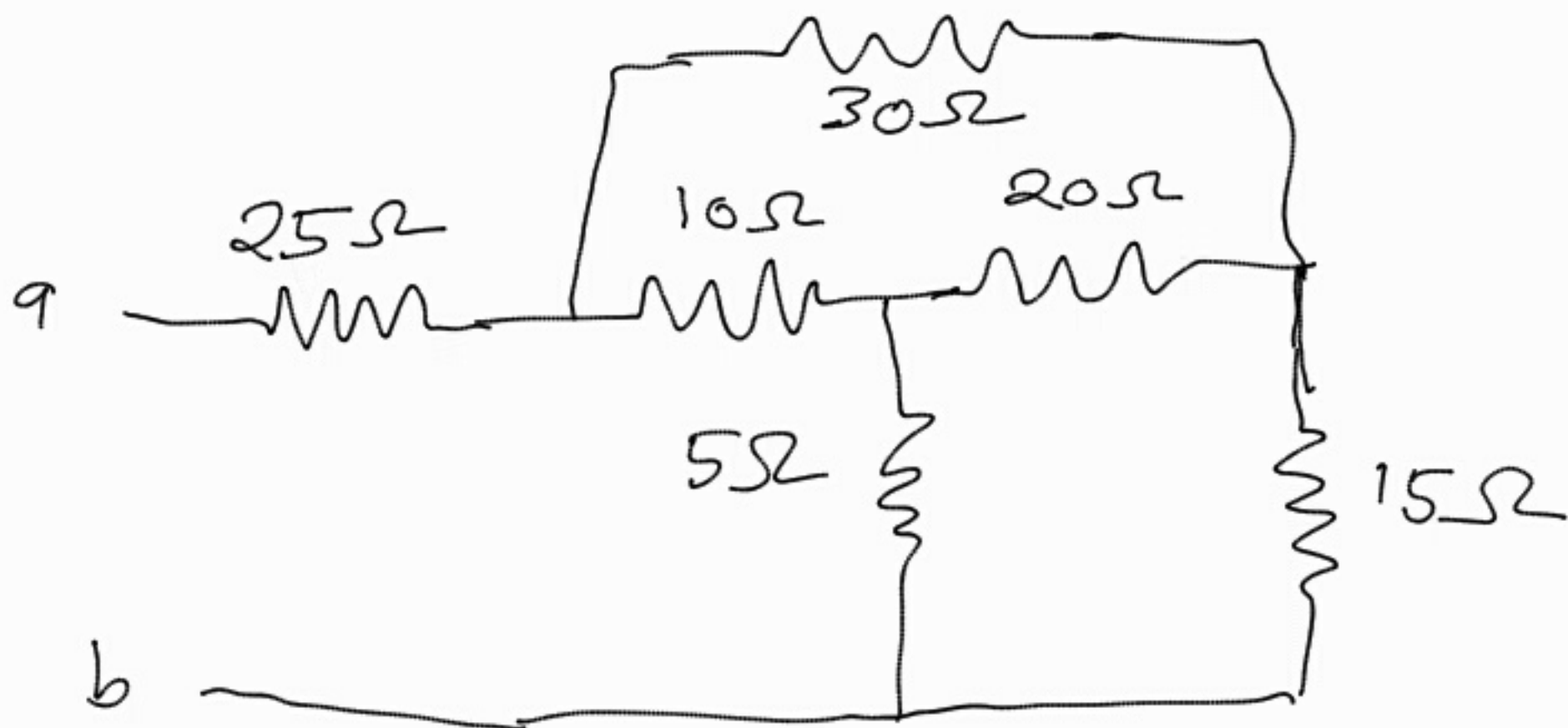

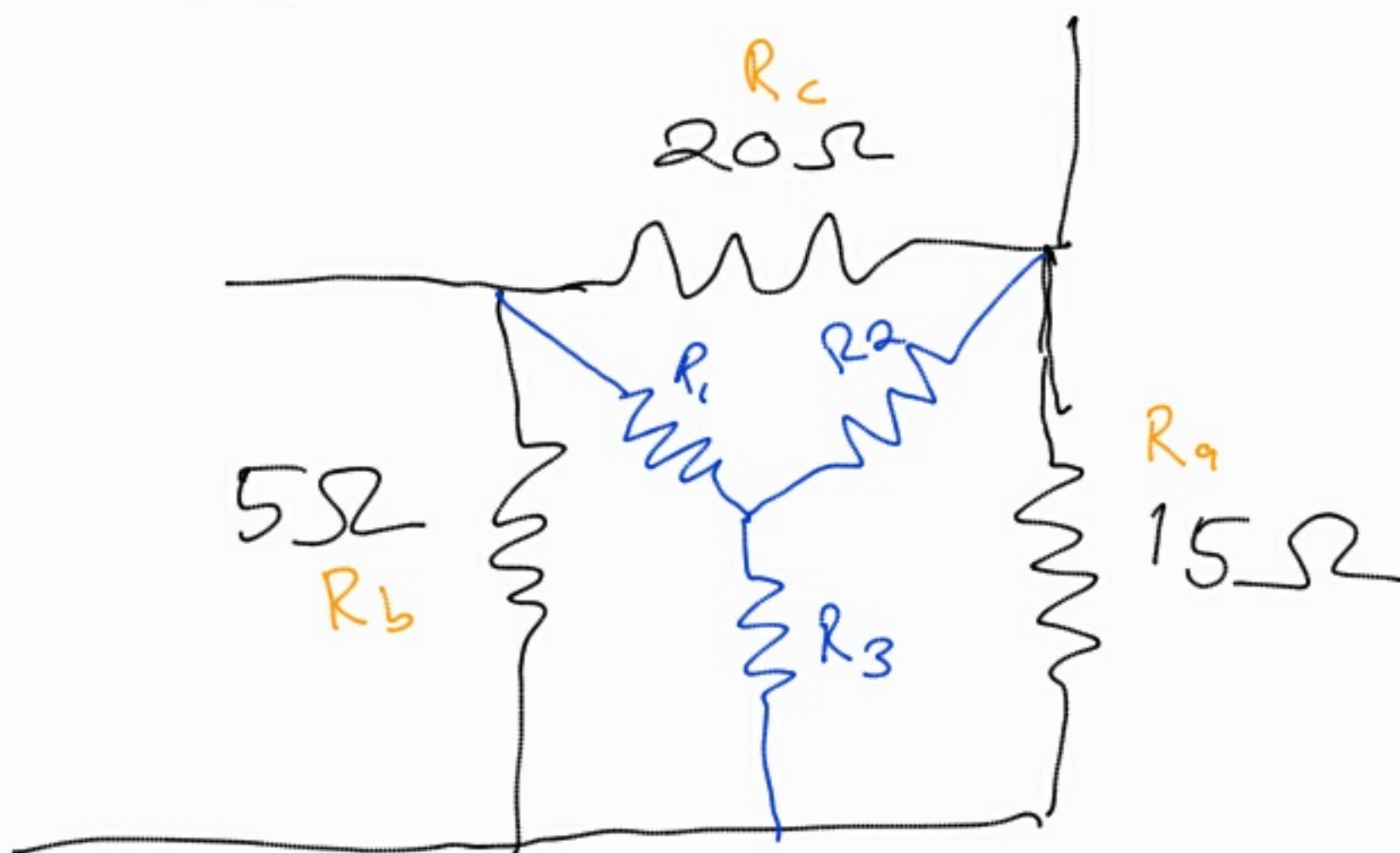- There are no parallel or series resistors
- Apply $\Delta \rightarrow Y$ transform



$$R_a = 15 \Omega, R_b = 5 \Omega, R_c = 20 \Omega$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$= \frac{5 \times 20}{15 + 5 + 20}$$

$$= 2.5 \Omega$$

$$R_2 = \frac{R_c R_a}{R_a + 5 + 20}$$


$$= \frac{20 \times 15}{15 + 5 + 20}$$

$$= 7.5 \Omega$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$


$$= \frac{15 \times 5}{15 + 5 + 20}$$

$$= 1.875 \Omega$$

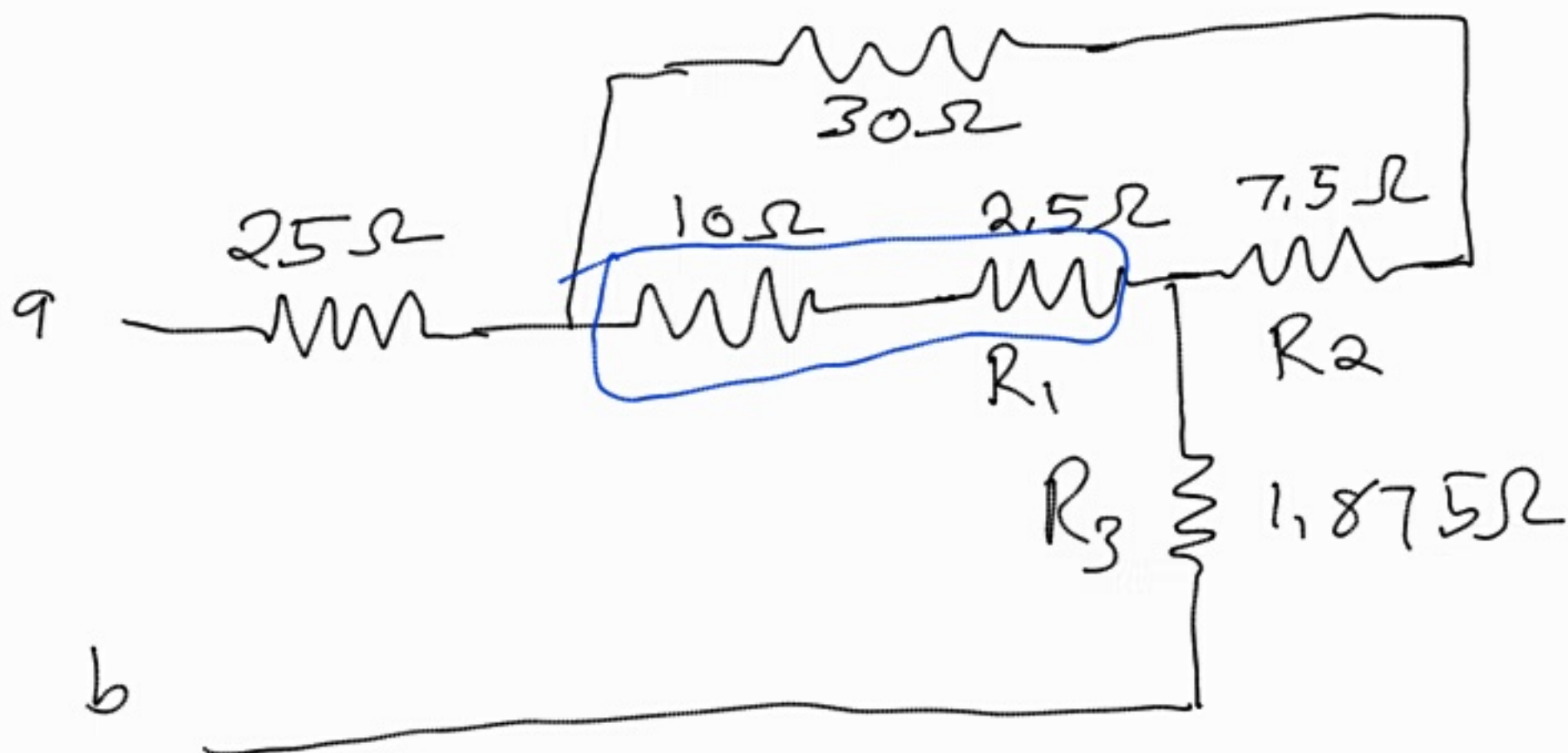

$$10 + 2.5\Omega = 12.5\Omega$$

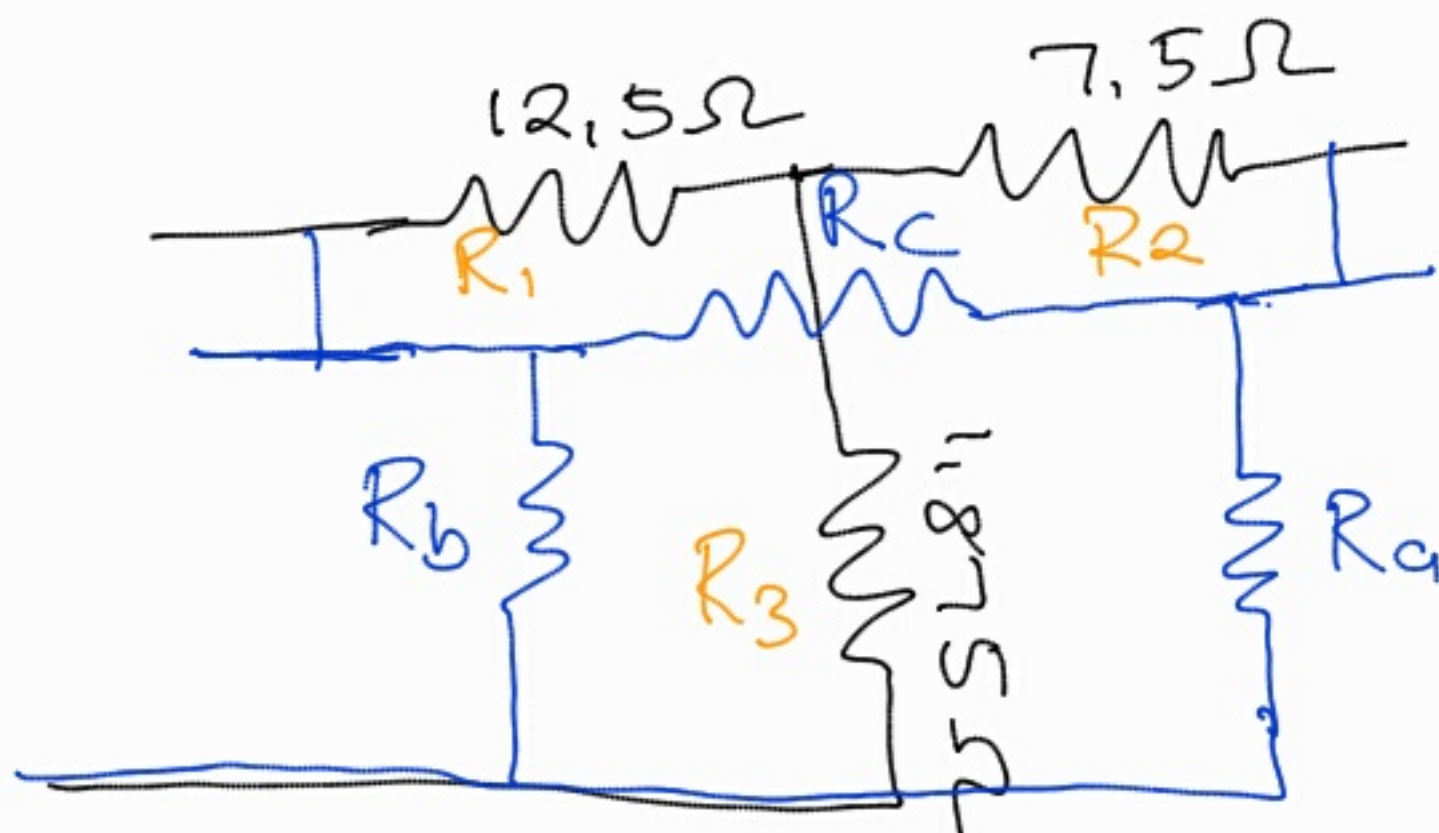Apply $\gamma \rightarrow \Delta$ transform



$$S = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$= 12,5 \times 7,5 + 7,5 \times 1,875 + 1,875 \times 12,5$$

$$= 131,25$$

$$R_a = \frac{S}{R_1}$$

$$= \frac{131,25}{12,5}$$

$$= 10,5 \, \Omega$$

$$R_b = \frac{S}{R_2}$$


$$= \frac{131,25}{7,5}$$

$$= 17,5 \, \Omega$$

$$R_c = \frac{S}{R_3}$$


$$= \frac{131,25}{1,875}$$

$$= 70 \, \Omega$$

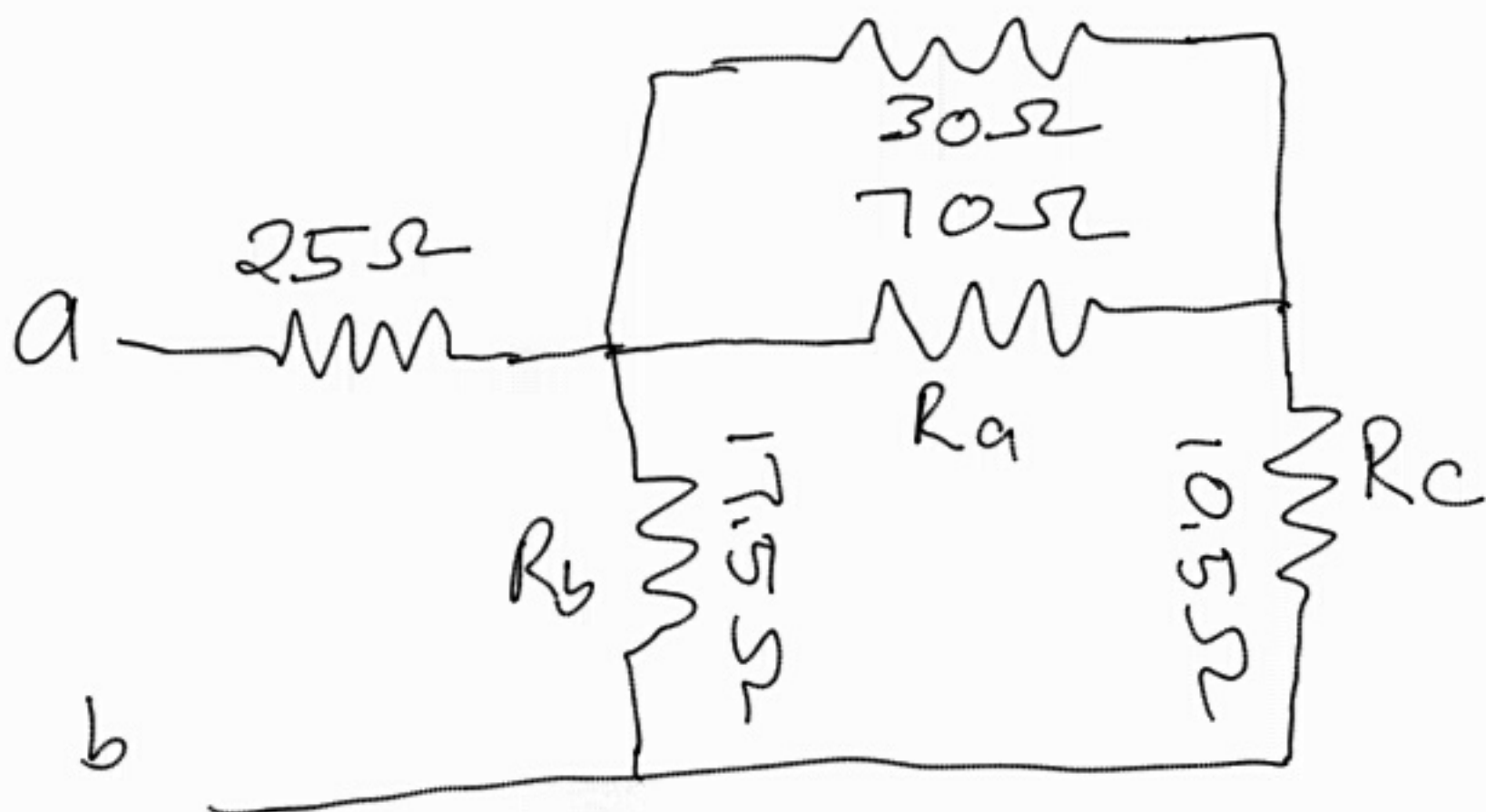

$$30 \parallel 70 = \frac{30 \times 70}{30 + 70}$$


$$= 21 \Omega$$

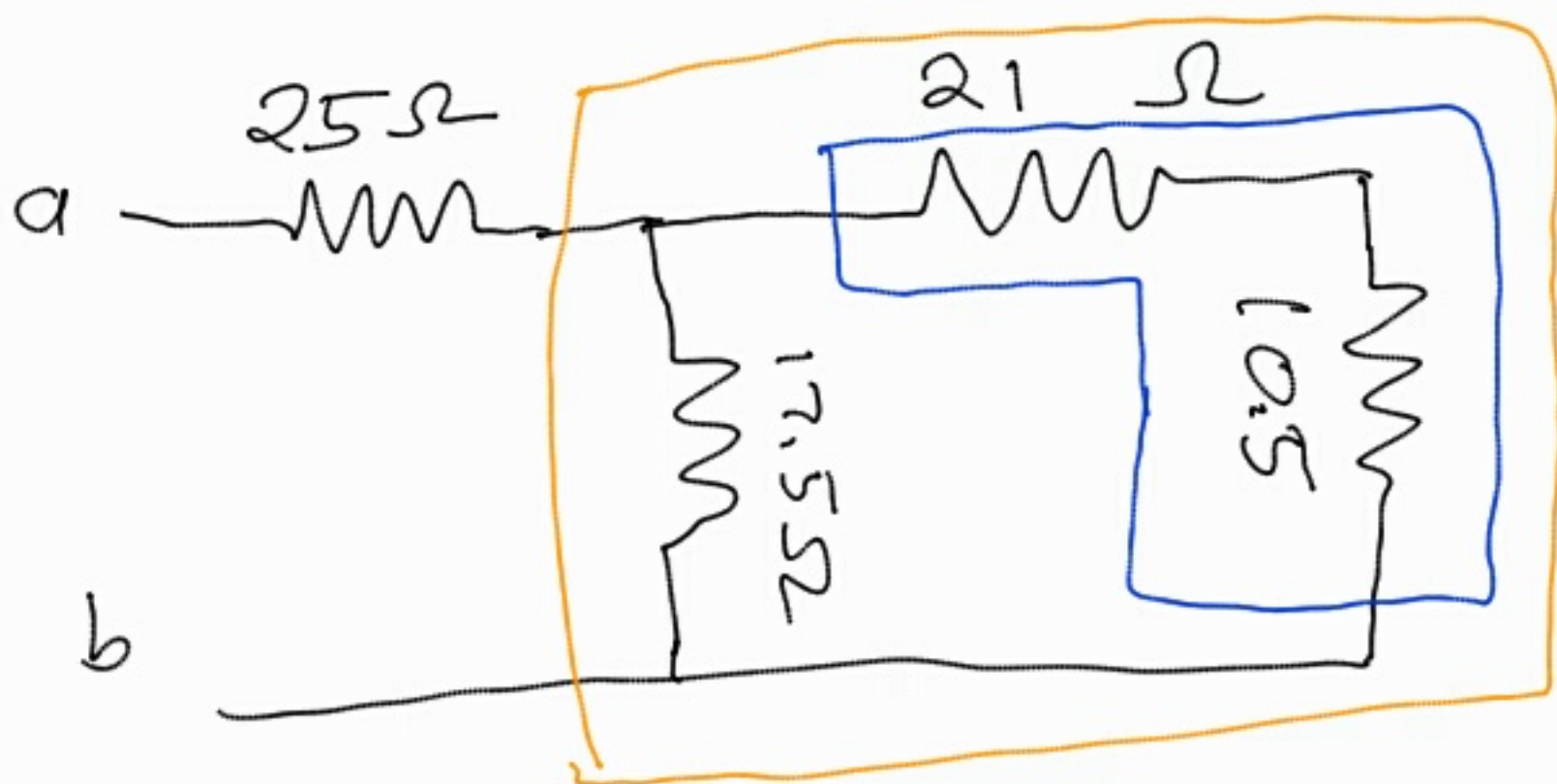

$$21 + 10.5 = 31.5$$

$$31.5 \parallel 17.5 = \frac{31.5 \times 17.5}{31.5 + 17.5}$$


$$= 11.25 \Omega$$

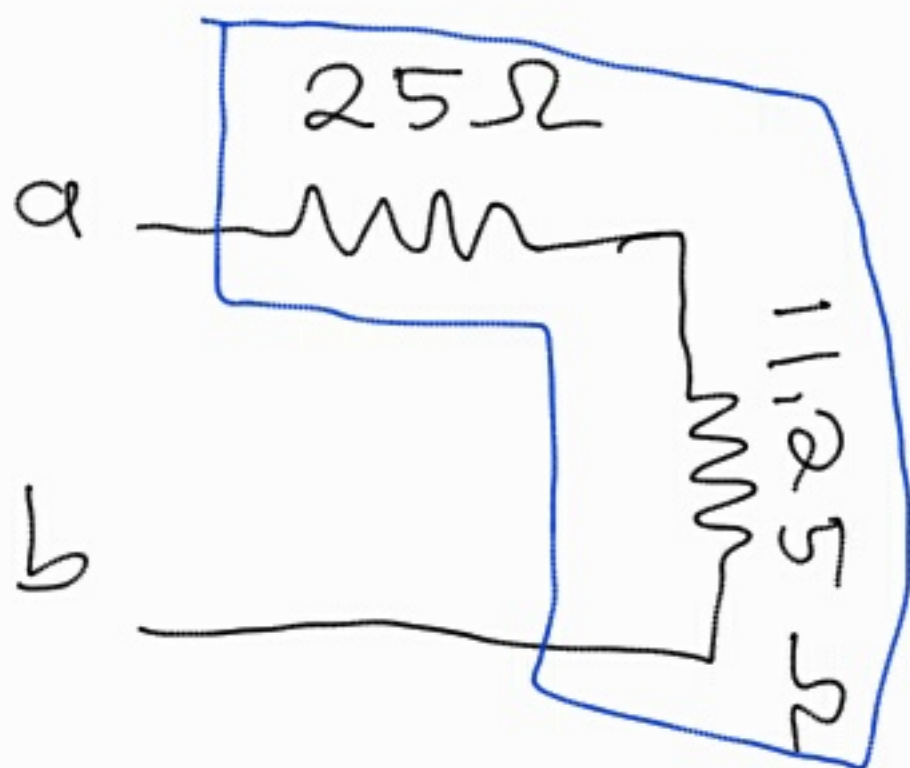

$$R_{eq} = 25 + 11.25$$

$$= 36.25 \Omega$$

2.53

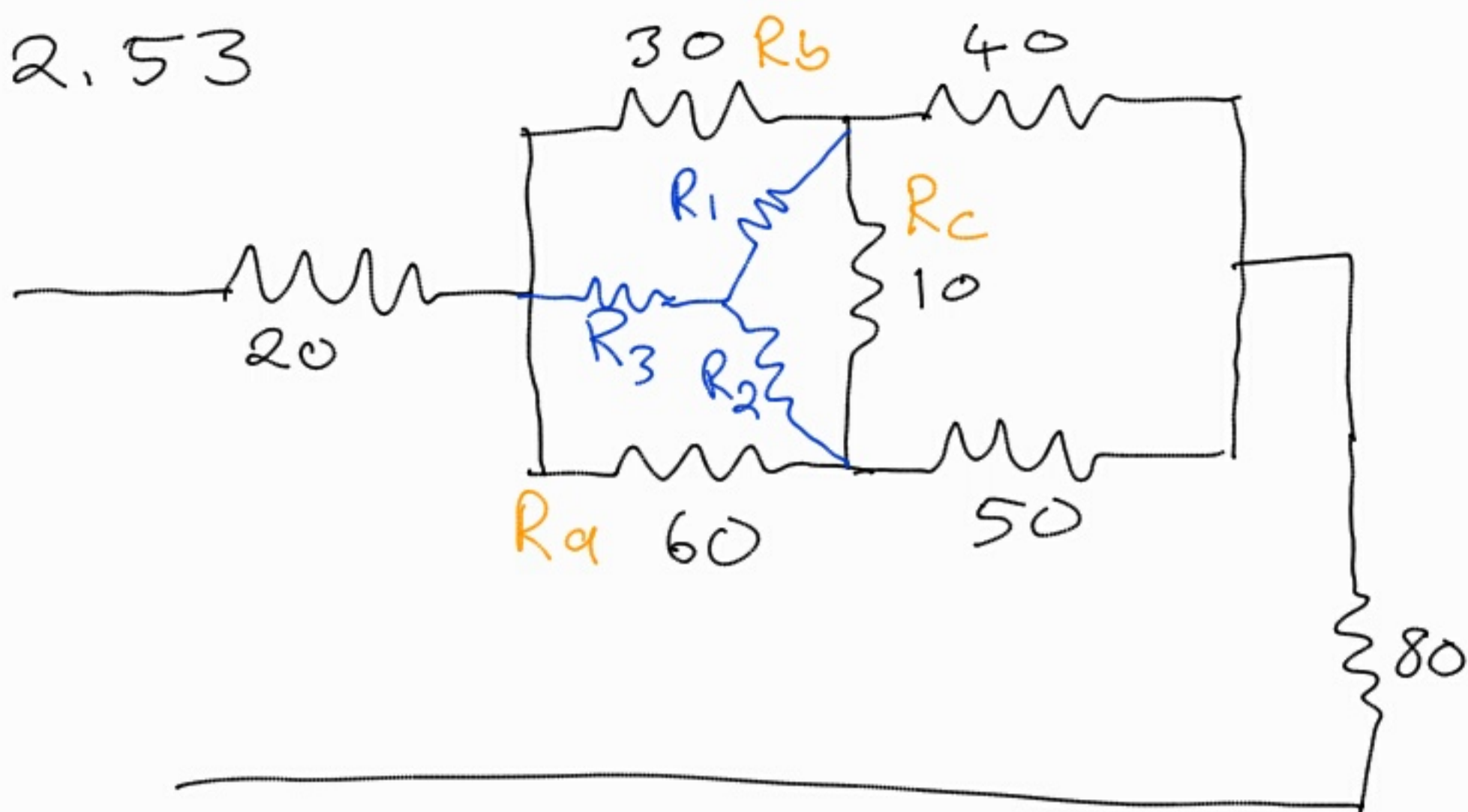

$$S = R_a + R_b + R_c$$


$$= 60 + 30 + 10$$

$$= 100 \Omega$$

$$R_1 = \frac{R_b R_c}{S} = \frac{30 \times 10}{100} = 3 \Omega$$

$$R_2 = \frac{R_c R_a}{S} = \frac{10 \times 60}{100} = 6 \Omega$$
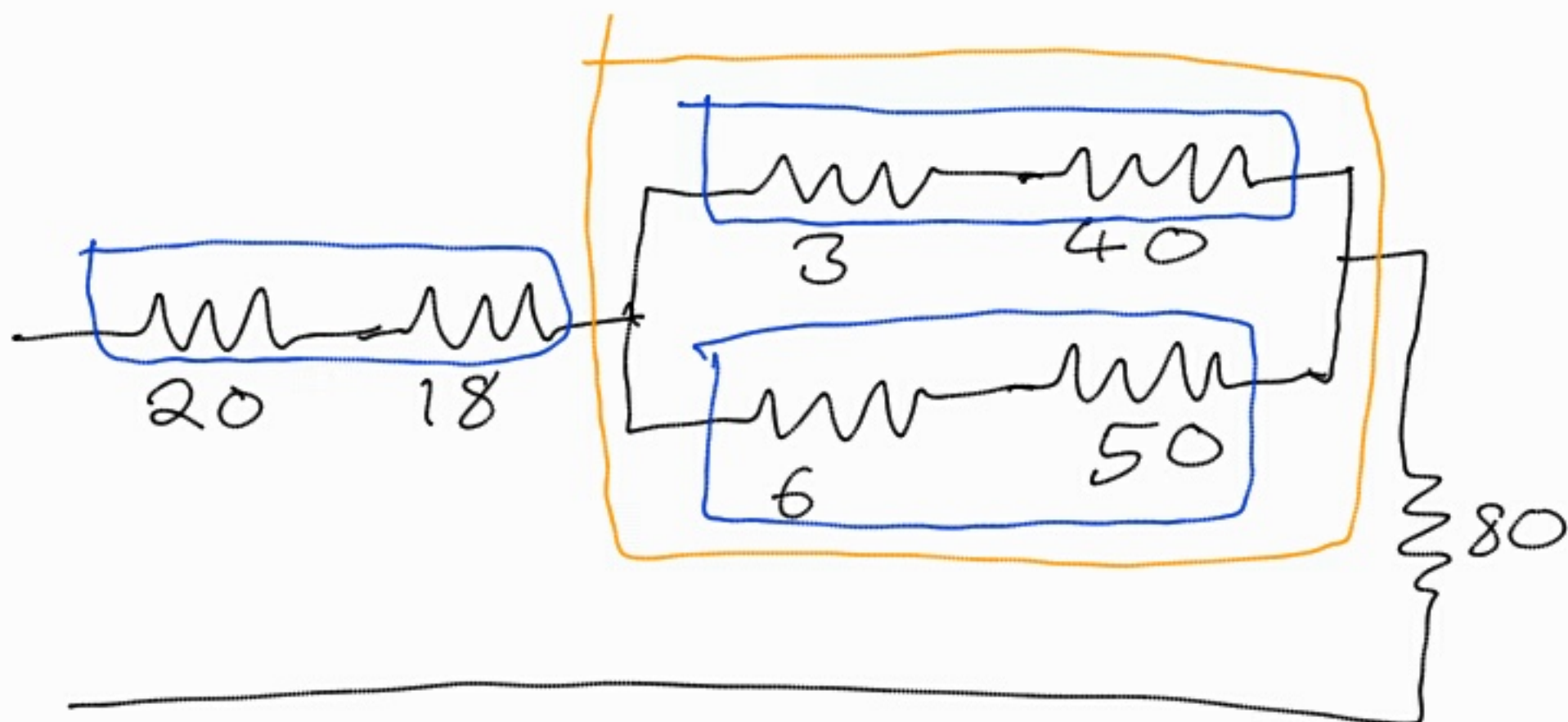
$$R_3 = \frac{R_a R_b}{S} = \frac{60 \times 30}{100} = 18 \Omega$$




$$20 + 18 = 38 \Omega$$

$$3 + 40 = 43 \Omega$$


$$6 + 50 = 56 \Omega$$

$$43 || 56 = \frac{43 \times 56}{43 + 56}$$

$$= 24,232 \Omega$$

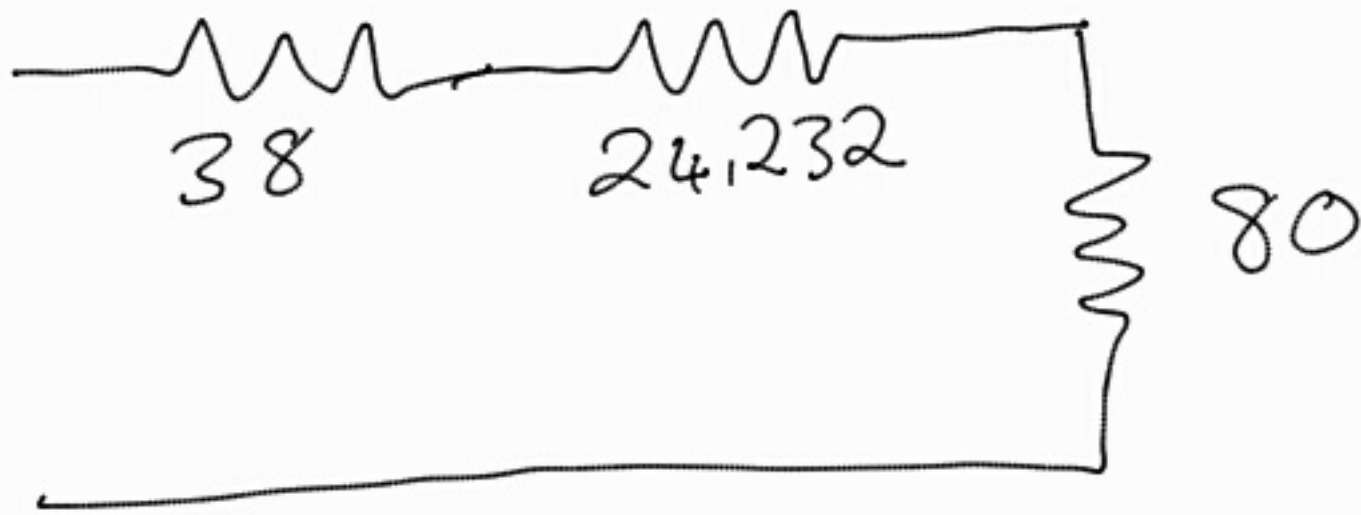

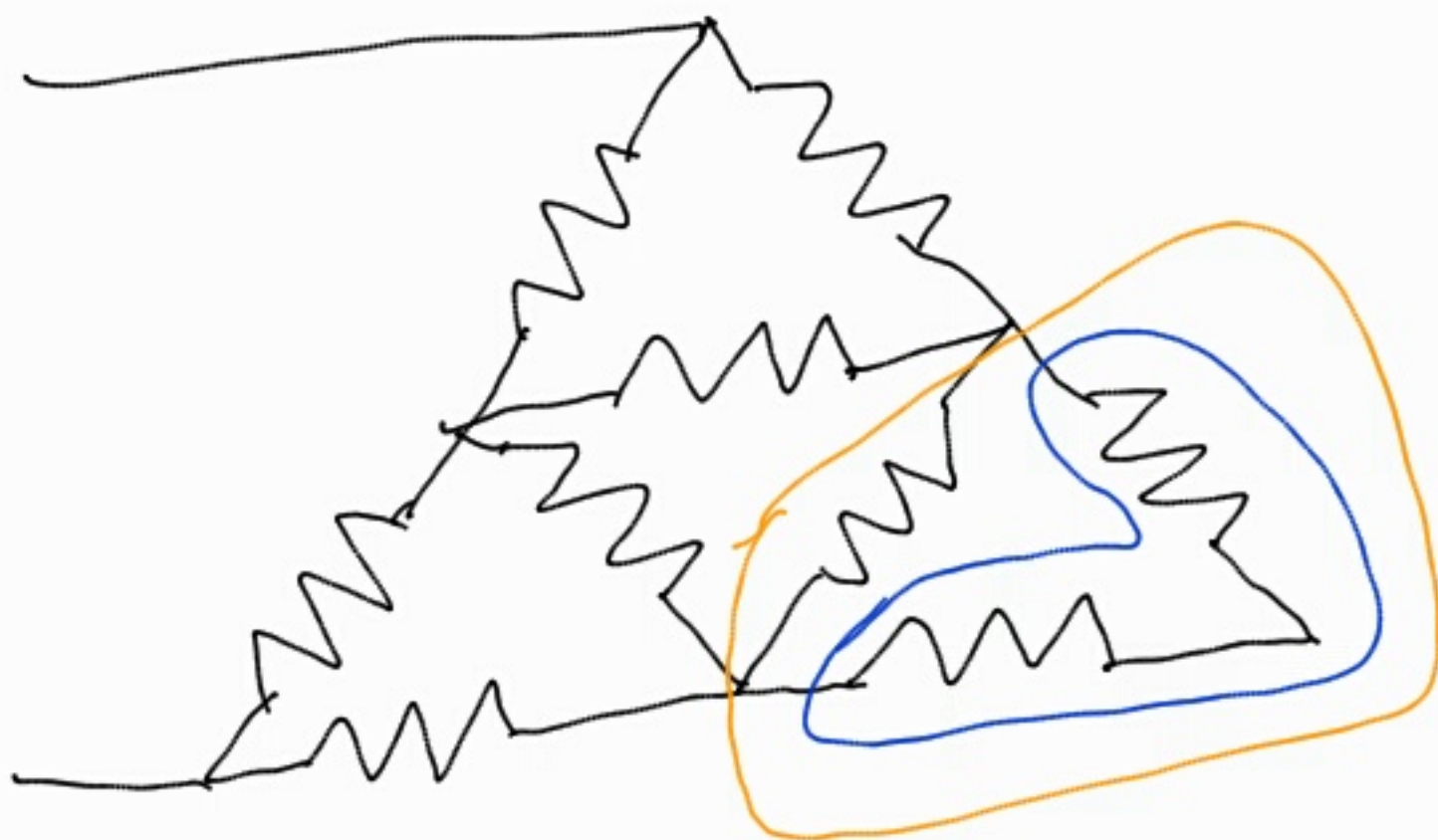
$$R_{eq} = 38 + 24,232 + 80$$
$$= 142,323 \, \Omega$$



$$30 + 30 = 60 \Omega$$

$$30 \parallel 60 = \frac{30 \times 60}{30 + 60}$$


$$= 20 \Omega$$

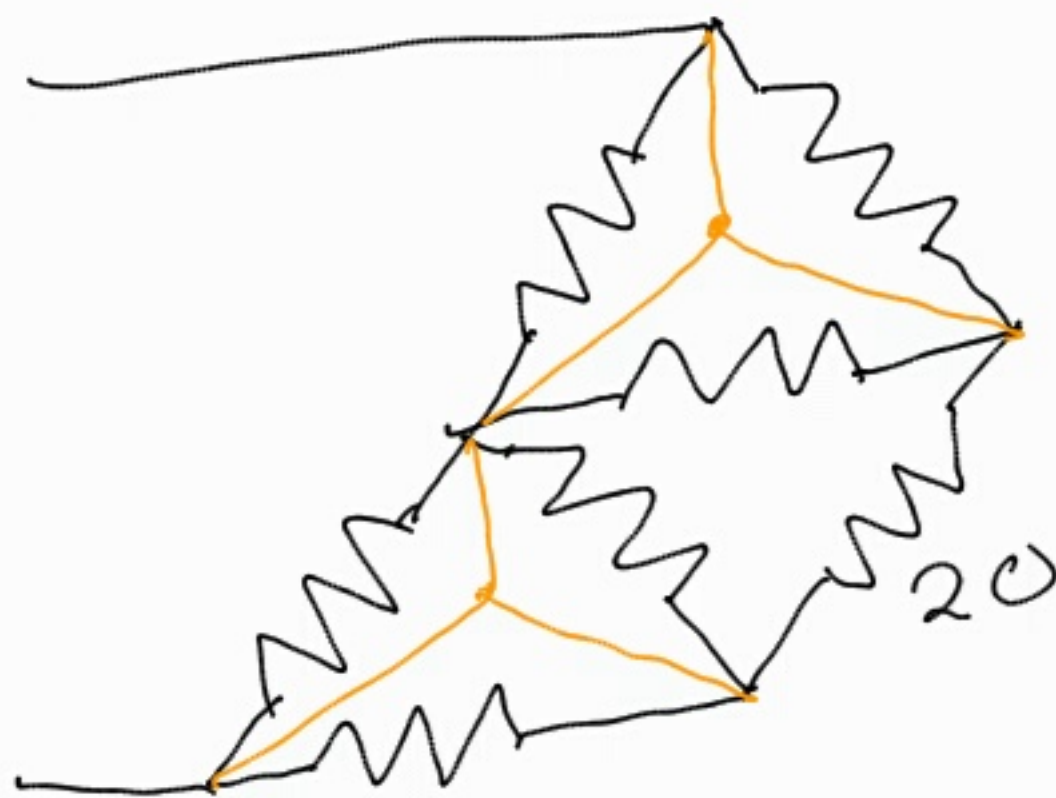

$$R_i = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$= \frac{30 \times 30}{30 + 30 + 30}$$

$$= 10 \Omega$$

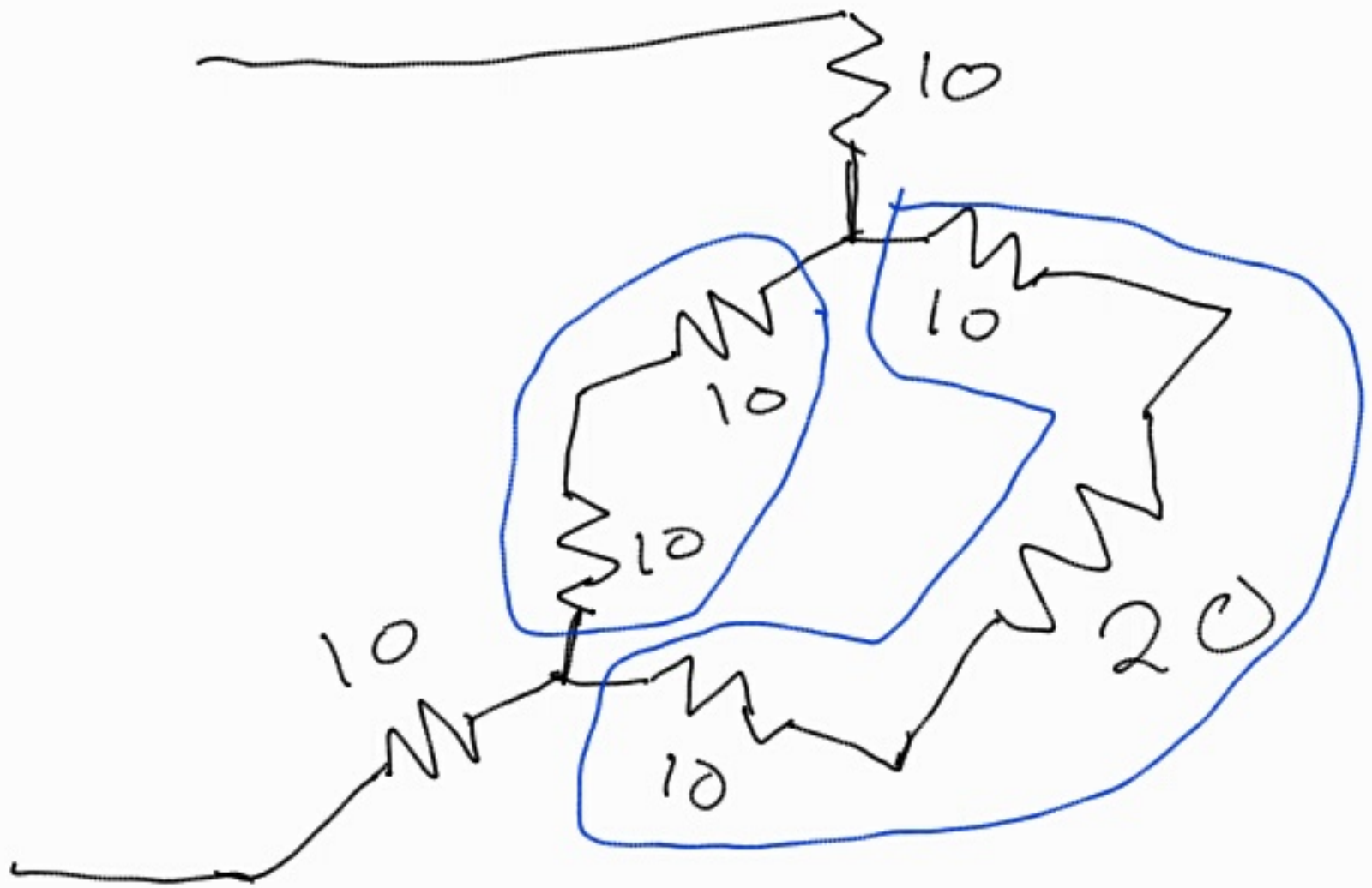

$$10 + 10 = 20 \Omega$$

$$10 + 20 + 10 = 40 \Omega$$

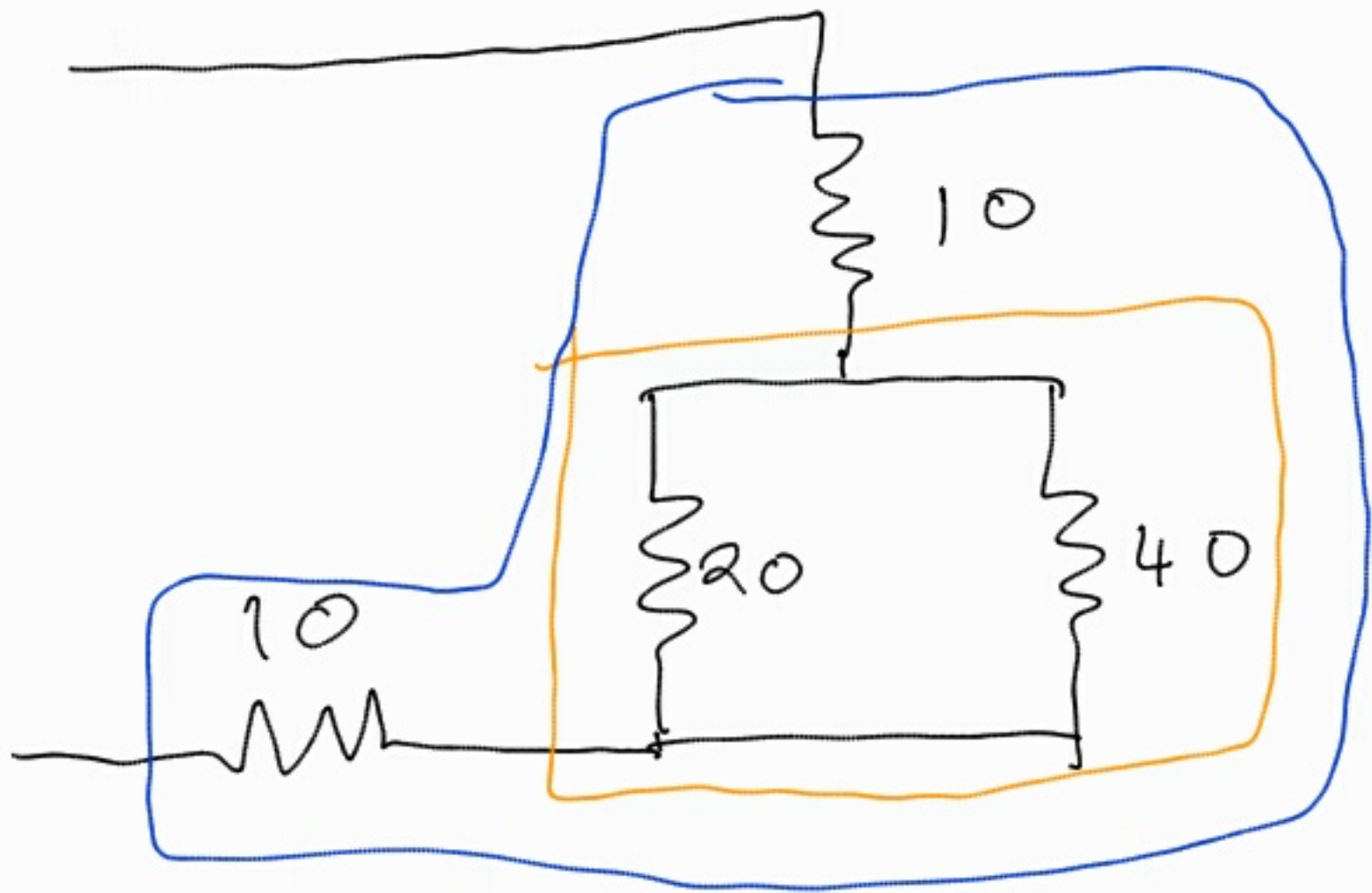


$$20 \parallel 40 = \frac{20 \times 40}{20 + 40}$$

$$= 13.333$$

$$R_{eq} = 10 + 13.333 + 10$$

$$= 33.333 \Omega$$

2,56

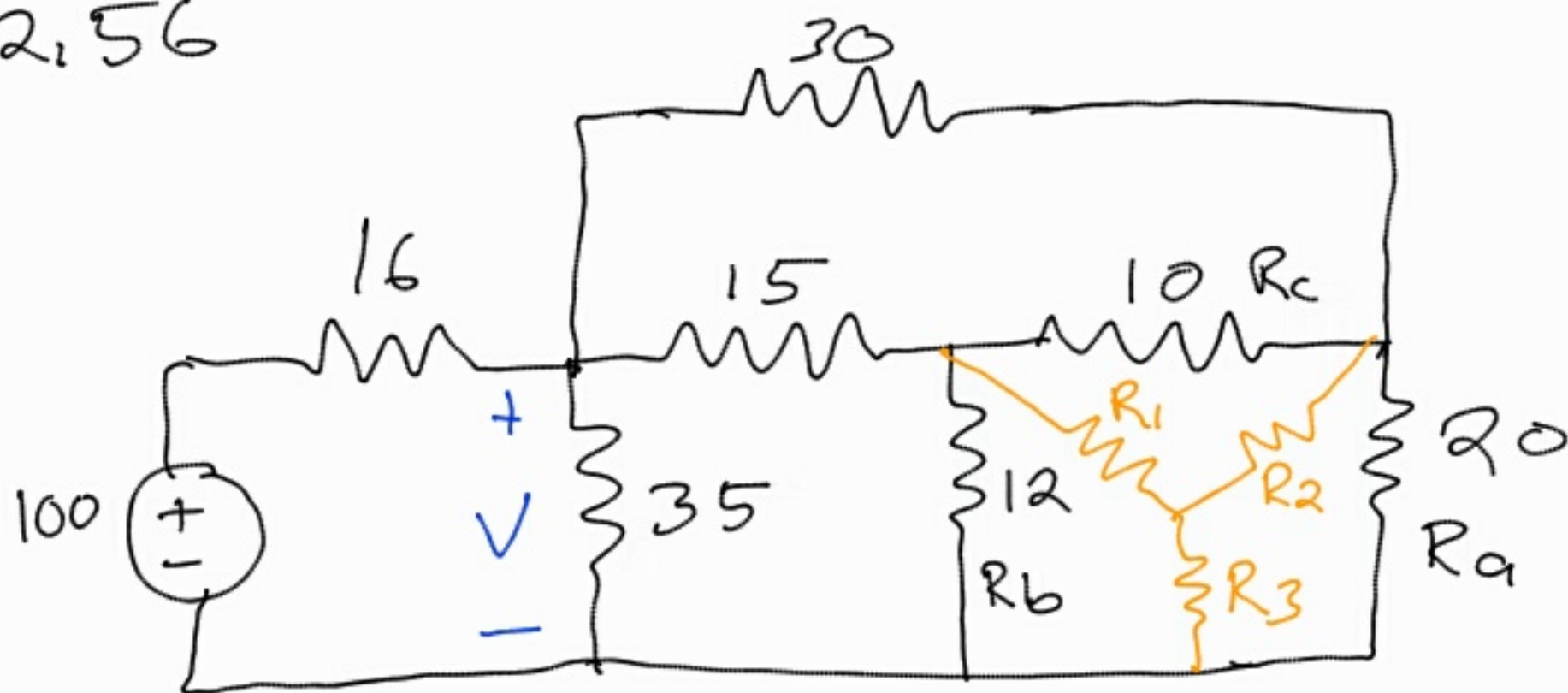


$$\begin{aligned}
 S &= R_a + R_b + R_c \\
 &= 20 + 12 + 10 \\
 &= 42 \Omega
 \end{aligned}$$

$$R_1 = \frac{R_b R_c}{S} = \frac{12 \times 10}{42} = 2,857 \Omega$$


$$R_2 = \frac{R_c R_a}{S} = \frac{10 \times 20}{42} = 4,762 \Omega$$
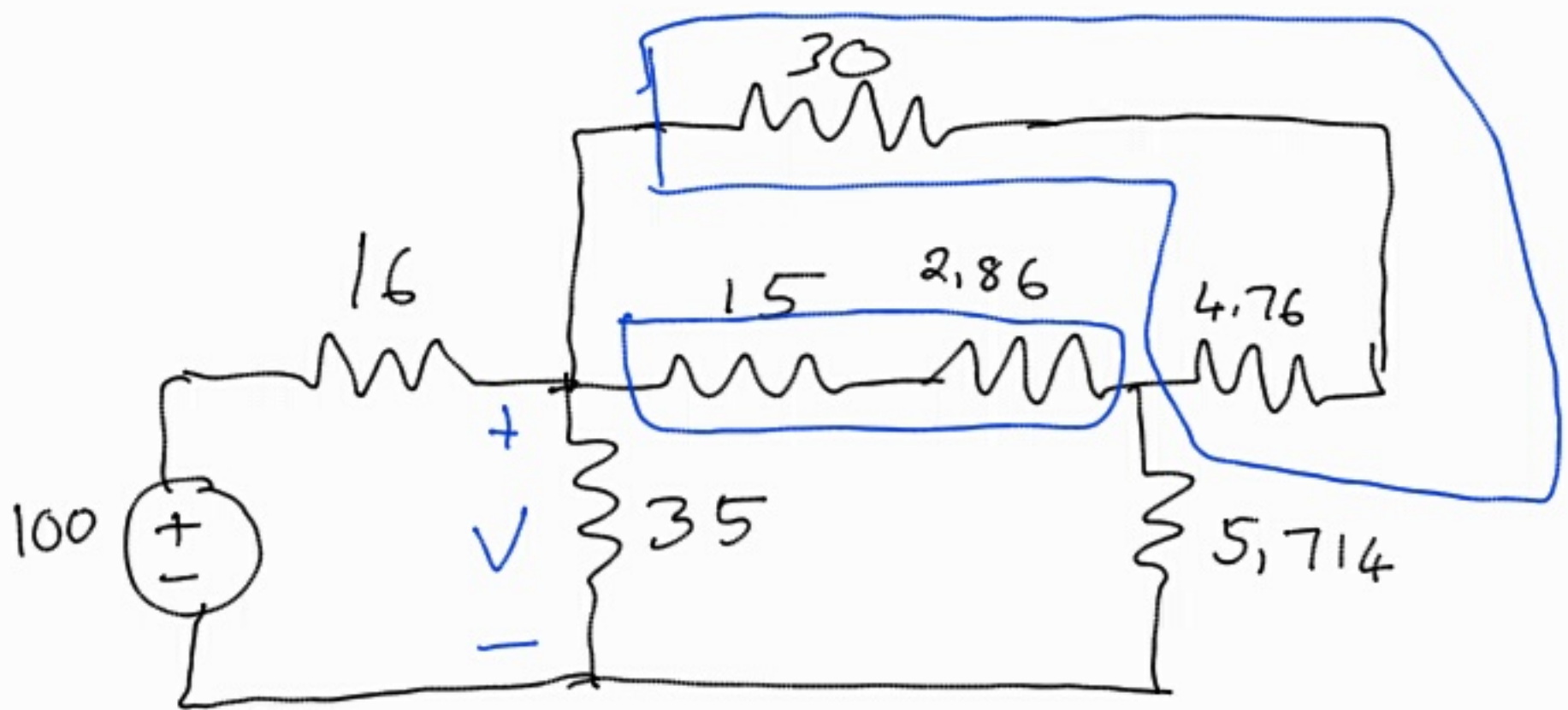
$$R_3 = \frac{R_a R_b}{S} = \frac{20 \times 12}{42} = 5,714 \Omega$$




$$15 + 2,857 = 17,857 \Omega$$

$$30 + 4,762 = 34,762$$

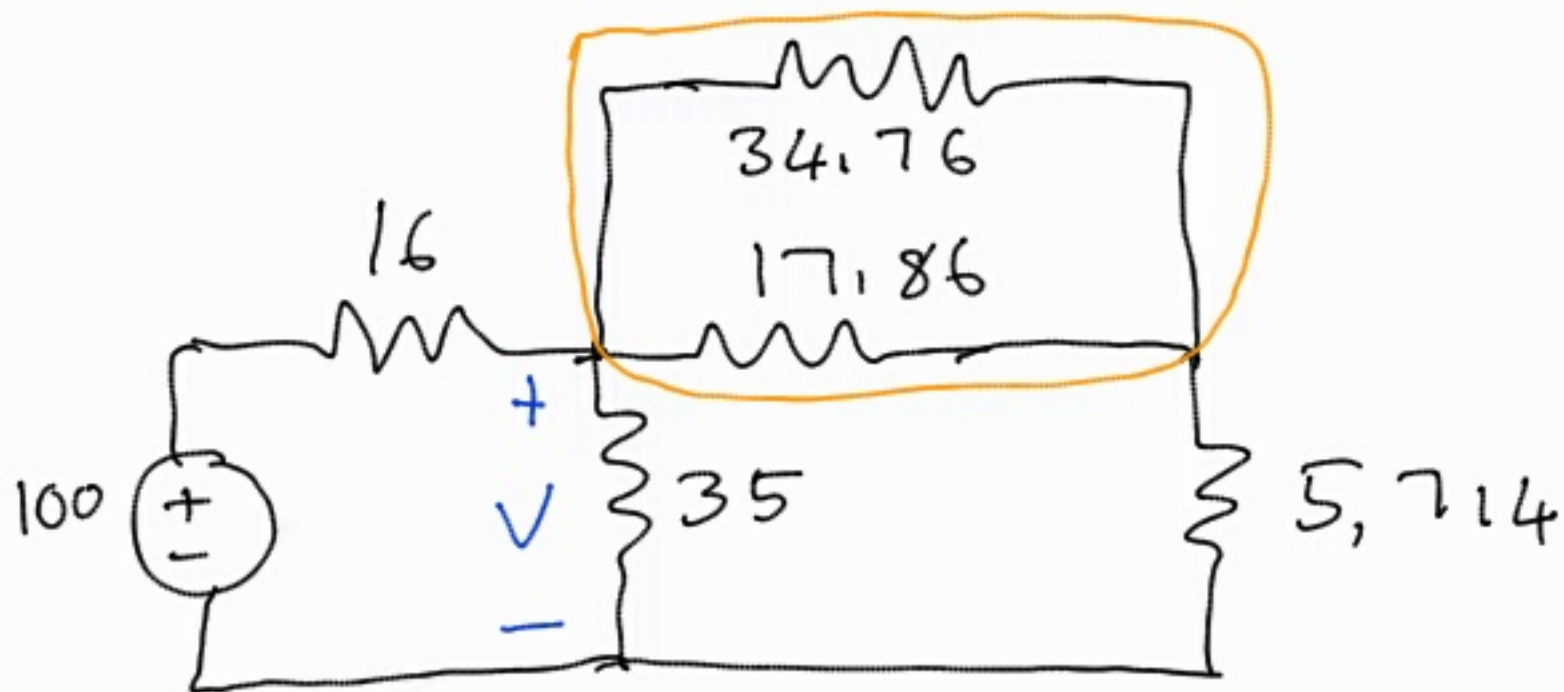

$$34,76 \parallel 17,86 = \frac{34,76 \times 17,86}{34,76 + 17,86}$$

$$= 11,798 \Omega$$

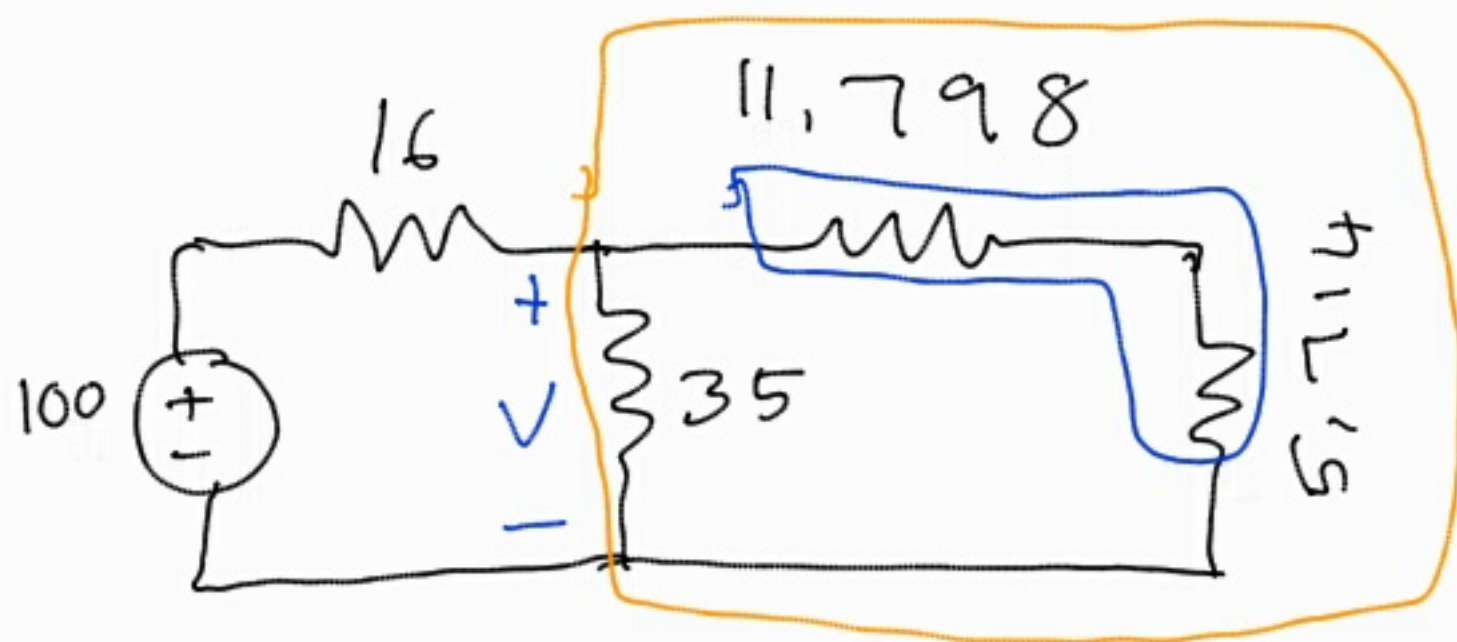


$$11,798 + 5,714 = 17,512$$

$$R_{eq} = 17,512 \parallel 35$$

$$= \frac{17,512 \times 35}{17,512 + 35}$$

$$= 11,672$$

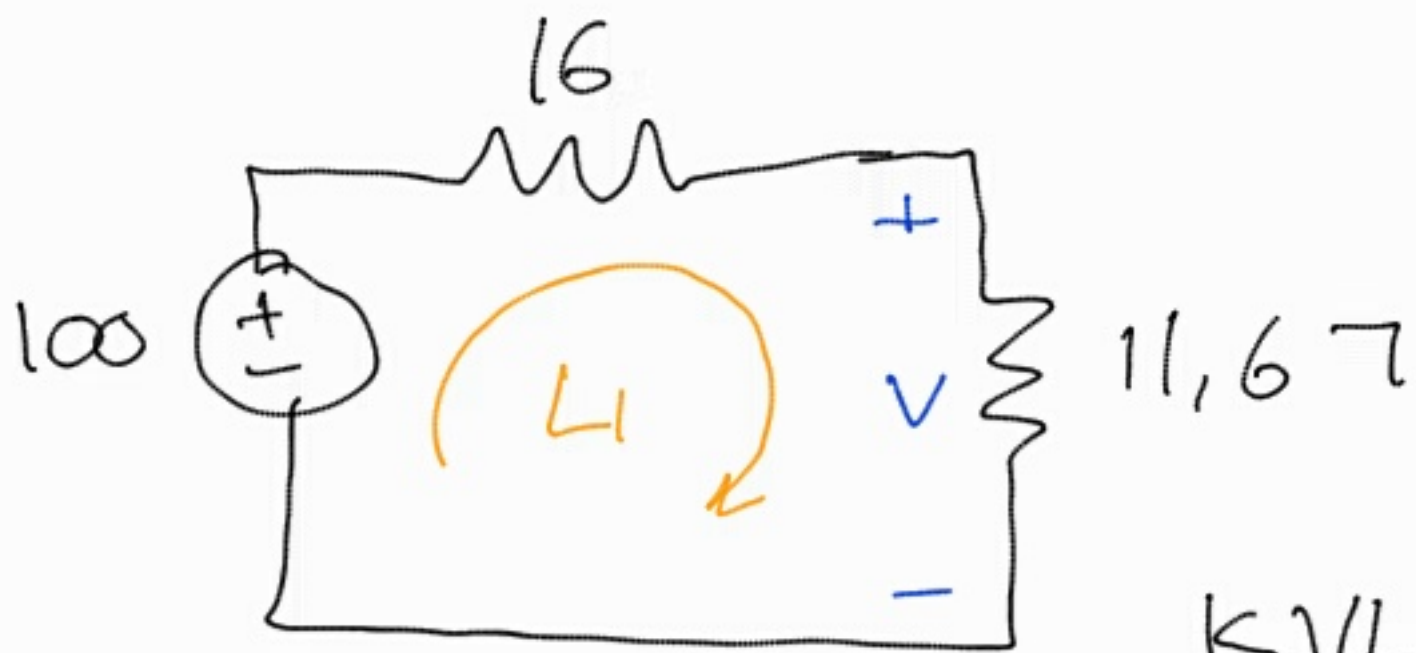

KVL ($\sum v = 0$)

$$-100 + 16I + 11,67I = 0$$

$$27,67I = 100$$

$$I = \frac{100}{27,67}$$

$$I = 3,614 \text{ A}$$

$$V = IR \text{ (Ohm's law)}$$

$$V = 3,614 \times 11,67$$

$$= 42,18 \text{ V}$$