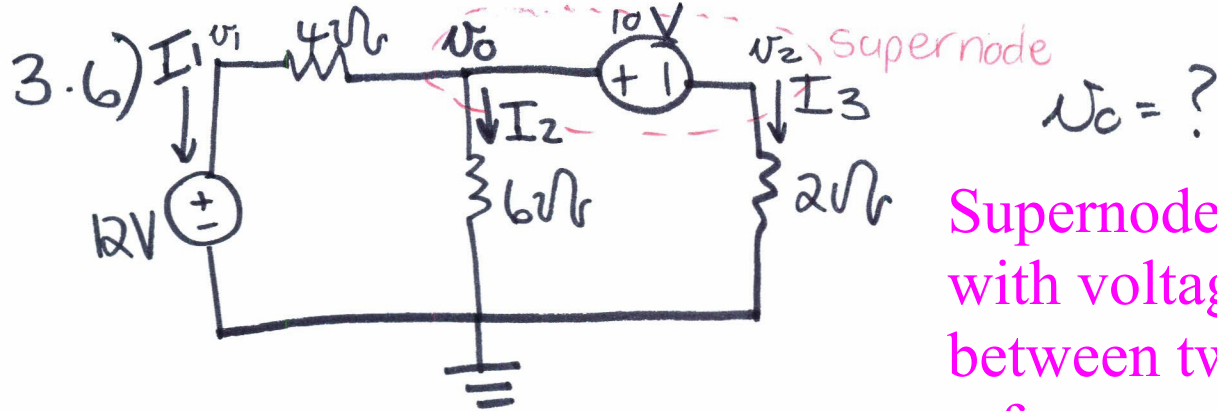




Supernode: Formed with voltage source between two non reference nodes

Nodal analysis: with Voltage sources.

Supernode: word gevorm met spannings bron tussen twee nie-verwysings nodes.


KCL: $I_1 + I_2 + I_3 = 0$

$$\frac{v_0 - v_1}{4} + \frac{v_0 - 0}{6} + \frac{v_2 - 0}{2} = 0$$

$$12(v_0 - v_1) + 8v_0 + 24v_2 = 0$$

$$20v_0 - 12v_1 + 24v_2 = 0 \dots\dots (1)$$

KVL op Supernode:

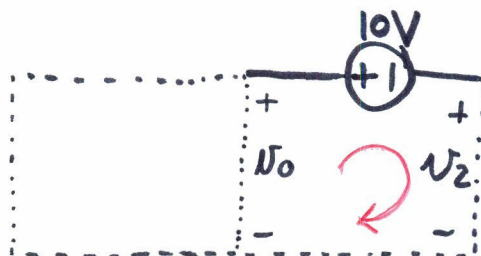

$$-v_0 + 10 + v_2 = 0$$

$$v_0 = 10 + v_2$$

$$v_2 = v_0 - 10 \dots\dots (2)$$


Substitute $v_1 = 12 \text{ V} \dots\dots (3)$

Vervang (3) & (2) in (1)

$$20v_0 - 12(12) + 24(v_0 - 10) = 0$$

$$44v_0 - 384 = 0$$

$$\underline{v_0 = 8.73 \text{ V}}$$

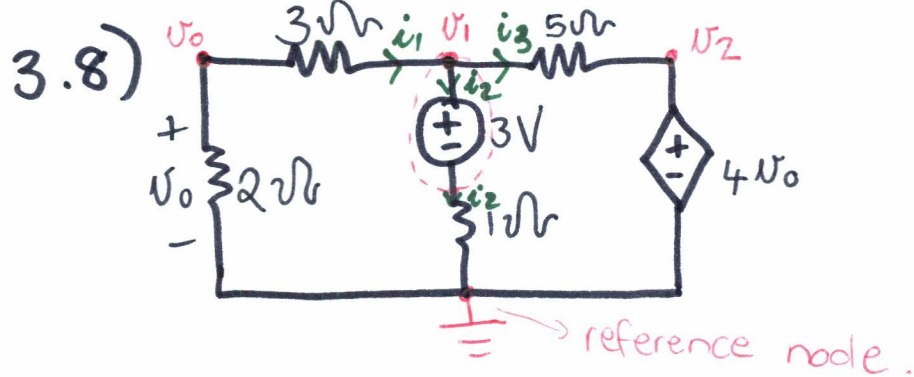

KCL node v_1 : $i_1 = i_2 + i_3$

$$\frac{v_0 - v_1}{3} = \frac{v_1 - 3}{1} + \frac{v_1 - v_2}{5}$$

$$5(v_0 - v_1) = 3(v_1 - 3) + 3(v_1 - v_2)$$

$$5v_0 - 5v_1 = 15v_1 - 45 + 3v_1 - 3v_2$$

$$5v_0 = 23v_1 - 3v_2 - 45 \quad \text{--- (1)}$$

$$v_2 = 4v_0 \quad \text{--- (2)}$$

$$v_0 = \frac{2}{2+3} \cdot v_1 \quad \text{--- (3)}$$


Voltage division
(8/44)

Vervang 2 & 3 in (1)

$$5v_0 = 23\left(\frac{5}{2}v_0\right) - 3(4v_0) - 45$$

$$-40.5v_0 = -45$$

$$v_0 = \frac{10}{9} = 1.111 \text{ V}$$

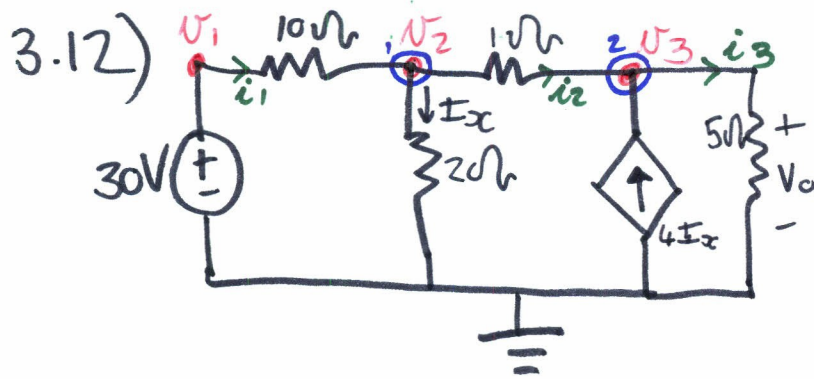

$V_0?$

③

KCL1: $i_1 - I_x - i_2 = 0$

$$\frac{v_1 - v_2}{10} - \frac{v_2 - 0}{20} - \frac{v_2 - v_3}{1} = 0$$

$$2(v_1 - v_2) - 10v_2 - 20(v_2 - v_3) = 0$$

$$2v_1 - 2v_2 - 10v_2 - 20v_2 + 20v_3 = 0$$

$$2v_1 - 32v_2 + 20v_3 = 0 \dots\dots ①$$

KCL2: $i_2 + 4I_x - i_3 = 0$

$$\frac{v_2 - v_3}{1} + 4I_x - \frac{V_0}{5} = 0$$

But!

Maar!

$$5(v_2 - v_3) + 20I_x - V_0 = 0$$

$$5v_2 - 5v_3 + 20I_x - V_0 = 0 \dots\dots ②$$

$$\underline{v_1 = 30} \rightarrow$$

$$\underline{v_3 = V_0} \rightarrow$$

$$\underline{I_x = \frac{v_2}{20}} \rightarrow$$

$$5v_2 - 5V_0 + 10v_2 - V_0 = 0$$

$$15v_2 - 6V_0 = 0$$

$$v_2 = \frac{6V_0}{15} \dots\dots ③$$

in ①

$$60 - 32\left(\frac{6V_0}{15}\right) + 20V_0 = 0$$


$$\frac{36}{5}V_0 = -60$$

$$V_0 = -8.333 \text{ V}$$



3.23)

(4)

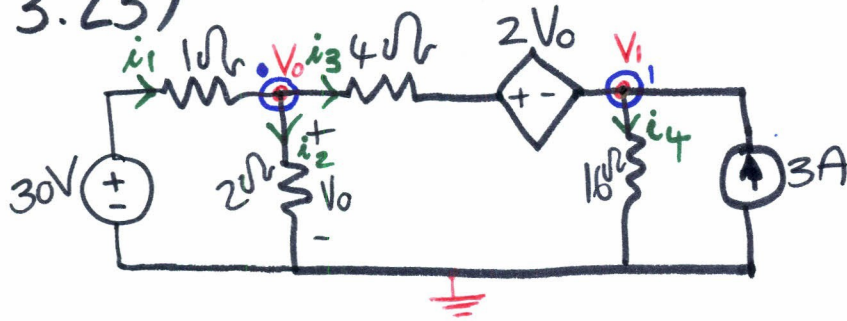

KCL: $i_1 - i_3 - i_2 = 0$

$$\frac{30 - V_0}{1} - \frac{V_0 - (2V_0 + V_1)}{4} - \frac{V_0 - 0}{2} = 0$$

$$8(30 - V_0) - 2(V_0 - (2V_0 + V_1)) - 4V_0 = 0$$

$$240 - 8V_0 - 2(-V_0 - V_1) - 4V_0 = 0$$

$$-10V_0 + 2V_1 + 240 = 0$$

$$V_1 = 5V_0 - 120 \quad (V)$$

KCL: $i_3 + 3 - i_4 = 0$

$$\frac{V_0 - (2V_0 + V_1)}{4} + 3 - \frac{V_1 - 0}{16} = 0$$

$$16(V_0 - (2V_0 + V_1)) + 192 - 4V_1 = 0$$

$$16(-V_0 - V_1) + 192 - 4V_1 = 0$$

$$-16V_0 - 16V_1 - 4V_1 + 192 = 0$$

$$-16V_0 - 20V_1 + 192 = 0$$

$$-16V_0 - 20(5V_0 - 120) + 192 = 0$$

$$-16V_0 - 100V_0 + 2400 + 192 = 0$$


$$-116V_0 + 2592 = 0$$

$$-116V_0 = -2592$$

$$V_0 = 22.34 \text{ V}$$

3.41)

⑤

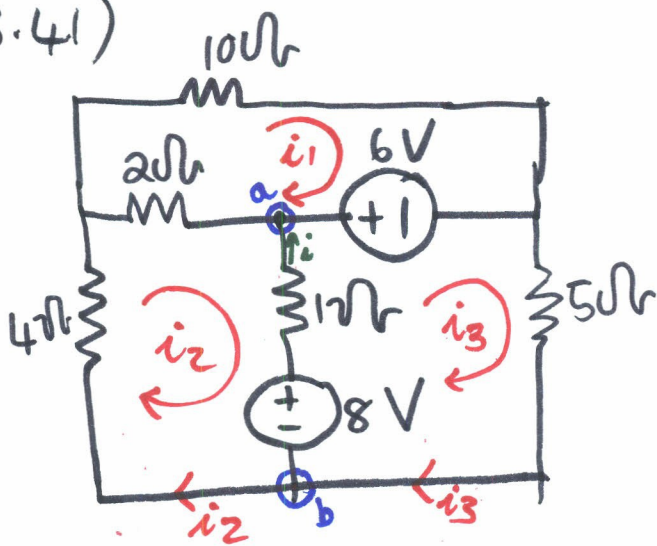

$$\text{KCL: } i_1 + i_2 = i_3$$

mesh is a loop
without any other loops
within.

$$\begin{aligned} \text{For loop 1: } 10i_1 - 6 + 2(i_1 - i_2) &= 0 \\ 12i_1 - 2i_2 + 0i_3 &= 6 \\ 6i_1 - i_2 + 0i_3 &= 3 \quad \dots\dots ① \end{aligned}$$

$$\begin{aligned} \text{For loop 2: } 4i_2 + 2(i_2 - i_1) + 1(i_2 - i_3) + 8 &= 0 \\ -2i_1 + 7i_2 - i_3 &= -8 \\ 2i_1 - 7i_2 + i_3 &= 8 \quad \dots\dots ② \end{aligned}$$

$$\begin{aligned} \text{For loop 3: } 6 + 5i_3 - 8 + 1(i_3 - i_2) &= 0 \\ 0i_1 - i_2 + 6i_3 &= 2 \quad \dots\dots ③ \end{aligned}$$

Sit ①, ② en ③ in matrics.

$$\begin{bmatrix} 6 & -1 & 0 \\ 2 & -7 & 1 \\ 0 & -1 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 8 \\ 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -1 & 0 \\ 2 & -7 & 1 \\ 0 & -1 & 6 \end{vmatrix} = \begin{vmatrix} a & b & c \\ d & e & f \\ g & h & i \end{vmatrix} = a \begin{vmatrix} e & f \\ h & i \end{vmatrix} - b \begin{vmatrix} d & f \\ g & i \end{vmatrix} + c \begin{vmatrix} d & e \\ g & h \end{vmatrix}$$

$$\therefore \Delta = -234$$

$$\Delta_2 = \begin{vmatrix} 6 & 3 & 0 \\ 2 & 8 & 1 \\ 0 & 2 & 6 \end{vmatrix} = 240$$


6

$$\Delta_3 = \begin{vmatrix} 6 & -1 & 3 \\ 2 & -7 & 8 \\ 0 & -1 & 2 \end{vmatrix} = -38$$

Vir i

$$\begin{aligned} i &= i_3 - i_2 \\ &= \frac{\Delta_3 - \Delta_2}{\Delta} = \frac{-38 - 240}{-234} = 1.188 A \end{aligned}$$

3.44)

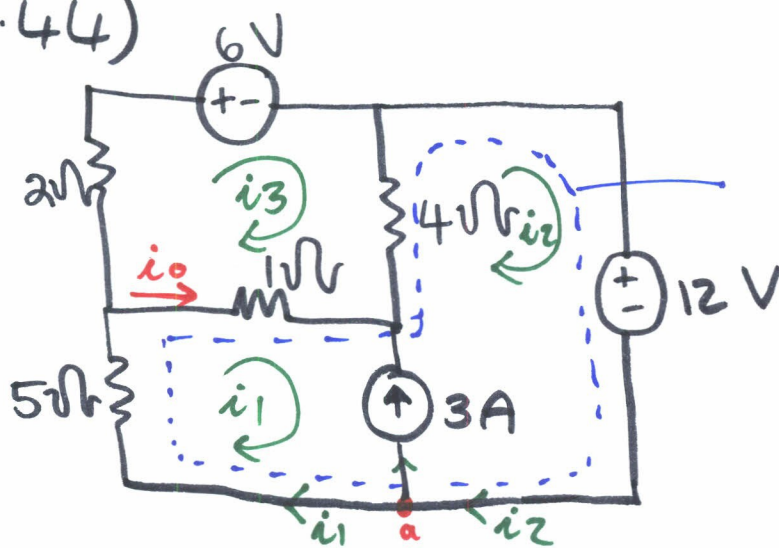Soek i_0 ?

⑦

Supermesh: if 2 meshes have a (dependent or independent current source in common.

For the Supermesh:

$$12 + 5i_1 + 1(i_1 - i_3) + 4(i_3 - i_2) = 0$$

$$6i_1 - 4i_2 + 3i_3 = -12$$

$$-6i_1 + 4i_2 - 3i_3 = 12 \dots\dots\dots ①$$

For loop 3: $+6 + 4(i_3 - i_2) + 1(i_3 - i_1) + 2i_3 = 0$

$$-i_1 - 4i_2 + 7i_3 = -6$$

$$i_1 + 4i_2 - 7i_3 = 6 \dots\dots\dots ②$$

KCLa: $i_1 + 3 = i_2 \dots\dots\dots ③$

vervang ③ in ①

$$-6i_1 + 4(i_1 + 3) - 3i_3 = 12$$

$$-2i_1 + 12 - 3i_3 = 12$$

$$-2i_1 - 3i_3 = 0$$

$$2i_1 = -3i_3$$

$$i_1 = -\frac{3}{2}i_3 \dots\dots\dots ④$$

vervang ③ in ②


$$i_1 + 4(i_1 + 3) - 7i_3 = 6$$

$$5i_1 + 12 - 7i_3 = 6 \dots\dots\dots ⑤$$

vervang ⑤ in ④

$$5\left(-\frac{3}{2}\right)i_3 + 12 - 7i_3 = 6$$

3.51)

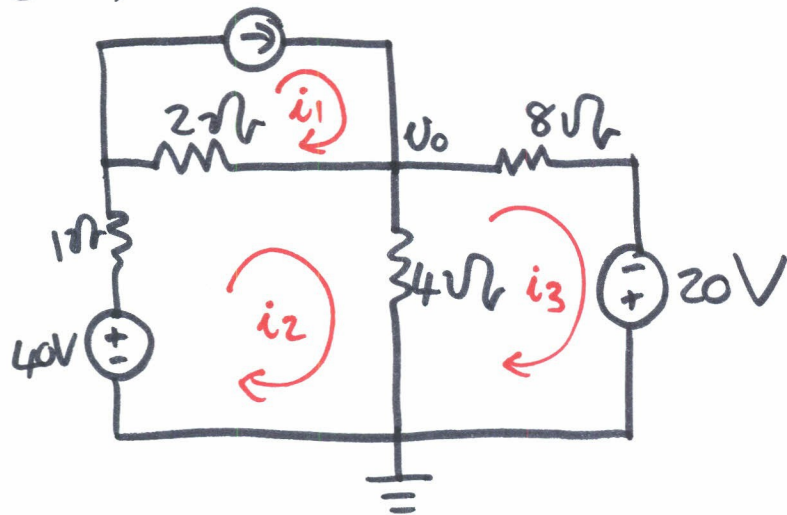 $v_o?$

loop 1: $i_1 = 5A \dots \textcircled{1}$

loop 2: $-40 + i_2 + 2(i_2 - i_1) + 4(i_2 - i_3) = 0$
 $-2i_1 + 7i_2 - 4i_3 - 40 = 0 \dots \textcircled{2}$

loop 3: $-20 + 4(i_3 - i_2) + 8i_3 = 0$
 $-4i_2 + 12i_3 - 20 = 0 \dots \textcircled{3}$

Subst. ① in ②

$$7i_2 - 4i_3 = 50 \dots \textcircled{5}$$

from ③ $-4i_2 + 12i_3 = 20$

$$i_2 - 3i_3 = -5$$

$$i_2 = -5 + 3i_3 \dots \textcircled{4}$$

Subst. ④ in ⑤

$$7(-5 + 3i_3) - 4i_3 = 50$$

$$-35 + 21i_3 - 4i_3 = 50$$

$$17i_3 = 85$$

$$i_3 = 5A \rightarrow$$


$$\therefore i_2 = 10A \rightarrow$$

$$v_o = (-i_3 + i_2)(R)$$

$$= (-5 + 10)(4)$$

3.26)

9

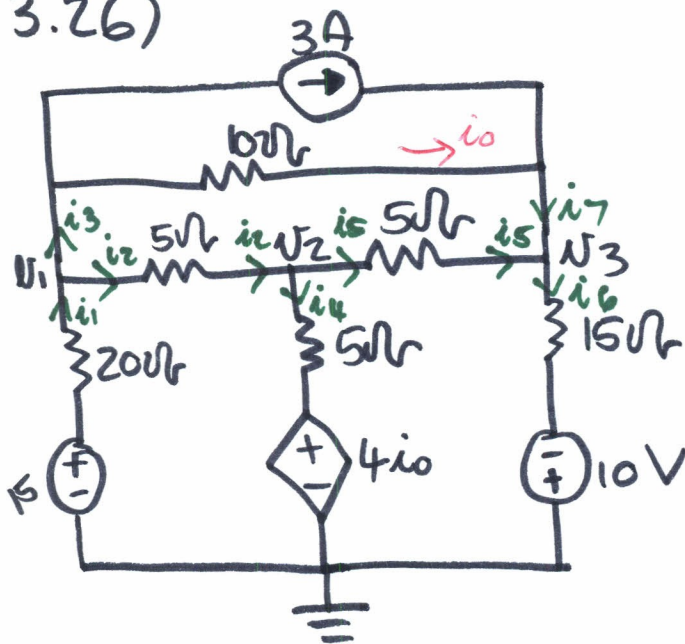Soek V_1, V_2 & V_3 ?Node 1: $i_1 = i_3 + i_2$

$$\frac{15 - V_1}{20} = \left(3 + \frac{V_1 - V_3}{10}\right) + \frac{V_1 - V_2}{5}$$

$$\therefore 7V_1 - 4V_2 - 2V_3 = -45 \dots \textcircled{1}$$

Node 2: $i_2 = i_4 + i_5$

$$\frac{V_1 - V_2}{5} = \frac{4i_o - V_2}{5} + \frac{V_2 - V_3}{5} \dots \textcircled{2}$$

$$i_o = \frac{V_1 - V_3}{10} \dots \textcircled{3}$$

vervang $\textcircled{3}$ in $\textcircled{2}$

$$0 = 7V_1 - 15V_2 + 3V_3 \dots \textcircled{4}$$

Node 3: $i_5 = i_6 - i_7$

$$\frac{V_2 - V_3}{5} = \frac{V_3 - (-10)}{15} + 3 + \frac{V_1 - V_3}{10}$$

$$\therefore 70 = -3V_1 - 6V_2 + 11V_3 \dots \textcircled{5}$$

10



10

10

10

10

10

10

10


10

10

10

10

3.46)

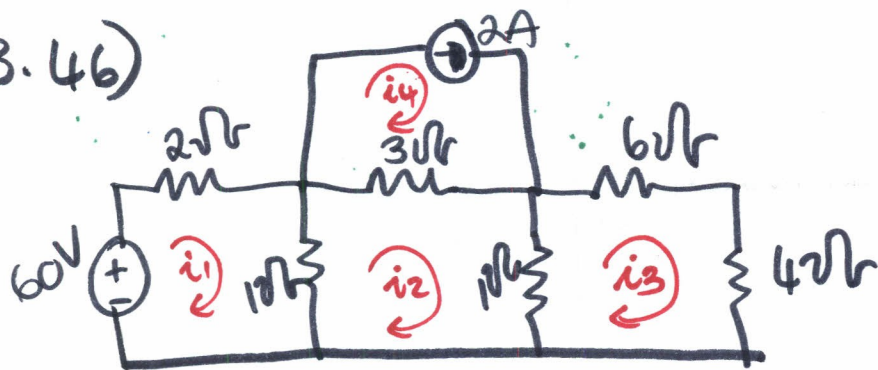

mesh analysis:

$$\text{mesh 1: } -60 + 2i_1 + 1(i_1 - i_2) = 0$$

$$3i_1 - i_2 = 60 \dots \dots \textcircled{1}$$

$$\text{mesh 2: } 1(i_2 - i_1) + 3(i_2 - i_4) + 1(i_2 - i_3) = 0$$


$$-i_1 + 5i_2 - i_3 - 3i_4 = 0 \dots \dots \textcircled{2}$$

$$\text{mesh 3: } 10i_3 + 1(i_3 - i_2) = 0$$

$$-i_2 + 11i_3 = 0 \dots \dots \textcircled{3}$$

$$\text{mesh 4: } \underline{i_4 = 2A}, \dots \dots \textcircled{4}$$

3.49)

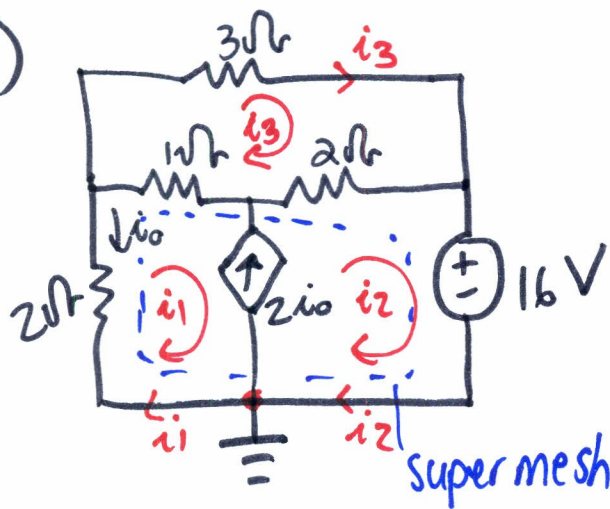

$i_o?$
 $i_3?$

12

KCL ground: $i_1 + 2i_o = i_2$

For the super mesh:

$$2i_1 + 1(i_1 - i_3) + 2(i_2 - i_3) + 16 = 0$$

$$3i_1 + 2i_2 - 3i_3 + 16 = 0 \quad \dots \textcircled{1}$$

at node $\perp$ $i_1 + 2i_o = i_2$

$$i_o = -i_1$$

$$\therefore i_2 = -i_1 \quad \dots \textcircled{2}$$

loop 3: $3i_3 + 2(i_3 - i_2) + 1(i_3 - i_1) = 0$


$$-i_1 - 2i_2 + 6i_3 = 0$$

$$\therefore 6i_3 = -i_1 \quad \dots \textcircled{3}$$

54)

13

use mesh analysis:

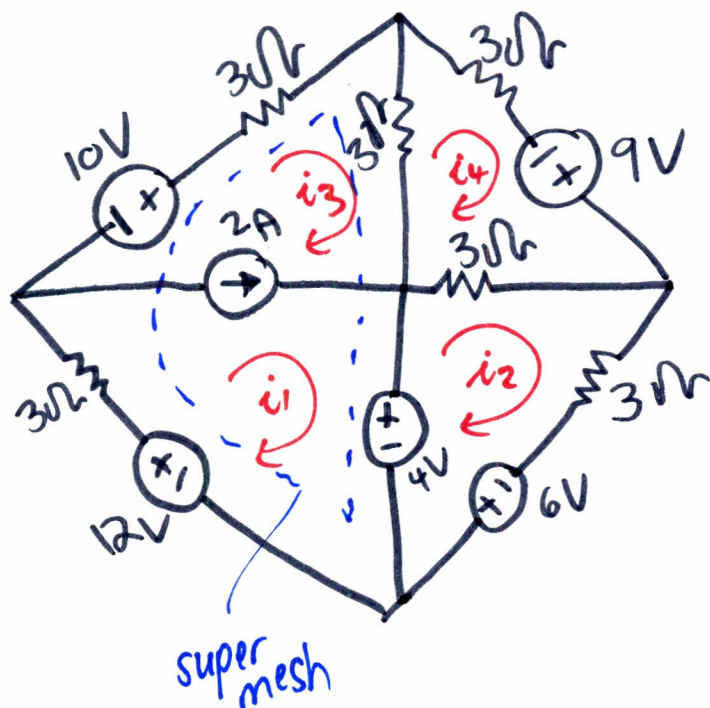

$$i_1 - i_3 = 2 \dots \textcircled{4}$$

From mesh ① & ③:

$$-10 + 3i_3 + 3(i_3 - i_4) + 4 - 12 + 3i_1 = 0$$

$$3i_1 + 0i_2 + 6i_3 - 3i_4 - 18 = 0 \dots \textcircled{1}$$

From mesh ②:

$$-4 + 3(i_2 - i_4) + 3i_2 - 6 = 0$$

$$6i_2 - 3i_4 - 10 = 0 \dots \textcircled{2}$$

mesh 4:

$$-9 + 3(i_4 - i_2) + 3(i_4 - i_3) + 3(i_4) = 0$$

$$-3i_2 - 3i_3 + 9i_4 - 9 = 0 \dots \textcircled{3}$$